

EE 221 – Circuits II

Homework #10

10 points

Date Assigned: 10/20

Date Due: 10/30

- 10.1 Text problem 16.1.
- 10.2 Text problem 16.4.
- 10.3 Text problem 16.11. The voltage is across a parallel combination of an L and C , which are connected through R to the source voltage.
- 10.4 Text problem 16.17.
- 10.5 Text problem 16.18.
- 10.6 Text problem 16.19.
- 10.7 Text problem 16.64.
- 10.8 Text problem 16.71.
- 10.9 Text problem 16.83.
- 10.10 Text problem 16.96.
- 10.11 Text problem 16.97.