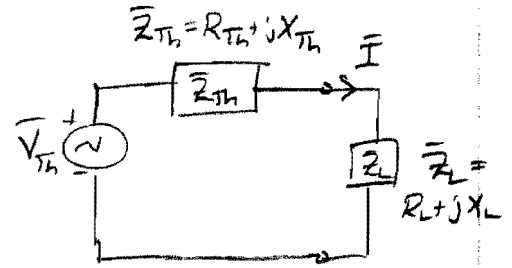


## Problem 2.1

$$\bar{I} = \frac{\bar{V}_{Th}}{\bar{Z}_{Th} + \bar{Z}_L} = \frac{\bar{V}_{Th}}{(R_{Th} + jX_{Th}) + (R_L + jX_L)} \quad (1)$$



The time avg. power  $P$  delivered to the load will be consumed entirely in  $R_L$  (none in  $X_L$ ). Consequently,

$$P = \frac{1}{2} |\bar{I}|^2 \cdot R_L$$

$$|\bar{I}|^2 = \bar{I} \cdot \bar{I}^* = \frac{|\bar{V}_{Th}|^2}{\left[ (R_{Th} + R_L) + j(X_{Th} + X_L) \right] \cdot \left[ (R_{Th} + R_L) + j(X_{Th} + X_L) \right]^*}$$

$$= \frac{|\bar{V}_{Th}|^2}{(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2}$$

$$\therefore P = \frac{1}{2} \frac{|\bar{V}_{Th}|^2 \cdot R_L}{(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2} \quad (2) \leftarrow (11.15)$$

To maximize this fact, we note it depends on two variables. So, we'll take partial derivatives wrt  $R_L$  &  $X_L$  setting each to zero separately:

$$\frac{\partial P}{\partial R_L} = 0 \quad ; \quad \frac{\partial P}{\partial X_L} = 0$$

From these two equations we'll find those  $R_L$  &  $X_L$  that produce maximum time avg power deposited in  $Z_L$ .

$$\frac{\partial P}{\partial R_L} = \frac{|\bar{V}_{Th}|^2}{2} \frac{\partial (2)}{\partial R_L} = \frac{|\bar{V}_{Th}|^2}{2} \left[ (R_{Th} + R_L)^2 + (X_{Th} + X_L)^2 \right]^{-2} \frac{\partial R_L}{\partial R_L} -$$

$$= \frac{|\bar{V}_{Th}|^2}{2} \frac{\left[ (R_{Th} + R_L)^2 + (X_{Th} + X_L)^2 \right] \frac{\partial R_L}{\partial R_L} - R_L \cdot \frac{\partial}{\partial R_L} \left[ (R_{Th} + R_L)^2 + (X_{Th} + X_L)^2 \right]}{\left[ (R_{Th} + R_L)^2 + (X_{Th} + X_L)^2 \right]^2}$$

$$= \frac{|\bar{V}_{Th}|^2}{2} \frac{(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2 - R_L \cdot 2 \cdot (R_{Th} + R_L)}{\left[ (R_{Th} + R_L)^2 + (X_{Th} + X_L)^2 \right]^2} = 0$$

Quotient Rule:

$$\Rightarrow R_{Th}^2 + R_L^2 + 2R_{Th}R_L - 2R_{Th}R_L - 2R_L^2 + (X_{Th} + X_L)^2 = 0$$

$$\text{or } R_L^2 = R_{Th}^2 + (X_{Th} + X_L)^2$$

$$\therefore R_L = \pm \sqrt{R_{Th}^2 + (X_{Th} + X_L)^2} \quad (11.18)$$

Then for

$$\frac{\partial P}{\partial X_L} = \frac{|\bar{V}_{Th}|^2}{2} \frac{\partial (2)}{\partial X_L} \stackrel{\text{Quotient Rule}}{=} \frac{|\bar{V}_{Th}|^2}{2} \cdot \frac{0 - R_L \cdot 2(X_{Th} + X_L)}{[(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2]^2} = 0$$

$$\Rightarrow \underline{X_L = -X_{Th}} \quad (11.17)$$

Sub. (11.17) into (11.18) gives


$$\underline{R_L} = \pm \sqrt{R_{Th}^2} = \underline{R_{Th}} \quad (3)$$

Consequently, for max. power transfer from the Thevenin circuit to the load

$$\underline{Z_L} = R_L + jX_L = \underbrace{R_{Th}}_{(3)} - j \underbrace{X_{Th}}_{(11.17)} = \underline{Z_{Th}^*} \quad (11.19)$$

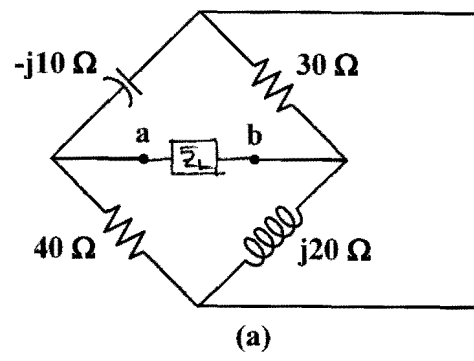**Solution 11.17**


We find  $Z_{eq}$  at terminals a-b following Fig. (a).



$$Z_{eq} = (-j10 + 30) \parallel (j20 + 40) = \frac{(30 - j10)(40 + j20)}{70 + j10} = 20 \Omega = Z_L^*$$

max power  $\times \frac{1}{2}$   
↓

We obtain  $V_{Thev}$  from Fig. (b).

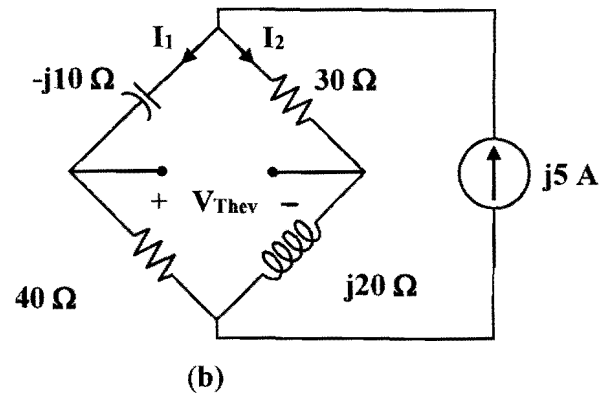

Using current division,


$$I_1 = \frac{30 + j20}{70 + j10} (j5) = -1.1 + j2.3 \text{ A}$$

$$I_2 = \frac{40 - j10}{70 + j10} (j5) = 1.1 + j2.7 \text{ A}$$

$$V_{Th} = 30I_2 + j10I_1 = 10 + j70 \text{ V}$$

or  $\bar{V}_{Th} = 40\bar{I}_1 - j20\bar{I}_2 = 10 + j70 \text{ V}$

or,  $P_{max} = \frac{1}{2} |\bar{I}|^2 R_L$   
 $= \frac{1}{2} \frac{|\bar{V}_{Th}|^2 R_L}{|Z_{Th} + Z_L|^2}$   
 $= \frac{1}{2} \frac{(70)^2 \cdot 20}{(20 + 20)^2}$   
 $= \underline{\underline{31.25 \text{ W}}}$

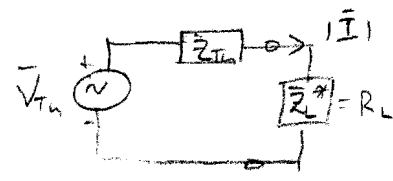

$$P_{max} = \frac{|\bar{V}_{Th}|^2}{2(Z_{eq} + Z_L)^2} Z_L = \frac{5000}{(2)(2 \times 20)^2} 20 = 31.25 \text{ W}$$

**Solution 11.19**

The variable resistor  $R$  in the circuit of Fig. 11.50 is adjusted until it absorbs the maximum average power. Find  $R$  and the ~~maximum~~ average power absorbed. *for this  $R$ .*

*available amongst all possible  $R$  values.*


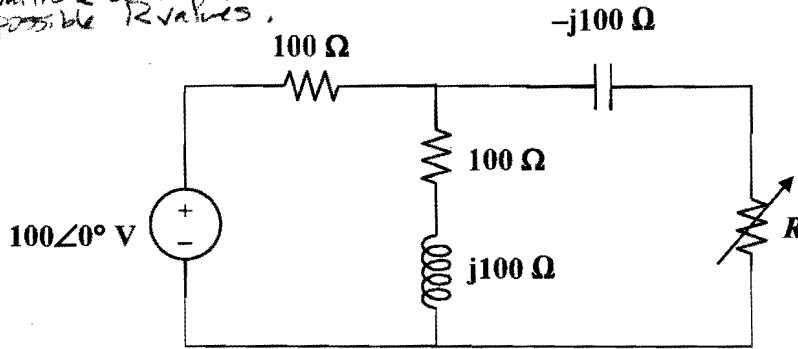


Figure 11.50  
For Prob. 11.19.

**Solution**

Step 1. We first remove  $R$  from the circuit and then find the Thevenin equivalent circuit. Once we have  $V_{Thev}$  and  $Z_{eq}$  we then know that for maximum power transfer to the load,  $R$  must be equal to  $|Z_{eq}|$  and  $P_{avg} = |V_{Thev}|^2 / (8R)$ . We now find  $V_{Thev}$  by writing and solving a nodal equation for the circuit shown below. To find  $Z_{eq}$ , we just set the source to zero (a short) and determine the impedance looking in from the right.  $Z_{eq} = -j100 + 100(100+j100)/(100+100+j100)$ .

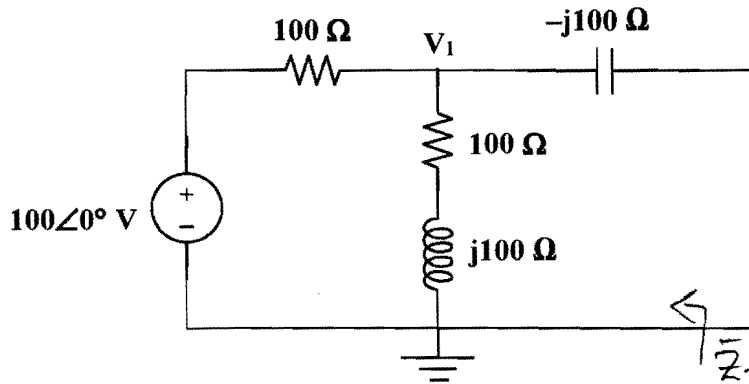*Not +ve!  
Only +ve if  
 $Z_L = Z_{Th}^*$*



$$V_{oc} = V_{Th} = \frac{100 + j100}{100 + j100 + 100} \cdot 100 \text{ V}$$

$$= 60 + j20 \text{ V}$$

$$Z_{Th} = Z_{eq} = -j100 + [(100 + j100) \parallel 100]$$

$$= 60 - j80 \Omega$$

$$[(V_1 - 100)/100] + [(V_1 - 0)/(100 + j100)] + 0 = 0 \text{ and } V_{oc} = V_{Thev} = V_1.$$

Step 2.  $Z_{eq} = -j100 + 100(1.4142 \angle 45^\circ) / (2.2361 \angle 26.57^\circ) = -j100 + 63.244 \angle 18.43^\circ$   
 $= -j100 + 60 + j20 = (60 - j80) \Omega = 100 \angle -53.13^\circ \Omega.$

The node equation becomes,  $(0.01 + 0.005 - j0.005)V_1 = 1 = 0.0158114 \angle -18.43^\circ V_1$  or  $V_1 = 63.246 \angle 18.43^\circ$ . Thus,


*or use voltage division*

From (11.18) w/  $X_L = 0 \Rightarrow R_L = |\bar{Z}_{Th}| = \underline{100 \Omega}$  will draw the most power from Thevenin  $\bar{E}_{Th}$ , cct than all possible  $R_L$  values.


$$R = 100 \Omega$$

$$\text{and } |\mathbf{I}| = 63.246 / |60 - j80 + 100| = 63.246 / 178.885 = 0.353557 \text{ A and}$$

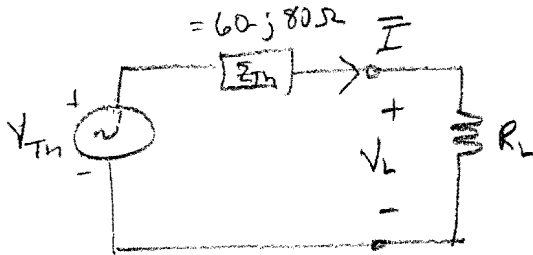
$$\text{the maximum } P_{\text{avg}} = [(0.353557)^2 / 2] 100 = \underline{\underline{6.25 \text{ W}}}.$$



## Prob. 2.4

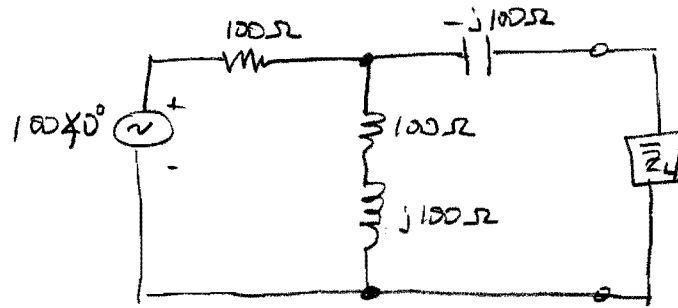Fig 11.50 but variable  $R \rightarrow \bar{Z}_L$ :

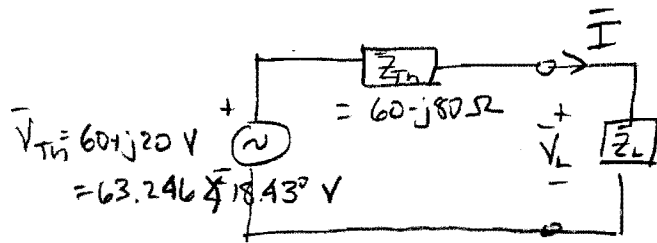From previous problem, the Thevenin equiv. circ. is



To extract maximum time avg. power from the circuit, select

$$\bar{Z}_L = \bar{Z}_{Th}^* = (60 - j80)^* = 60 + j80 \Omega$$

$$\bar{I} = \frac{\bar{V}_{Th}}{\bar{Z}_{Th} + \bar{Z}_{Th}^*} = \frac{60 + j20}{60 - j80 + 60 + j80} = 0.5270 \angle 18.43^\circ \text{ A.}$$

$$P_{\bar{Z}_L} = \frac{1}{2} \text{Re}(\bar{V}_L \cdot \bar{I}^*) = \frac{1}{2} \text{Re}(\bar{I} \cdot \bar{Z}_L \cdot \bar{I}^*) = \frac{1}{2} \text{Re}(|\bar{I}|^2 \cdot \bar{Z}_L)$$

$$= \frac{1}{2} |\bar{I}|^2 \cdot \text{Re}(\bar{Z}_L) = \frac{1}{2} |\bar{I}|^2 \cdot R_L$$

$$\therefore \underline{P_{\bar{Z}_L}} = \frac{1}{2} 0.5270^2 \cdot 60 = \underline{8.33 \text{ W}}$$

This is different from the previous problem, and greater. With a conjugate matched load, we have satisfied the maximum power transfer theorem. No load will extract more time avg. power from the circuit than this one.

Because we have conjugate<sup>2</sup> matched, eqn. (11.20) is applicable:

$$\underline{P_{\max}} = \frac{|\bar{V}_{Th}|^2}{8R_{Th}} = \frac{63.246^2}{8 \cdot 60} = \underline{8.33 \text{ W}}$$

**Solution 11.23**

Using Fig. 11.54, design a problem to help other students to better understand how to find the rms value of a waveshape.

**Problem**

Determine the rms value of the voltage shown in Fig. 11.54. Choose  $V_p = 10\text{ V}$ ;  $T = 3\text{ s}$ .

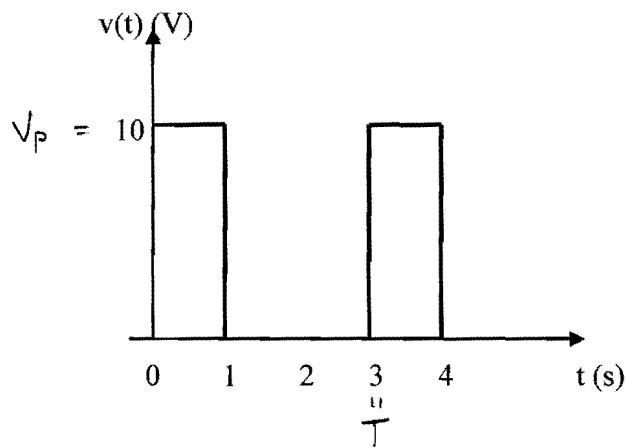


Figure 11.54 For Prob. 11.23.

By definition,

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$

$$\text{or } V_{rms}^2 = \frac{1}{T} \int_0^T v^2(t) dt$$

$$\therefore V_{rms}^2 = \frac{1}{T} \int_0^{T/3} v^2(t) dt + \frac{1}{T} \int_{T/3}^T 0^2 dt$$

$$= \frac{10^2}{3} + \frac{0}{3}$$


**Solution**

$$V_{rms}^2 = \frac{1}{T} \int_0^T v^2(t) dt = \frac{1}{3} \int_0^1 10^2 dt = \frac{100}{3}$$

$$\underline{\underline{V_{rms} = 5.7735\text{ V}}}$$
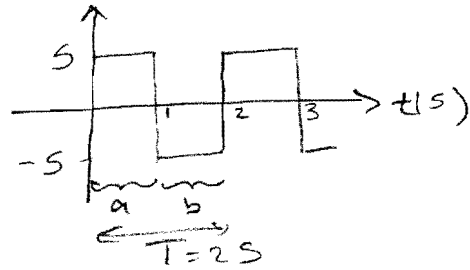
## Solution 11.24

$$T=2, \quad v(t) = \begin{cases} 5, & 0 < t < 1 \\ -5, & 1 < t < 2 \end{cases}$$



$$V_{\text{rms}}^2 = \frac{1}{2} \left[ \underbrace{\int_0^1 5^2 dt}_a + \underbrace{\int_1^2 (-5)^2 dt}_b \right] = \frac{25}{2} [1+1] = 25$$

$$\boxed{V_{\text{rms}} = 5\text{V}}$$

By definition  $V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$


$$\therefore V_{\text{rms}}^2 = \frac{1}{T} \int_0^T v^2(t) dt = \frac{1}{2} \int_0^{T/2} \underbrace{v^2(t)}_{=5^2} dt + \frac{1}{2} \int_{T/2}^T \underbrace{v^2(t)}_{=(-5)^2} dt$$


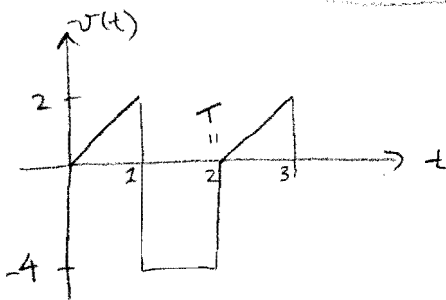
## Solution 11.31

$$V_{rms}^2 = \frac{1}{2} \int_0^2 v(t) dt = \frac{1}{2} \left[ \int_0^1 (2t)^2 dt + \int_1^2 (-4)^2 dt \right] = \frac{1}{2} \left[ \frac{4}{3} + 16 \right] = 8.6667 \text{ V}^2$$

$$V_{rms} = \underline{2.944 \text{ V}}$$




By definition,

$$V_{rms}^2 = \frac{1}{T} \int_0^T v^2(t) dt$$

$$= \frac{1}{T} \int_0^{T/2} \underbrace{v^2(t)}_{(2t)^2} dt + \frac{1}{T} \int_{T/2}^T \underbrace{v^2(t)}_{(-4)^2} dt$$

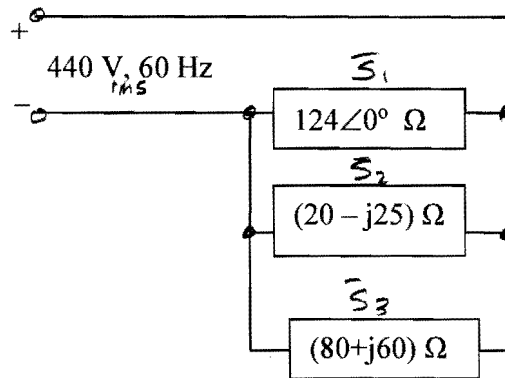**Solution 11.38**

For the power system in Fig. 11.67, find: (a) the average power, (b) the reactive power, (c) the power factor. Note that 440 V is an rms value.



In general

$$\bar{S} = \frac{1}{2} \bar{V} \cdot \bar{I}^* = \frac{\bar{V}}{\sqrt{2}} \cdot \frac{\bar{V}^*}{\sqrt{2} \bar{Z}^*}$$

$$= \frac{\bar{V}_{rms} \cdot \bar{V}_{rms}^*}{\bar{Z}^*} = \frac{|\bar{V}_{rms}|^2}{\bar{Z}^*} = \frac{V_{rms}^2}{\bar{Z}^*}$$

$$\therefore \bar{S} = \frac{V_{rms}^2}{\bar{Z}^*}$$

Figure 11.67  
For Prob. 11.38.

**Solution**

$$S_1 = V^2 / (Z_1)^* = 1.56129 \text{ kW.} \quad \left( = \frac{(440 V_{rms})^2}{124} \right)$$

$$S_2 = V^2 / (Z_2)^* = 193,600 / (32.0156 \angle 51.34^\circ) = 6,047.05 \angle -51.34^\circ \text{ VA}$$

$$= 3.7776 \text{ kW} - j4.7219 \text{ kVAR}$$

$$S_3 = V^2 / (Z_3)^* = 193,600 / (100 \angle -36.87^\circ) = 1,936 \angle 36.87^\circ \text{ VA}$$

$$= 1.5488 \text{ kW} + j1.1616 \text{ kVAR.}$$

$$S = S_1 + S_2 + S_3 = (1.56129 + 3.7776 + 1.5488) \text{ kW} + j(0 - 4.7219 + 1.1616) \text{ kVAR}$$


$$= 6.888 \text{ kW} - j3.56 \text{ kVAR.}$$

Therefore,

(a)  $P = \text{Re}(S) = 6.888 \text{ kW}$

(b)  $Q = \text{Im}(S) = -3.56 \text{ kVAR (leading)}$

(c)  $\text{pf} = \cos [\tan^{-1}([-3.56/6.888)]], \cos \{ \tan^{-1}[-0.51684] \}$   
 $= \cos(-27.332^\circ) = 0.89$

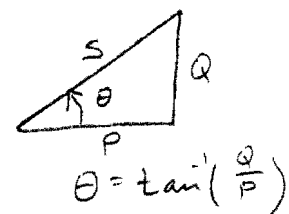


**Solution 11.41**

$$\bar{z}_1$$

$$(a) -j2 \parallel (j5 - j2) = -j2 \parallel -j3 = \frac{(-j2)(-j3)}{j} = -j6$$

$$\mathbf{Z}_T = 4 - j6 = 7.211 \angle -56.31^\circ$$

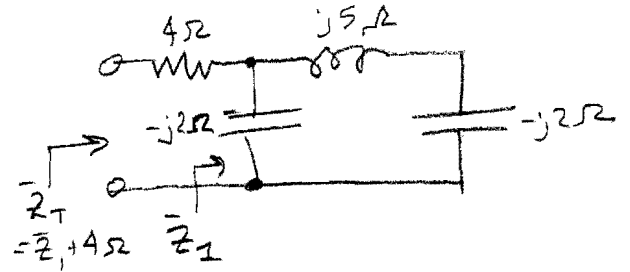
$$\text{pf} = \cos(-56.31^\circ) = 0.5547 \quad (\text{leading})$$



In general,  $\bar{Z} = \frac{\bar{V}}{\bar{I}} = \frac{|\bar{V}|}{|\bar{I}|} \angle (\theta_V - \theta_I)$

$$\therefore \angle \bar{Z}_T = \angle \text{pf.}$$

$$\therefore \text{pf} = \cos(\angle \bar{Z}_T)$$

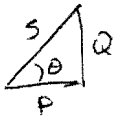**Solution 11.42**

(a)  $S = 120 \text{ VA}$  (lagging)  $pf = 0.707 = \cos \theta \rightarrow \theta = 45^\circ$

$$\bar{S} = \underbrace{S \cos \theta}_P + j \underbrace{S \sin \theta}_Q = \underline{84.84 + j84.84 \text{ VA}}$$


(b)  $S = V_{rms} I_{rms} \rightarrow I_{rms} = \frac{S}{V_{rms}} = \frac{120}{110} = \underline{1.091 \text{ A rms}}$

(c)  $\bar{S} = I_{rms}^2 \bar{Z} \rightarrow \bar{Z} = \frac{\bar{S}}{I_{rms}^2} = \underline{71.278 + j71.278 \Omega}$

(d) If  $\bar{Z} = R + j\omega L$ , then  $R = \underline{71.278 \Omega}$

$$\omega L = 2\pi fL = 71.278 \rightarrow L = \frac{71.278}{2\pi \times 60} = \underline{0.1891 \text{ H} = 189.1 \text{ mH}}$$


↑  
60 Hz

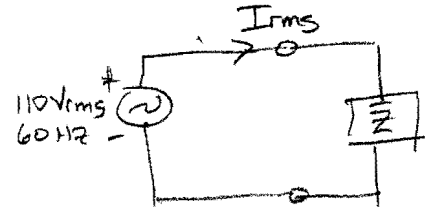

## Solution 11.46

$$(a) \quad \mathbf{S} = \mathbf{VI}^* = \overbrace{(220 \angle 30^\circ)}^{\mathbf{V}_{rms}} \overbrace{(0.5 \angle -60^\circ)}^{\mathbf{I}_{rms}^*} = \underline{110 \angle -30^\circ}$$

$$- \quad \mathbf{S} = \underbrace{[95.26]}_P - \underbrace{j55}_Q \text{ VA} \quad |\mathbf{S}| = S$$

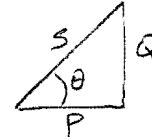

- Apparent power = **110 VA** =  $|\mathbf{S}|$
- Real power = **95.26 W**
- Reactive power = **55 VAR**
- pf is **leading** because current leads voltage

$$(b) \quad \mathbf{S} = \mathbf{VI}^* = \overbrace{(250 \angle -10^\circ)}^{\mathbf{V}_{rms}} \overbrace{(6.2 \angle 25^\circ)}^{\mathbf{I}_{rms}^*} = \underline{1550 \angle 15^\circ}$$

$$- \quad \mathbf{S} = \underbrace{[1497.2]}_P + \underbrace{j401.2}_Q \text{ VA} \quad |\mathbf{S}| = S$$

- Apparent power = **1550 VA** =  $|\mathbf{S}|$
- Real power = **1497.2 W**
- Reactive power = **401.2 VAR**
- pf is **lagging** because current lags voltage