

**Solution 12.5** positive abc phase sequence. From Table 12.1:

$$V_{AB} = 1.7321 \times V_{AN} \angle +30^\circ = 207.8 \angle (32^\circ + 30^\circ) = 207.8 \angle 62^\circ \text{ V or}$$

$$\bar{V}_{AB} = 207.8 \cos(\omega t + 62^\circ) \text{ V}$$


which also leads to,

$$\bar{V}_{BC} = 207.8 \cos(\omega t - 58^\circ) \text{ V}$$

and

$$\bar{V}_{CA} = 207.8 \cos(\omega t + 182^\circ) \text{ V}$$
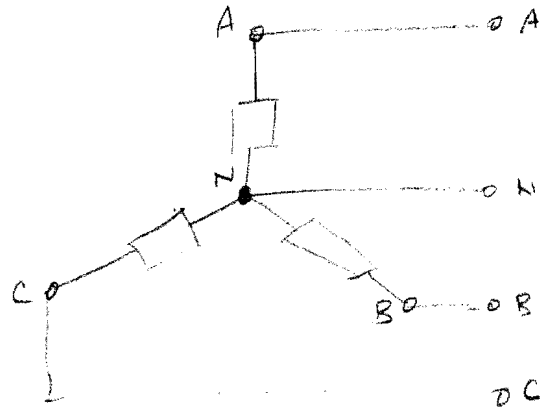
$$207.8 \cos(\omega t + 62^\circ) \text{ V}, 207.8 \cos(\omega t - 58^\circ) \text{ V}, 207.8 \cos(\omega t + 182^\circ) \text{ V}$$





## Solution 12.8

In a balanced three-phase wye-wye system, the source is an acb-sequence of voltages and  $V_{cn} = 120\angle 35^\circ$  V rms. The line impedance per phase is  $(1+j2)\Omega$ , while the per phase impedance of the load is  $(11+j14)\Omega$ . Calculate the line currents and the load voltages.

**Solution** Refer to Fig. 12.10 for the Y-Y connection. Can analyze each phase separately.

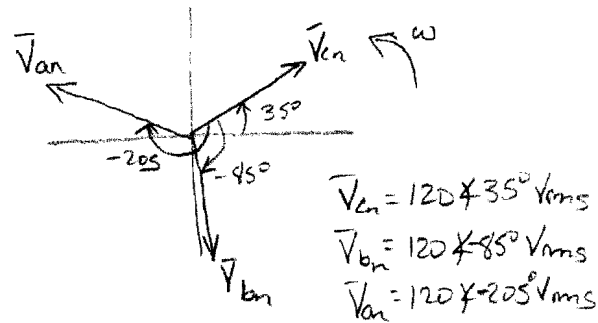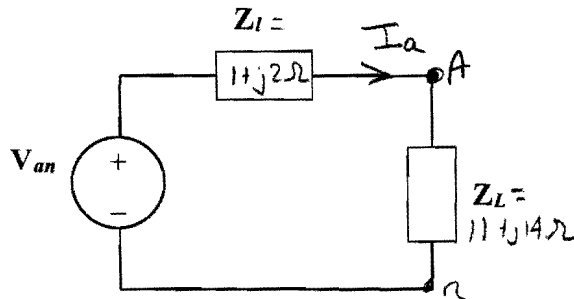Consider the per phase equivalent circuit shown below.



Since the sequence is acb and  $V_{cn} = 120\angle 35^\circ$  V<sub>rms</sub>, then  $V_{an} = 120\angle 155^\circ$  V<sub>rms</sub> and  $V_{bn} = 120\angle -85^\circ$  V<sub>rms</sub>

$$I_a = V_{an} / (Z_l + Z_L) = (120\angle 155^\circ) / (12 + j16) = (120\angle 155^\circ) / (20\angle 53.13^\circ)$$

$$= 6\angle 101.87^\circ \text{ amps. } A_{rms}$$

$$I_b = I_a \angle 120^\circ = 6\angle 221.87^\circ \text{ amps. } A_{rms}$$

$$I_c = I_a \angle -120^\circ = 6\angle -18.13^\circ \text{ amps. } A_{rms}$$

acb sequence

$$V_{an} = I_a Z_L = (6\angle 101.87^\circ)(11 + j14) = (6\angle 101.87^\circ)(17.8045\angle 51.843^\circ)$$

$$= 106.83\angle 153.71^\circ \text{ volts. } V_{rms}$$

$$V_{bn} = V_{an} \angle 120^\circ = 106.83\angle -86.29^\circ \text{ volts. } V_{rms}$$

$$V_{cn} = V_{an} \angle -120^\circ = 106.83\angle 33.71^\circ \text{ volts. } V_{rms}$$

acb sequence

## Solution 12.9

Refer to Fig. 12.10 for the Y-Y connection. Can analyze each phase separately.

$$\bar{I}_a = \frac{\bar{V}_{an}}{\bar{Z}_L + \bar{Z}_Y} = \frac{120 \angle 0^\circ}{20 + j15} = 4.8 \angle -36.87^\circ \text{ Arms}$$

$$\bar{I}_b = \bar{I}_a \angle -120^\circ = 4.8 \angle -156.87^\circ \text{ Arms}$$


$$\bar{I}_c = \bar{I}_a \angle 120^\circ = 4.8 \angle 83.13^\circ \text{ Arms}$$

As a balanced system,  $\bar{I}_n = 0 \text{ A}$

With  $\bar{V}_{an} = 120 \angle 0^\circ \text{ Vrms}$   
 $\bar{V}_{bn} = 120 \angle -120^\circ \text{ Vrms}$   
 $\bar{V}_{cn} = 120 \angle 120^\circ \text{ Vrms}$

We recognize a positive abc sequencing.

For phase a:

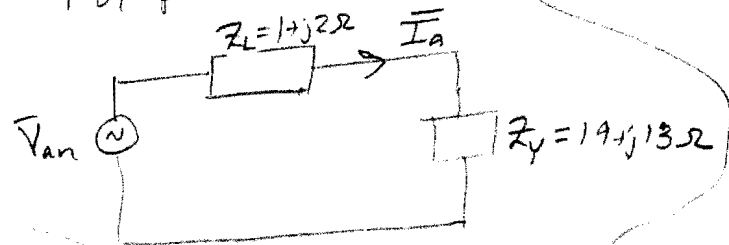

To check:  $\bar{I}_a + \bar{I}_b + \bar{I}_c = 4.8 \angle -36.87^\circ + 4.8 \angle -156.87^\circ + 4.8 \angle 83.13^\circ = 0 \text{ A}$

Problem 4.4**Problem**

Solve for the line currents in the Y- $\Delta$  circuit of Fig. 12.45. Take  $Z_{\Delta} = 60\angle 45^{\circ}\Omega$ .

recognize a positive abc phase sequencing:


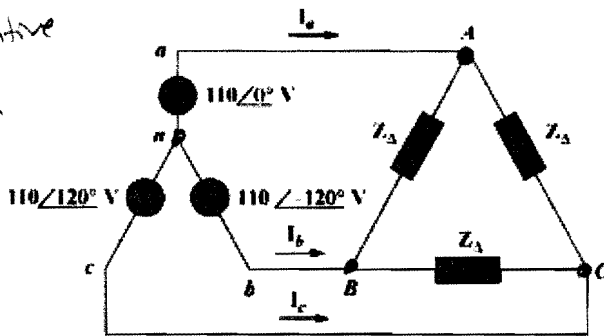


Figure 12.45

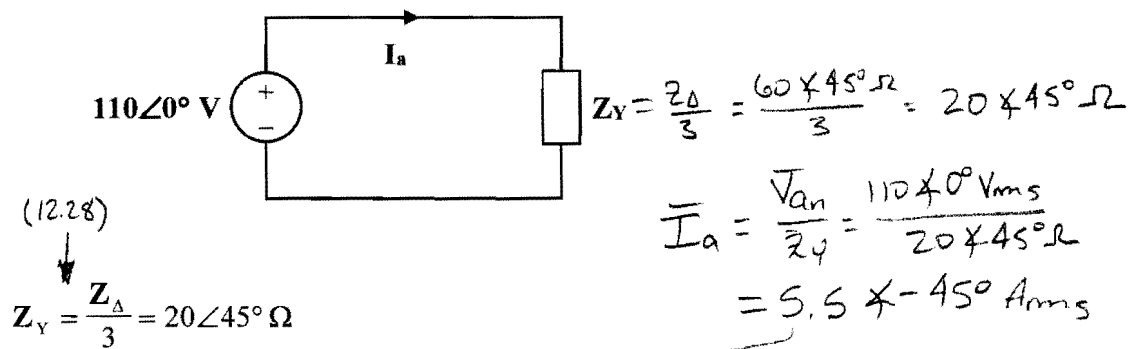**Solution**

Convert the delta-load to a wye-load and apply per-phase analysis.



(12.28)

$$Z_Y = \frac{Z_{\Delta}}{3} = 20\angle 45^{\circ}\Omega$$


$$I_a = \frac{110\angle 0^{\circ}}{20\angle 45^{\circ}} = 5.5\angle -45^{\circ} A_{rms}$$

$$I_b = I_a\angle -120^{\circ} = 5.5\angle -165^{\circ} A_{rms}$$

$$I_c = I_a\angle 120^{\circ} = 5.5\angle 75^{\circ} A_{rms}$$
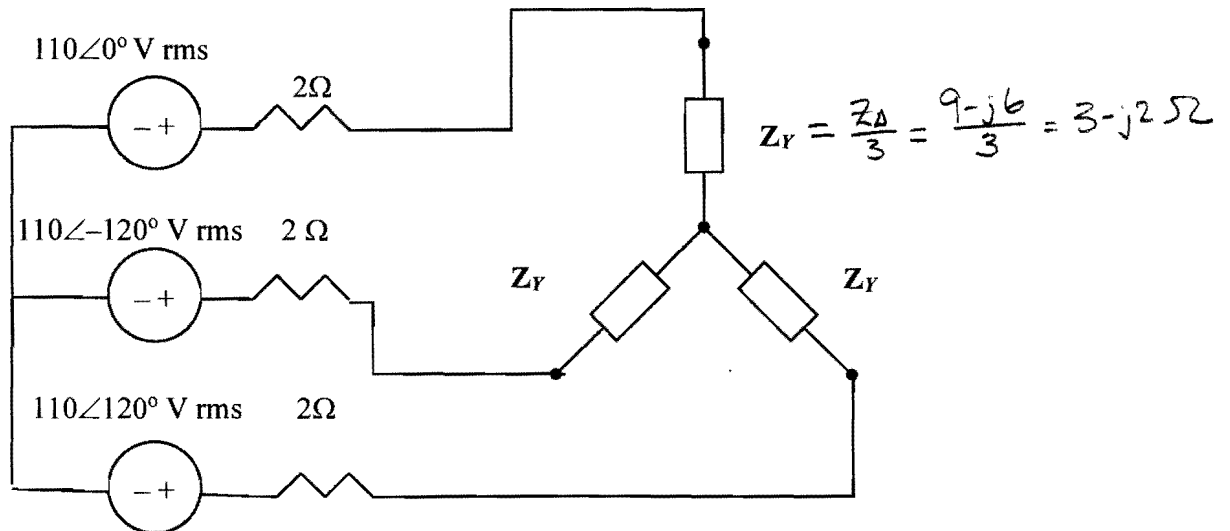
## Solution 12.13


Convert the delta load to wye as shown below.



eqn (12.28):

$$Z_Y = \frac{1}{3} Z_{\Delta} = 3 - j2 \Omega$$

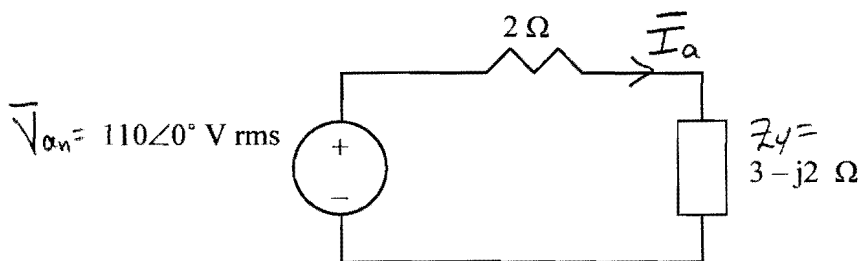We consider the single phase equivalent shown below.



$$\begin{aligned} \bar{I}_a &= \frac{\bar{V}_{an}}{2 + Z_Y} = \frac{110 \angle 0^\circ}{2 + 3 - j2} \\ &= 20.43 \angle 21.8^\circ \text{ Arms} \end{aligned}$$

$$\bar{I}_a = 110 / (2 + 3 - j2) = 20.43 \angle 21.8^\circ \text{ Arms}$$

$$I_L = |\bar{I}_a| = 20.43 \text{ Arms} \leftarrow \text{same for every phase.}$$

$$\begin{aligned} \bar{S} &= \bar{V} \bar{I}^* \\ &= \bar{I} \cdot \bar{Z}_Y \cdot \bar{I}^* \\ &= |\bar{I}|^2 \cdot \bar{Z}_Y \end{aligned}$$

$$S = 3 |\bar{I}_a|^2 Z_Y = 3 (20.43)^2 (3 - j2) = 4514 \angle -33.96^\circ = \overset{3756}{3744} - j2504 \text{ VA}$$

$$P = \text{Re}(S) = 3.744 \text{ kW}$$

all 3 phases

**Solution 12.19**

For the  $\Delta$ - $\Delta$  circuit of Fig. 12.50, calculate the phase and line currents.

See that there is abc positive phase sequencing.

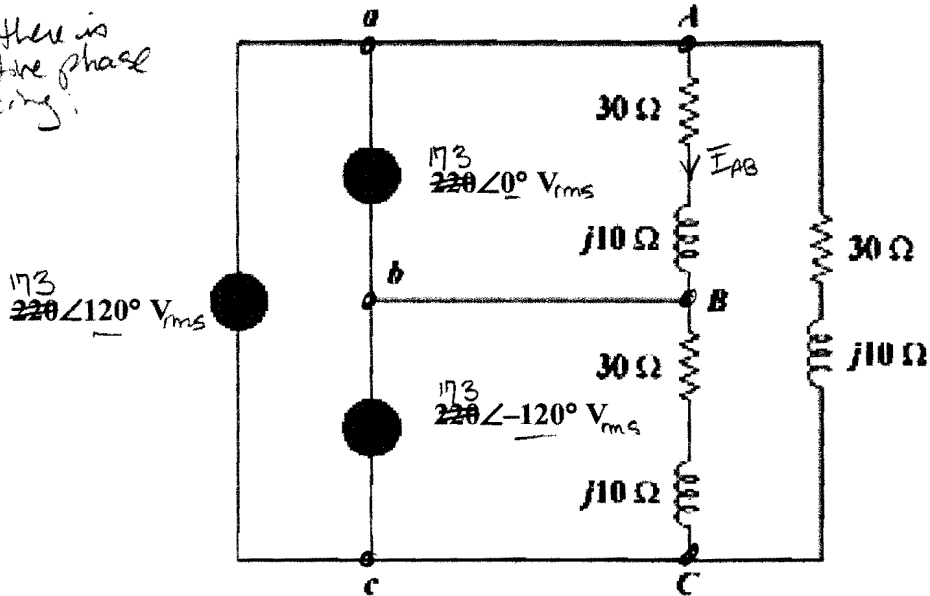


Figure 12.50  
For Prob. 12.19.

**Solution**

$$Z_{\Delta} = 30 + j10 = 31.62 \angle 18.43^{\circ} \Omega$$

From directly observe this circuit we see that The phase currents are

$$I_{AB} = \frac{V_{ab}}{Z_{\Delta}} = \frac{173 \angle 0^{\circ}}{31.62 \angle 18.43^{\circ}} = 5.471 \angle -18.43^{\circ} \text{ A}_{rms}$$

$$I_{BC} = I_{AB} \angle -120^{\circ} = 5.471 \angle -138.43^{\circ} \text{ A}_{rms}$$

$$I_{CA} = I_{AB} \angle 120^{\circ} = 5.471 \angle 101.57^{\circ} \text{ A}_{rms}$$

The line currents are

From Table 12.1  $I_a = I_{AB} \sqrt{3} \angle -30^{\circ}$

$$I_a = I_{AB} \sqrt{3} \angle -30^{\circ} = 9.476 \angle -48.43^{\circ} \text{ A}$$

$$I_b = I_a \angle -120^{\circ} = 9.476 \angle -168.43^{\circ} \text{ A}$$

$$I_c = I_a \angle 120^{\circ} = 9.476 \angle 71.57^{\circ} \text{ A}$$

## Solution 12.21

Three 440-volt generators, form a delta connected source which is connected to a balanced delta connected load of  $Z_L = (8.66 + j5) \Omega$  per phase as shown in Fig. 12.52. Determine the value of  $I_{BC}$  and  $I_{aA}$ . What is the pf of the load?

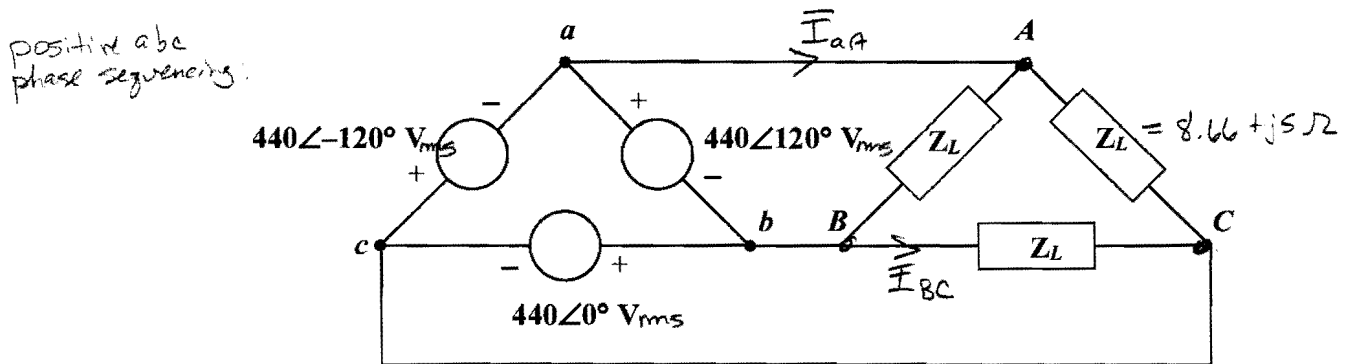


Figure 12.52  
For Prob. 12.21.

**Solution** Directly from the circuit we observe that  $\underline{I}_{BC} = \frac{\underline{V}_{BC}}{Z_L} = \frac{\underline{V}_{bc}}{Z_L}$  :


$$\underline{I}_{BC} = \underline{V}_{BC}/Z_L = 440/(10\angle 30^\circ) = 44\angle -30^\circ \text{ Arms.}$$

$$\underline{I}_{aA} = \underline{I}_{aC} + \underline{I}_{aB} = [440\angle 60^\circ/(10\angle 30^\circ)] + [440\angle 120^\circ/(10\angle 30^\circ)] \\ = [44\angle 30^\circ] + [44\angle 90^\circ] = 38.105 + j22 + j44 = 38.105 + j66 = 76.21\angle 60^\circ \text{ A.}$$

$$\text{pf} = 8.66/10 = 0.866.$$

$$\underline{I}_{cA} = 44\angle -150^\circ \text{ Arms}$$
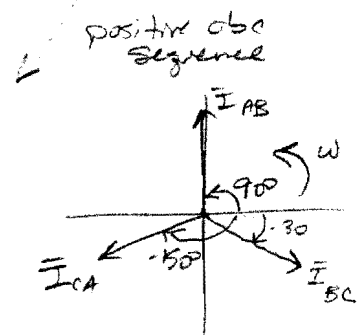
$$\underline{I}_{aB} = 44\angle -270^\circ \text{ Arms}$$



From Table 12.1

$$\underline{I}_a = \underline{I}_{AB} \sqrt{3} \angle -30^\circ = 44 \cdot \sqrt{3} \angle (-270^\circ - 30^\circ)$$

$$\underline{I}_a = 76.21 \angle -30^\circ = 76.21 \angle 60^\circ \text{ Arms}$$

$$\underline{S} = \underline{V} \cdot \underline{I} = 3 \cdot \underline{V}_{BC} \cdot \underline{I}_{BC}^* = 3 (440\angle 0^\circ) (44\angle +30^\circ) = 150,896 + j87,120$$

$$\underline{\text{Pf}} = \cos \theta = \frac{P}{S} = \frac{150,896}{174,235} = 0.866$$

**Solution 12.25**

positive abc sequencing.  $\Delta$ -Y connection.  
Convert to a Y-Y connection using

Convert the delta-connected source to an equivalent wye-connected source and consider the single-phase equivalent. Or, from Table 12.1  $E_a = \frac{\bar{V}_p \angle -30^\circ}{\sqrt{3} Z_Y}$


$$I_a = \frac{440 \angle (10^\circ - 30^\circ)}{\sqrt{3} Z_Y}$$

where  $Z_Y = 3 + j2 + 10 - j8 = 13 - j6 = 14.318 \angle -24.78^\circ \Omega$

$$I_a = \frac{440 \angle -20^\circ}{\sqrt{3} (14.318 \angle -24.78^\circ)} = 17.742 \angle 4.78^\circ \text{ Amps}$$

$$I_b = I_a \angle -120^\circ = 17.742 \angle -115.22^\circ \text{ Amps}$$

$$I_c = I_a \angle +120^\circ = 17.742 \angle 124.78^\circ \text{ Amps}$$

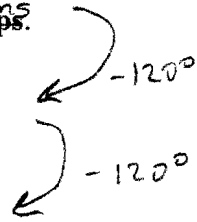



**Solution 12.27** See Fig. 12.18 for the circuit.  $\bar{V}_{ab} = 208 \angle 0^\circ \text{ V}_{rms}$

Since  $\bar{Z}_L$  and  $\bar{Z}_Y$  are in series, we can lump them together so that  $\bar{Z}_Y = \bar{Z}_L + \bar{Z}_R$  or

$$\bar{Z}_Y = (2 + j) + (6 + j4) = 8 + j5 \Omega$$

$$\Rightarrow \bar{I}_a = \frac{V_p \angle -30^\circ}{\sqrt{3} \bar{Z}_Y} = \frac{208 \angle -30^\circ}{\sqrt{3}(8 + j5)} = 12.729 \angle -62.01^\circ \text{ A}_{rms}$$

$$\bar{V}_L = (6 + j4)\bar{I}_a = \frac{208(0.866 - j0.5)(6 + j4)}{\sqrt{3}(8 + j5)} = 80.81 - j43.54 = 91.79 \angle -28.32^\circ \text{ V}_{rms}$$


$$\bar{V}_L = \bar{I}_a \cdot \bar{Z}_R$$

( $= \bar{V}_{AN}$ )

$$\underline{\underline{|V_L| = 91.79 \text{ V}}}$$

From Table 12.1,  $\bar{I}_a = \frac{V_p \angle -30^\circ}{\sqrt{3} \bar{Z}_Y}$

$V_p$  in this case is the source voltage  $\bar{V}_{ab} = V_p \angle 0^\circ$ .

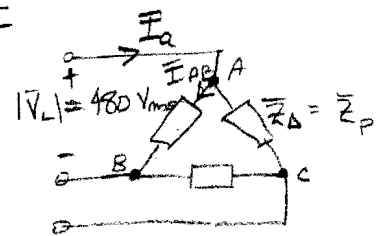


**Solution 12.31**

A balanced delta-connected load is supplied by a 60-Hz three-phase source with a line voltage of 480V. Each load phase draws 24 kW at a lagging power factor of 0.8. Find:

- (a) the load impedance per phase
- (b) the line current magnitude
- (c) the value of capacitance needed to be connected in parallel with each load phase to minimize the current from the source.

**Solution**

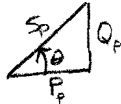

(a) per phase:

$$P_p = 24,000, \quad \cos \theta = 0.8, \Rightarrow S_p = \frac{P_p}{\cos \theta} = 24 / 0.8 = 30 \text{ kVA} \quad \text{and } \theta = 36.87^\circ$$

$$Q_p = S_p \sin \theta = 18 \text{ kVAR}$$

$$S = 3S_p = 3(24 + j18) = 72 + j54 \text{ kVA} = 90 \angle 36.87^\circ \text{ kVA}$$

For delta-connected load,  $V_p = V_L = 480 \text{ V}_{rms}$ . But  $S = 3S_p = 3V_p \cdot I_p^* = 3V_p \cdot \frac{V_p^*}{Z_p^*} = \frac{3V_p^2}{Z_p^*}$

$$\bar{S} = \frac{3V_p^2}{\bar{Z}_p^*} \rightarrow \bar{Z}_p^* = \frac{3V_p^2}{\bar{S}} = \frac{3(480)^2}{(72 + j54) \times 10^3}, \quad \bar{Z}_p = [6.144 + j4.608] \Omega = \bar{Z}_\Delta$$

eqn (12.50):

$$(b) \quad P_p = \frac{\sqrt{3} V_L I_L \cos \theta}{3} \rightarrow I_L = \frac{3 \cdot 24,000}{\sqrt{3} \times 480 \times 0.8} = 108.24 \text{ A}_{rms}$$

(c) We find C to bring the power factor to unity

$$Q_c = Q_p = 18 \text{ kVA} \rightarrow C = \frac{Q_c}{\omega V_{rms}^2} = \frac{18,000}{2\pi \times 60 \times 480^2} = 207.2 \mu\text{F}$$

check

$$\bar{I}_{AB} = \frac{V_{AB}}{\bar{Z}_\Delta}$$

From Table 12.1,  $\bar{I}_a = \bar{I}_{AB} \sqrt{3} \angle 30^\circ \Rightarrow |\bar{I}_a| = \sqrt{3} |\bar{I}_{AB}| = \sqrt{3} \left| \frac{480}{\bar{Z}_p} \right|$

$$= \sqrt{3} \cdot \frac{480}{|6.144 + j4.608|}$$

$$= 108.25 \text{ A}_{rms}$$

**Solution 12.49**

Each phase load consists of a 20-ohm resistor and a 10-ohm inductive reactance. With a line voltage of 480 V rms, calculate the average power taken by the load if:

- the three phase loads are delta-connected,
- the loads are wye-connected.

**Solution**

- (a) For the delta-connected load,  $Z_p = 20 + j10\Omega$ ,  $V_p = V_L = 480 \text{ V(rms)}$ ,

$$\bar{S} = \frac{3V_p^2}{Z_p^*} = \frac{3 \times 480^2}{(20 - j10)} = \frac{(13,824 + j6,912)k}{500} = \underbrace{(27.648)}_{=P} + \underbrace{j13.824}_{=Q} \text{ kVA}$$

$$P = 27.65 \text{ kW}$$

- (b) For the wye-connected load,  $Z_p = 20 + j10\Omega$ ,  $V_p = V_L / \sqrt{3}$ , ← See Table 12.1 or (12.12)

$$\bar{S} = \frac{3V_p^2}{Z_p^*} = \frac{3 \times 480^2}{3(20 - j10)} = \underbrace{(9.216)}_{=P} + \underbrace{j4.608}_{=Q} \text{ kVA}$$

$$P = 9.216 \text{ kW}$$