

## EE 221 – *Circuits II*

### Homework #7

10 points

*Date Assigned:* 9/29

*Date Due:* 10/6

- 7.1 Text problem 14.16.
- 7.2 Text problem 14.22.
- 7.3 Text problem 14.23.
- 7.4 Text problem 14.29.
- 7.5 Text problem 14.30.
- 7.6 Text problem 14.36.
- 7.7 Text problem 14.40
- 7.8 Text problem 14.39. This is neither a series nor a parallel RLC circuit. It is the “infamous”  $RL||C$  circuit.
- 7.9 Text problem 14.47.
- 7.10 Text problem 14.50.
- 7.11 Text problem 14.53.