

$$H(s) = \frac{1.6}{s(s^2 + s + 16)}, \quad s = j\omega$$


**Solution 14.16** Factor out 16 and express in standard form:

$$H(\omega) = \frac{\frac{1.6}{16}}{j\omega \left[ 1 + j\omega + \left(\frac{j\omega}{4}\right)^2 \right]} = \frac{0.1}{j\omega \left[ 1 + j\omega + \left(\frac{j\omega}{4}\right)^2 \right]}$$

$$H_{db} = 20 \log_{10}|0.1| - 20 \log_{10}|j\omega| - 20 \log_{10} \left| 1 + j\omega + \left(\frac{j\omega}{4}\right)^2 \right|$$

*ignore*

The magnitude and phase plots are shown below.

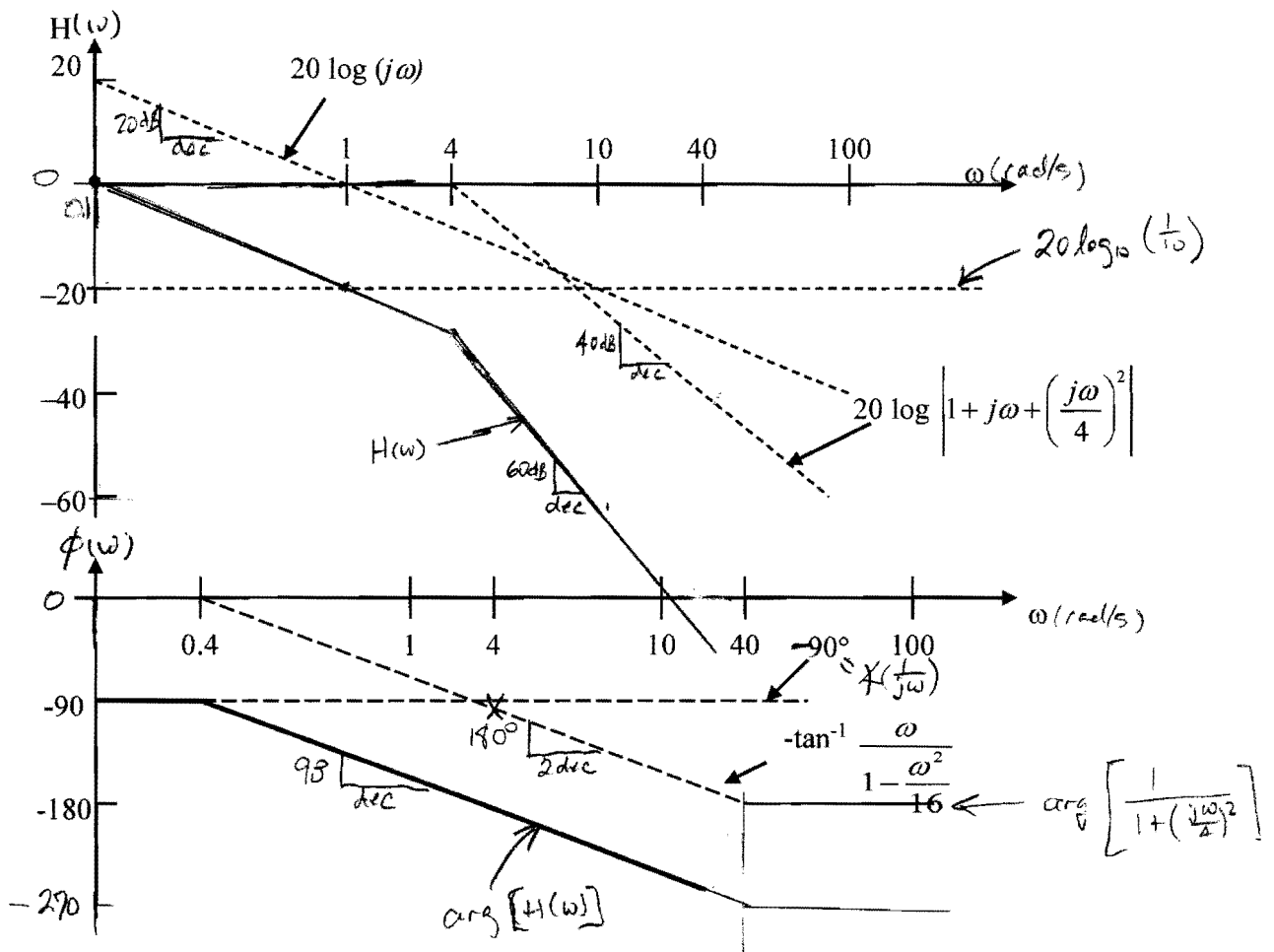

**Solution 14.22**

Find the transfer function  $\mathbf{H}(\omega)$  with the Bode magnitude plot shown in Fig. 14.74.

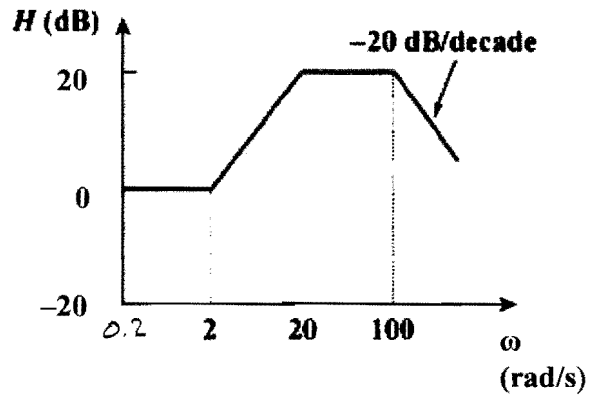


Figure 14.74  
For Prob. 14.22.

**Solution**

$$0 = 20 \log_{10} k \longrightarrow k = 1$$

$$\text{A zero of slope } +20 \text{ dB/dec at } \omega = 2 \longrightarrow 1 + j\omega/2$$

$$\text{A pole of slope } -20 \text{ dB/dec at } \omega = 20 \longrightarrow \frac{1}{1 + j\omega/20}$$

$$\text{A pole of slope } -20 \text{ dB/dec at } \omega = 100 \longrightarrow \frac{1}{1 + j\omega/100}$$

Hence,

$$\mathbf{H}(\omega) = \frac{\pm 1(1 + j\omega/2)}{(1 + j\omega/20)(1 + j\omega/100)} = \frac{\pm 1,000(2 + j\omega)}{(20 + j\omega)(100 + j\omega)}$$

**Solution 14.23**

The Bode magnitude plot of  $H(\omega)$  is shown in Fig. 14.75. Find  $H(\omega)$ .

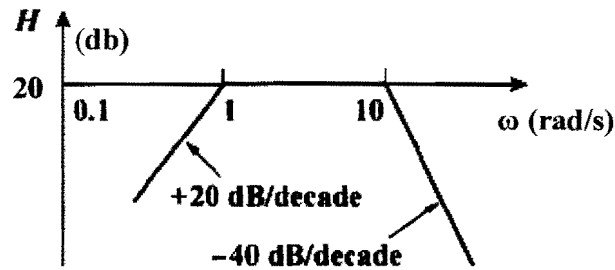


Figure 14.75  
For Prob. 14.23.

**Solution**

The initial slope indicates we have  $j\omega$  in the numerator. Our approach to plotting requires the plot of  $j\omega$  to cross 0db at  $\omega = 1$  rad/s. Since it crosses at 20db, that indicates that the overall gain is 20db or,

$$20 = 20 \log_{10} |\text{gain}| \stackrel{=K}{=} \text{the gain has to be } 10. = K$$

A zero of slope +20 dB/dec at the origin  $\longrightarrow j\omega$

A pole of slope -20 dB/dec at  $\omega = 1$   $\longrightarrow \frac{1}{1 + j\omega/1}$


A pole of slope -40 dB/dec at  $\omega = 10$   $\longrightarrow \frac{1}{(1 + j\omega/10)^2}$

Hence,

$$H(\omega) = \frac{\pm 10j\omega}{(1 + j\omega)(1 + j\omega/10)^2}$$


$$H(\omega) = \frac{\pm 1,000j\omega}{(1 + j\omega)(10 + j\omega)^2}$$

(It should be noted that this function could also have a minus sign out in front and still be correct. The magnitude plot does not contain this information. It can only be obtained from the phase plot.)

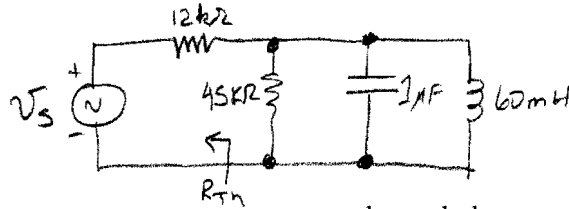**Solution 14.29**

We convert the voltage source to a current source as shown below.

Parallel RLC network

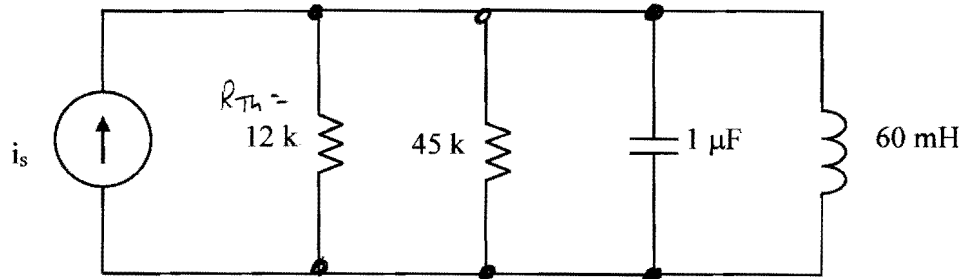

not needed

$$i_s = \frac{20}{12} \cos \omega t, \quad R_{\text{eff}} = 12 // 45 = \frac{12 \times 45}{57} = 9.4737 \text{ k}\Omega$$

$$(14.44): \quad \omega_o = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{60 \times 10^{-3} \times 1 \times 10^{-6}}} = 4.082 \text{ krad/s} = 4.082 \text{ krad/s} \Rightarrow f_o = 649.7 \text{ Hz}$$

$$(14.46): \quad B = \frac{1}{R_{\text{eff}} C} = \frac{1}{9.4737 \times 10^3 \times 10^{-6}} = 105.55 \text{ rad/s} = 105.55 \text{ rad/s} \quad \Delta f = 16.80 \text{ Hz}$$

$$(14.47): \quad Q = \frac{\omega_o}{B} = \frac{4082}{105.55} = 38.674 = 38.67$$

**4.082 krad/s, 105.55 rad/s, 38.67**

**Solution 14.30**

(a)  $f_0 = 15,000$  Hz leads to  $\omega_0 = 2\pi f_0 = 94.25$  krad/s =  $1/(LC)^{0.5}$  or

$LC = 1/8.883 \times 10^9$  or  $C = 1/(8.883 \times 10^9 \times 10^{-2}) = 11.257 \times 10^{-9}$  F = 11.257 nF

$$f_0 = \frac{1}{2\pi\sqrt{LC}} \Rightarrow f_0^2 = \frac{1}{4\pi^2 LC}$$

$$C = \frac{1}{4\pi^2 f_0^2 L}$$


$$C = [4\pi^2 (15 \times 10^3)^2 \cdot 10 \times 10^{-3}]^{-1}$$


$$C = 11.257 \text{ nF}$$

(b) since the capacitive reactance cancels out the inductive reactance at resonance, the current through the series circuit is given by

$$|\bar{I}| = 120/20 = 6 \text{ A}_{\text{rms}}$$

(14.38): (c)  $Q = \omega_0 L/R = 94.25 \times 10^3 (0.01)/20 = 47.12$ .

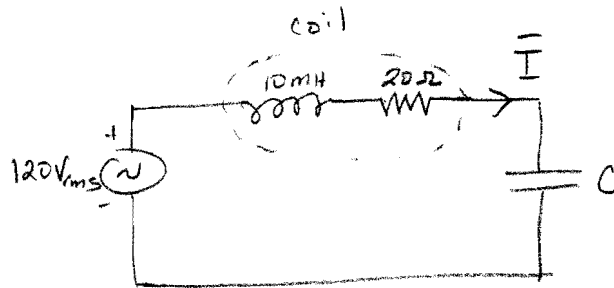

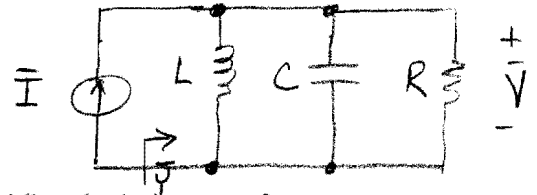**Solution 14.36**

It is expected that a parallel  $RLC$  resonant circuit has a midband admittance of  $25 \times 10^{-3} \text{ S}$ , quality factor of 120, and a resonant frequency of 200 krad/s. Calculate the values of  $R$ ,  $L$ , and  $C$ . Find the bandwidth and the half-power frequencies.

**Solution**

At resonance,  $Z_L \parallel Z_C \rightarrow \infty \Rightarrow \bar{Y} = \frac{1}{R}$

$$Y = \frac{1}{R} \longrightarrow R = \frac{1}{Y} = \frac{1}{25 \times 10^{-3}} = 40 \Omega$$


$$(14.47): Q = \omega_0 RC \longrightarrow C = \frac{Q}{\omega_0 R} = \frac{120}{(200 \times 10^3)(40)} = 15 \mu\text{F}$$


$$\omega_0 = \frac{1}{\sqrt{LC}} \longrightarrow L = \frac{1}{\omega_0^2 C} = \frac{1}{(4 \times 10^{10})(15 \times 10^{-6})} = 1.6667 \mu\text{H}$$

$$B = \frac{\omega_0}{Q} = \frac{200 \times 10^3}{120} = 1.6667 \text{ krad/s} \quad (\Delta f = \frac{f_0}{Q} = \frac{31,831}{120} = 265.3 \text{ Hz})$$

$$\omega_1 \approx \omega_0 - \frac{B}{2} = 200 - 0.8333 = 199.167 \text{ krad/s} \quad (f_1 \approx f_0 - \frac{\Delta f}{2} = 31,698.4 \text{ Hz})$$
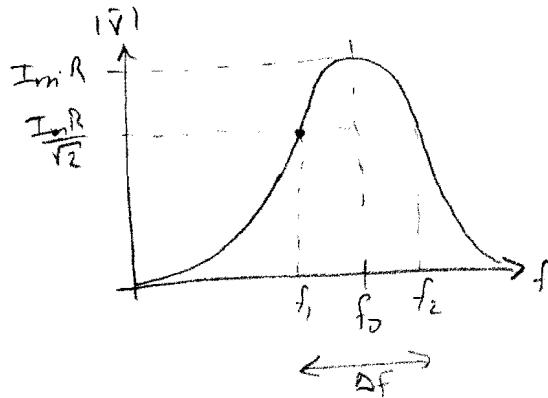
$$\omega_2 \approx \omega_0 + \frac{B}{2} = 200 + 0.8333 = 200.833 \text{ krad/s} \quad (f_2 \approx f_0 + \frac{\Delta f}{2} = 31,963.7 \text{ Hz})$$



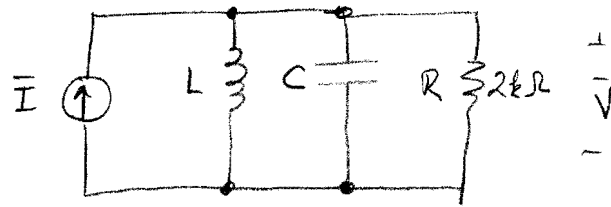

## Solution 14.40

$$(a) \quad B = \omega_2 - \omega_1 = 2\pi \overset{= \Delta f}{(f_2 - f_1)} = 2\pi(90 - 86) \times 10^3 = 8\pi \text{krad/s}$$

$$\omega_0 \approx \frac{1}{2}(\omega_1 + \omega_2) = 2\pi(88) \times 10^3 = 176\pi \times 10^3$$


$$(14.46): \quad \Delta\omega = B = \frac{1}{RC} \longrightarrow C = \frac{1}{BR} = \frac{1}{8\pi \times 10^3 \times 2 \times 10^3} = \underline{19.89 \text{nF}}$$

$$(14.44): (b) \quad \omega_0 = \frac{1}{\sqrt{LC}} \longrightarrow L = \frac{1}{\omega_0^2 C} = \frac{1}{(176\pi \times 10^3)^2 \times 19.89 \times 10^{-9}} = \underline{164.45 \mu\text{H}}$$

$$(c) \quad \omega_0 = 176\pi = \underline{552.9 \text{krad/s}} \Rightarrow f_0 = 88 \text{kHz} \quad \text{check, } \frac{1}{2\pi\sqrt{LC}} = 88 \text{kHz} \checkmark$$

$$(d) \quad B = 8\pi = \underline{25.13 \text{krad/s}} \leftarrow \text{from (a)}$$
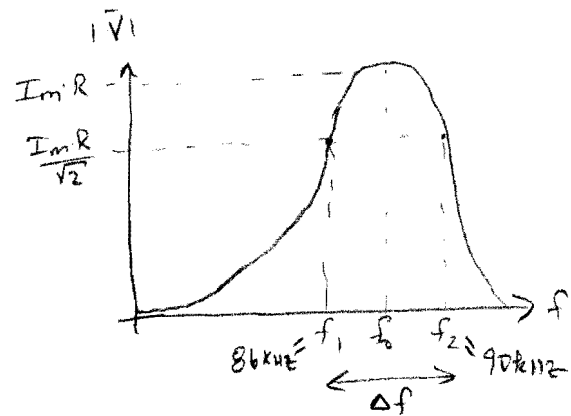
$$(e) \quad Q = \frac{\omega_0}{B} = \frac{176\pi}{8\pi} = \underline{22}$$



$$\Delta f = (90 - 86) \text{kHz} = 4 \text{kHz}$$

$$f_0 \approx \frac{1}{2}(f_1 + f_2) = 88 \text{kHz}$$

$$Q = \frac{f_0}{\Delta f} = \underline{22}$$

## Solution #.39

$$\bar{Y}_{in} = \frac{1}{R + j\omega L} + j\omega C = j\omega C + \frac{R - j\omega L}{R^2 + \omega^2 L^2}$$


At resonance,  $\text{Im}(\bar{Y}_{in}) = 0$ , i.e.

$$\omega_0 C - \frac{\omega_0 L}{R^2 + \omega_0^2 L^2} = 0$$

$$R^2 + \omega_0^2 L^2 = \frac{L}{C}$$

$$\omega_0 = \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}} = \sqrt{\frac{1}{(40 \times 10^{-3})(1 \times 10^{-6})} - \left(\frac{50}{40 \times 10^{-3}}\right)^2}$$

$$\omega_0 = 4.841 \text{ krad/s}$$

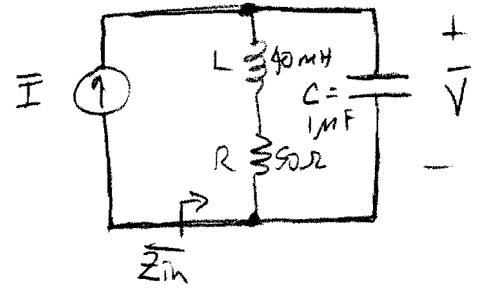

OR, alternatively, at resonance  $\text{Im}(\bar{Z}_{in}) = 0$ .

$$\bar{Z}_{in} = (R + j\omega L) \parallel \frac{1}{j\omega C} = \frac{(R + j\omega L) \cdot \frac{1}{j\omega C}}{R + j\omega L + \frac{1}{j\omega C}} = \frac{R + j\omega L}{1 + j\omega RC - \omega^2 LC} \cdot \frac{1 - \omega^2 LC - j\omega RC}{1 - \omega^2 LC - j\omega RC}$$

$$\bar{Z}_{in} = \frac{(R + j\omega L)(1 - \omega^2 LC - j\omega RC)}{(1 - \omega^2 LC)^2 + \omega^2 RC} = \frac{R(1 - \omega^2 LC) - j\omega R^2 C + j\omega L(1 - \omega^2 LC) + \omega^2 LRC}{\text{DEN}}$$

Den is now a real #

$$\text{For resonance, } \text{Im}(\bar{Z}_{in}) = 0 \Rightarrow -\omega_0 R^2 C + \omega_0 L(1 - \omega_0^2 LC) = 0$$

$$L - \omega_0^2 L^2 C = R^2 C$$

$$\text{or } \omega_0^2 L^2 C = L - R^2 C$$

$$\Rightarrow \omega_0^2 = \frac{L}{L^2 C} - \frac{R^2 C}{L^2 C} = \frac{1}{LC} - \frac{R^2}{L^2}$$


$$\therefore \omega_0 = \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}} = 4,841.2 \frac{\text{rad}}{\text{s}}$$

$$(\text{or } f_0 = 770.5 \text{ Hz})$$


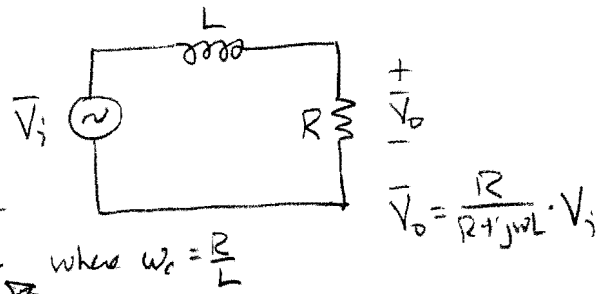
## Solution 14.47

$$H(\omega) = \frac{V_o}{V_i} = \frac{R}{R + j\omega L} = \frac{1}{1 + j\omega L/R} = \frac{1}{1 + j\frac{\omega}{\omega_c}}$$



where  $\omega_c = \frac{R}{L}$

$H(0) = 1$  and  $H(\infty) = 0$  showing that this circuit is a lowpass filter.

Low pass filter form.


At the corner frequency,  $|H(\omega_c)| = \frac{1}{\sqrt{2}}$ , i.e.

$$\frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1 + \left(\frac{\omega_c L}{R}\right)^2}} \longrightarrow 1 = \frac{\omega_c L}{R} \quad \text{or} \quad \omega_c = \frac{R}{L}$$

Hence,

$$\omega_c = \frac{R}{L} = 2\pi f_c$$

$$f_c = \frac{1}{2\pi} \cdot \frac{R}{L} = \frac{1}{2\pi} \cdot \frac{10 \times 10^3}{2 \times 10^{-3}} = 796 \text{ kHz}$$

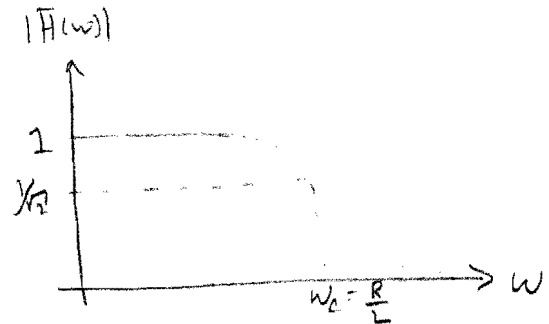

**Solution 14.50**

Determine what type of filter is in Fig. 14.87. Calculate the corner frequency  $f_c$ .

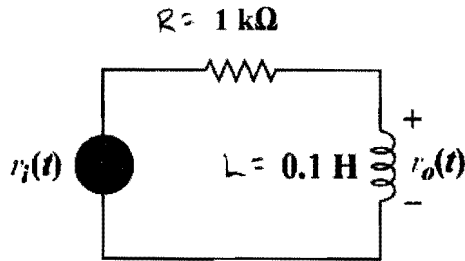


Figure 14.87  
For Prob. 14.50.

**Solution** By voltage division  $\bar{V}_o = \frac{j\omega L}{j\omega L + R} \bar{V}_i$


$$H(\omega) = \frac{V_o}{V_i} = \frac{j\omega L}{R + j\omega L} = \frac{1}{1 + \frac{R}{j\omega L}} = \frac{1}{1 - j\frac{\omega_c}{\omega}} \quad \text{where } \omega_c = \frac{R}{L}$$

$H(0) = 0$  and  $H(\infty) = 1$  showing that **this circuit is a highpass filter.**

$$|H(\omega_c)| = \frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1 + \left(\frac{R}{\omega_c L}\right)^2}} \longrightarrow 1 = \frac{R}{\omega_c L}$$

or  $\omega_c = \frac{R}{L} = 2\pi f_c$
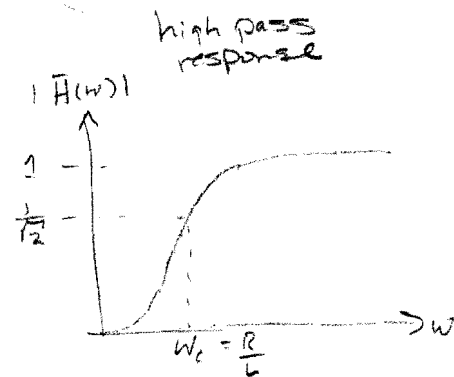
$$f_c = \frac{1}{2\pi} \cdot \frac{R}{L} = \frac{1}{2\pi} \cdot \frac{1,000}{0.1} = 1.5915 \text{ kHz.}$$



## Solution 14.53

$$\omega_1 = 2\pi f_1 = 20\pi \times 10^3 \text{ rad/s}$$

$$\omega_2 = 2\pi f_2 = 22\pi \times 10^3 \text{ rad/s}$$

$$B = \omega_2 - \omega_1 = 2\pi \times 10^3 \text{ rad/s}$$

$$\omega_0 \approx \frac{\omega_2 + \omega_1}{2} = 21\pi \times 10^3 \text{ rad/s}$$

$$Q = \frac{\omega_0}{B} = \frac{21\pi}{2\pi} = 10.5$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \longrightarrow L = \frac{1}{\omega_0^2 C}$$

$$L = \frac{1}{(21\pi \times 10^3)^2 (80 \times 10^{-12})} = 2.872 \text{ H}$$

huge!!

(14.39):

$$B = \frac{R}{L} \longrightarrow R = BL$$

$$R = (2\pi \times 10^3)(2.872) = 18.045 \text{ k}\Omega$$

unusual for a series RLC circuit to have such a large resistance.

