

Solution 14.62

This is a highpass filter.

$$H(\omega) = \frac{j\omega RC}{1 + j\omega RC} = \frac{1}{1 - j/\omega RC}$$

$$H(\omega) = \frac{1}{1 - j\omega_c/\omega}, \quad \omega_c = \frac{1}{RC} = 2\pi(1000)$$

$$H(\omega) = \frac{1}{1 - jf_c/f} = \frac{1}{1 - j1000/f}$$

As $\omega \rightarrow 0$, $H(\omega) = 0$
 $\omega \rightarrow \infty$, $H(\omega) = 1$
 ∴ HPF

(a) $H(f = 200 \text{ Hz}) = \frac{1}{1 - j5} = \frac{V_o}{V_i}$
 $f_c/f = \frac{1000}{200}$

$|V_i| = 120 \text{ mV}$

$$|V_o| = \frac{120 \text{ mV}}{|1 - j5|} = 23.53 \text{ mV}$$

(b) $H(f = 2 \text{ kHz}) = \frac{1}{1 - j0.5} = \frac{V_o}{V_i}$
 $f_c/f = \frac{1000}{2000}$


$$|V_o| = \frac{120 \text{ mV}}{|1 - j0.5|} = 107.3 \text{ mV}$$

(c) $H(f = 10 \text{ kHz}) = \frac{1}{1 - j0.1} = \frac{V_o}{V_i}$
 $f_c/f = \frac{1000}{10000}$

$$|V_o| = \frac{120 \text{ mV}}{|1 - j0.1|} = 119.4 \text{ mV}$$

$$|V_o| = |H(f)| |V_i|$$

increasing $|V_o|$ w/ increasing f . makes sense for HPF

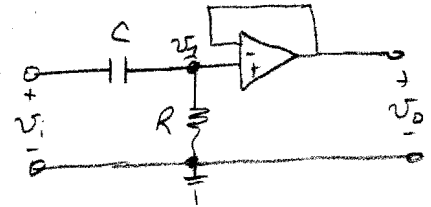

$$\begin{matrix} v_- = v_o \\ v_+ = v_1 \end{matrix} \left. \vphantom{\begin{matrix} v_- = v_o \\ v_+ = v_1 \end{matrix}} \right\} v_+ = v_- \Rightarrow v_o = v_1$$

With input impedance to the op amp = ∞ , then by voltage division

$$v_1 = \frac{R}{R + \frac{1}{j\omega C}} v_i$$

$$v_o = \frac{j\omega C R}{1 + j\omega C R} v_i$$

$$\Rightarrow H(\omega) = \frac{v_o(\omega)}{v_i(\omega)} = \frac{j\omega C R}{1 + j\omega C R}$$

Solution 14.63

For an active highpass filter,

$$\bar{H}(s) = \frac{sC_i R_f}{1 + sC_i R_i} \stackrel{s=j\omega}{=} - \frac{j\omega C_i R_f}{1 + j\omega C_i R_i} \quad (1) \quad (14.63)$$

But given


$$\bar{H}(s) = \frac{10s}{1 + s/10} = - \frac{j\omega 10}{1 + \frac{j\omega}{10}} \quad (2)$$

Comparing (1) and (2) leads to:

$$C_i R_f = 10 \quad \xrightarrow{C_i = 1\mu F} \quad \underline{\underline{R_f = \frac{10}{C_i} = 10M\Omega}} \quad \leftarrow \text{Huge!}$$

$$C_i R_i = 0.1 \quad \xrightarrow{C_i = 1\mu F} \quad \underline{\underline{R_i = \frac{0.1}{C_i} = 100k\Omega}}$$

Fig. 14.43:

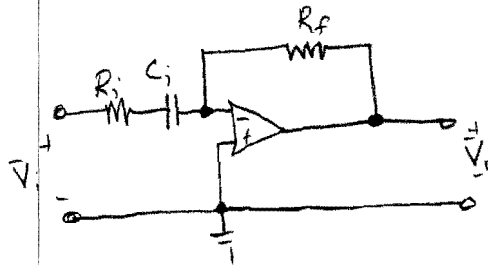HPF:

Solution 14.65

$$\bar{V}_+ = \frac{R}{R + 1/j\omega C} \bar{V}_i = \frac{j\omega RC}{1 + j\omega RC} \bar{V}_i$$


$$\bar{V}_- = \frac{R_i}{R_i + R_f} \bar{V}_o$$

Since $\bar{V}_+ = \bar{V}_-$,

$$\frac{R_i}{R_i + R_f} \bar{V}_o = \frac{j\omega RC}{1 + j\omega RC} \bar{V}_i$$

$$\mathbf{H}(\omega) = \frac{\bar{V}_o}{\bar{V}_i} = \left(1 + \frac{R_f}{R_i}\right) \left(\frac{j\omega RC}{1 + j\omega RC}\right)$$

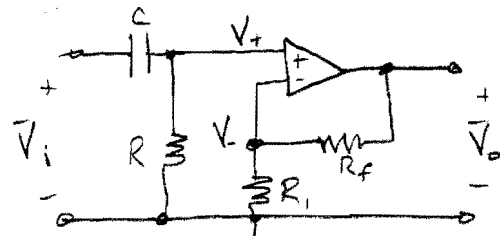It is evident that as $\omega \rightarrow \infty$, the gain is $\underline{\underline{1 + \frac{R_f}{R_i}}}$ and that the corner frequency is $\underline{\underline{\frac{1}{RC}}}$.



$$\bar{V}_- = \frac{R_i}{R_i + R_f} \bar{V}_o \quad \text{and} \quad \bar{V}_- = \bar{V}_+$$

$$\bar{V}_+ = \frac{R}{R + \frac{1}{j\omega C}} \bar{V}_i$$

$$\bar{V}_o = \left(1 + \frac{R_f}{R_i}\right) \cdot \frac{j\omega RC}{1 + j\omega RC} \cdot \bar{V}_i$$

$$\begin{aligned} \bar{H}(\omega) &= \frac{\bar{V}_o(\omega)}{\bar{V}_i(\omega)} = \left(1 + \frac{R_f}{R_i}\right) \cdot \left(\frac{j\omega RC}{1 + j\omega RC}\right) \\ &= \left(1 + \frac{R_f}{R_i}\right) \left(\frac{j\omega/\omega_c}{1 + j\omega/\omega_c}\right) \quad \text{where } \omega_c = \frac{1}{RC} \end{aligned}$$

Solution 14.67

$$\text{DC gain} = \frac{R_f}{R_i} = \frac{1}{4} \xrightarrow{\text{given}} R_i = 4R_f$$


$$\text{Corner frequency} = \omega_c = \frac{1}{R_f C_f} = 2\pi(500) \text{ rad/s} \xrightarrow{\text{given}}$$

If we select $R_f = 20 \text{ k}\Omega$, then $R_i = 80 \text{ k}\Omega$ and

$$C = \frac{1}{(2\pi)(500)(20 \times 10^3)} = \underline{\underline{15.915 \text{ nF}}}$$

Therefore, if $R_f = 20 \text{ k}\Omega$, then $R_i = 80 \text{ k}\Omega$ and $C = 15.915 \text{ nF}$

From Fig. 14.42

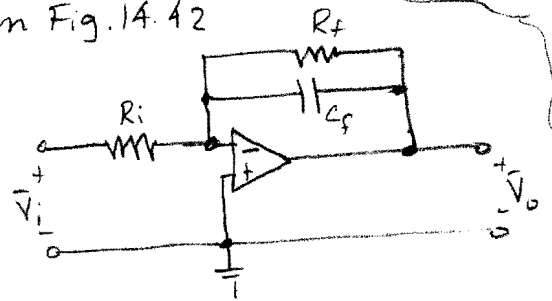

From (14.60):

$$H(\omega) = -\frac{R_f}{R_i} \frac{1}{1 + j\omega C_f R_f}$$

$$= -\frac{R_f}{R_i} \frac{1}{1 + j\frac{\omega}{\omega_c}}$$

$$\omega_c = \frac{1}{C_f R_f}$$

Solution 14.69

This is a highpass filter with $f_c = 2 \text{ kHz}$.

From (14.44): $\omega_c = 2\pi f_c = \frac{1}{RC}$

$$RC = \frac{1}{2\pi f_c} = \frac{1}{4\pi \times 10^3}$$

10^8 Hz may be regarded as high frequency. Hence the high-frequency gain is

$$\frac{-R_f}{R} = \frac{-10}{4}$$

or $R_f = 2.5R$

If we let $R = 10 \text{ k}\Omega$, then $R_f = 25 \text{ k}\Omega$, and $C = \frac{1}{4000\pi \times 10^4} = 7.96 \text{ nF}$.

This is a first-order active high pass filter of Fig. 14.43. where $R_i = R$ & $C_i = C$.

relative to $f_c = 2 \text{ kHz}$.

Solution 14.102 : $R = 4 \text{ k}\Omega$; $C = 40 \text{ nF}$

- (a) When $R_s = 0$ and $R_L = \infty$, we have a low-pass filter.

$$\omega_c = 2\pi f_c = \frac{1}{RC}$$

$$f_c = \frac{1}{2\pi RC} = \frac{1}{(2\pi)(4 \times 10^3)(40 \times 10^{-9})} = \underline{\underline{994.7 \text{ Hz}}}$$



- (b) We obtain R_{Th} across the capacitor. - as seen by the capacitor.

$$R_{Th} = R_L \parallel (R + R_s) \quad R_s = 1 \text{ k}\Omega, R_L = 5 \text{ k}\Omega \rightarrow$$

$$R_{Th} = 5 \parallel (4 + 1) = 2.5 \text{ k}\Omega$$

$$f_c = \frac{1}{2\pi R_{Th} C} = \frac{1}{(2\pi)(2.5 \times 10^3)(40 \times 10^{-9})}$$

$$\underline{\underline{f_c = 1.59 \text{ kHz}}}$$

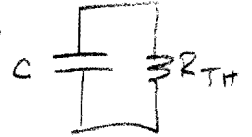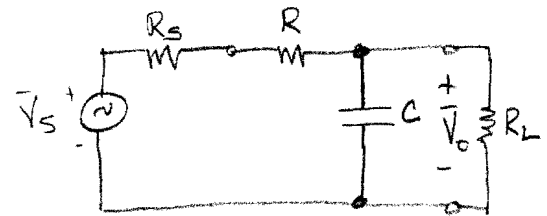

Solution 15.3

From Tables 15.1 & 15.2 :

$$(a) \quad \mathcal{L}[e^{-2t} \cos(3t)u(t)] = \frac{s+2}{(s+2)^2+9} \quad ; \quad \mathcal{L}\{e^{-at} \cos(\omega t)u(t)\} = \frac{s+a}{(s+a)^2+\omega^2}$$

$$(b) \quad \mathcal{L}[e^{-2t} \sin(4t)u(t)] = \frac{4}{(s+2)^2+16} \quad ; \quad \mathcal{L}\{e^{-at} \sin(\omega t)u(t)\} = \frac{\omega}{(s+a)^2+\omega^2}$$

$$(c) \quad \text{Since } \mathcal{L}[\cosh(at)] = \frac{s}{s^2-a^2} \quad ; \quad \cosh(u) = \cos(ju) \Rightarrow \mathcal{L}\{\cosh(at)\} = \mathcal{L}\{\cos(jat)\} = \frac{s}{s^2-a^2}$$

$$\mathcal{L}[e^{-3t} \cosh(2t)u(t)] = \frac{s+3}{(s+3)^2-4} \quad \text{Frequency shift: } e^{-at} f(t) \xleftrightarrow{\mathcal{L}} F(s+a), a=3$$

$$(d) \quad \text{Since } \mathcal{L}[\sinh(at)] = \frac{a}{s^2-a^2} \quad ; \quad \sinh(u) = -j \sin(ju) \Rightarrow \mathcal{L}\{\sinh(at)\} = \mathcal{L}\{\sin(jat)\} = \frac{-j \cdot ja}{s^2-a^2}$$

$$\mathcal{L}[e^{-4t} \sinh(t)u(t)] = \frac{1}{(s+4)^2-1} \quad \text{Frequency shift: } e^{-at} f(t) \xleftrightarrow{\mathcal{L}} F(s+a), a=4$$

$$(e) \quad \mathcal{L}[e^{-t} \sin(2t)] = \frac{2}{(s+1)^2+4} \quad \leftarrow \text{First step.}$$

$$\text{If } f(t) \leftrightarrow F(s)$$

$$t f(t) \leftrightarrow \frac{-d}{ds} F(s) \quad ; \quad \text{Table 15.1}$$


$$\text{Thus, } \mathcal{L}[te^{-t} \sin(2t)] = \frac{-d}{ds} [2((s+1)^2+4)^{-1}] = -\frac{d}{ds} \left[\frac{2}{(s+1)^2+4} \right] = -2 \left\{ \frac{0 - 2(s+1) \cdot 1}{[(s+1)^2+4]^2} \right\}$$

$$= \frac{2}{((s+1)^2+4)^2} \cdot 2(s+1) = \frac{4(s+1)}{[(s+1)^2+4]^2}$$

$$\mathcal{L}[te^{-t} \sin(2t)] = \frac{4(s+1)}{((s+1)^2+4)^2}$$

Practice Problem 15.5

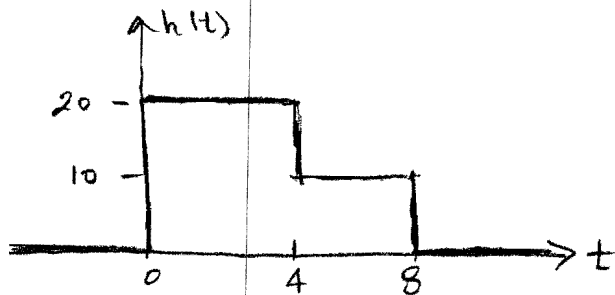Determine the Laplace transform of the function $h(t)$!



We can write $h(t)$ as

$$h(t) = 20 [u(t) - u(t-4)] + 10 [u(t-4) - u(t-8)]$$

Since $\mathcal{L}[u(t)] = \frac{1}{s}$ ϵ

$$\therefore \mathcal{L}[f(t-a)u(t-a)] = e^{-as} F(s)$$

then

$$H(s) = 20 \left[\frac{1}{s} - \frac{e^{-4s}}{s} \right] + 10 \left[\frac{e^{-4s}}{s} - \frac{e^{-8s}}{s} \right]$$

$$\text{or } H(s) = \frac{10}{s} [2 - 2e^{-4s} + e^{-4s} - e^{-8s}]$$

$$H(s) = \frac{10}{s} [2 - e^{-4s} - e^{-8s}]$$

Solution 15.16

Obtain the Laplace transform of $f(t)$ in Fig. 15.28.

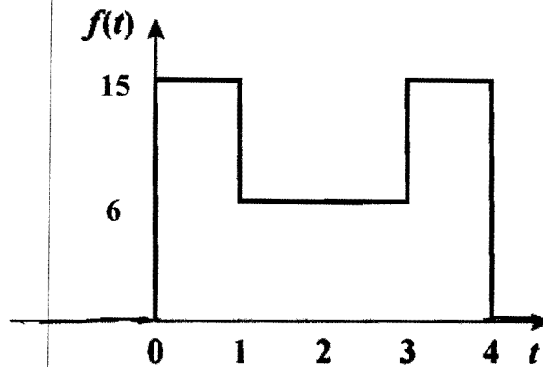


Figure 15.28
For Prob. 15.16.


Solution From the figure above, we can express $f(t)$ directly as

$$f(t) = 15u(t) - 9u(t-1) + 9u(t-3) - 15u(t-4)$$

$$F(s) = [15 - 9e^{-s} + 9e^{-3s} - 15e^{-4s}] / s.$$

$$\mathcal{L}[u(t)] = \frac{1}{s}$$
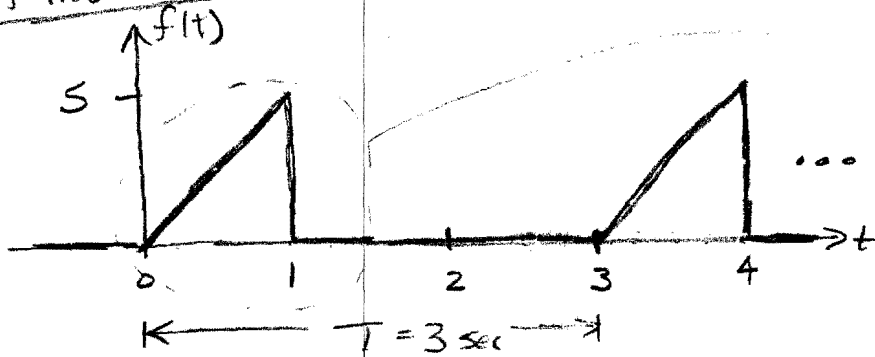
$$\therefore \mathcal{L}[f(t-a)u(t-a)] = e^{-as} F(s)$$



$$f_1(t) = \frac{5t}{1} \cdot t = \frac{5}{1} \cdot t$$



From Table 15.1 for a periodic function

$$\mathcal{L}\{f(t) = f(t+nT)\} = \frac{F_1(s)}{1-e^{-sT}}$$

Laplace transform over first period.

$$F(s) = \mathcal{L}\{f(t)\} = \frac{1}{1-e^{-3s}} \cdot \mathcal{L}\{f_1(t)\}$$
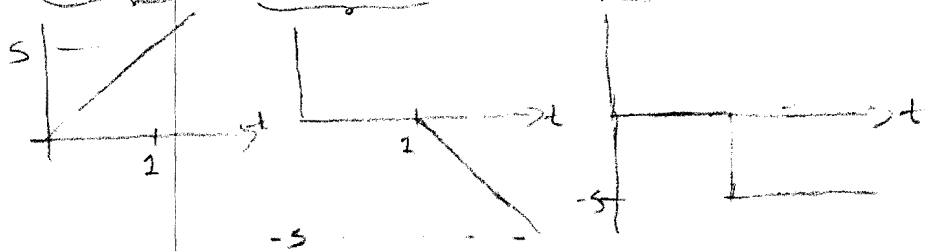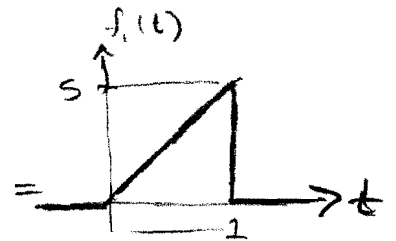
$$f_1(t) = 5t u(t) - 5(t-1)u(t-1) - 5u(t-1)$$



$$F(s) = \frac{1}{1-e^{-3s}} \left[\mathcal{L}\{5t u(t)\} - \mathcal{L}\{5(t-1)u(t-1)\} - \mathcal{L}\{5u(t-1)\} \right]$$

$$= \frac{5}{1-e^{-3s}} \left[\frac{1}{s^2} - \frac{e^{-1 \cdot s}}{s^2} - \frac{e^{-1 \cdot s}}{s} \right]$$

$$F(s) = \frac{5}{s^2(1-e^{-3s})} \cdot (1 - e^{-s} - s e^{-s})$$

Practice Problem 15.7

Obtain the initial and final values of

$$G(s) = \frac{3s^3 + 2s + 6}{s(s+1)^2(s+1.5)} = \frac{3s^3 + 2s + 6}{s(s^2 + 2s + 1)(s + 1.5)}$$

- Using the initial value theorem from Table 15.1:

$$\underline{g(0)} = \lim_{s \rightarrow \infty} sG(s) = \lim_{s \rightarrow \infty} \left[\frac{3s^3 + 2s + 6}{(s^2 + 2s + 1)(s + 1.5)} \right] \rightarrow \frac{3s^3}{s^3} \rightarrow \underline{\underline{3}}$$

- Using the final value theorem from Table 15.1:

$$\underline{\underline{g(\infty)}} = \lim_{s \rightarrow 0} sG(s) = \lim_{s \rightarrow 0} \left[\frac{3s^3 + 2s + 6}{(s^2 + 2s + 1)(s + 1.5)} \right] \rightarrow \frac{6}{1.5} = \underline{\underline{4}}$$