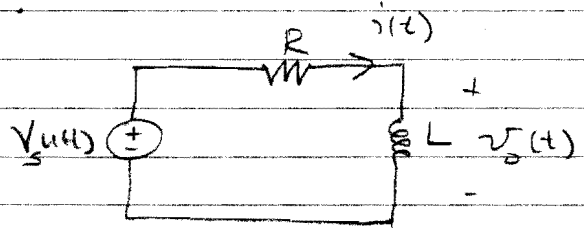


Section 16.1

Let's consider this simple RL circuit:



We'll assume zero initial conditions for the voltage and current.

By KVL: $V_s(t) = R i(t) + L \frac{di(t)}{dt}$ (1)

You analyzed this circuit in Section 7.6.

For $t > 0$, (1) becomes $\frac{di(t)}{dt} + \frac{R}{L} i(t) = \frac{V_s}{L}$

The current $i(t)$ that satisfies this 1st order ODE is

$$i(t) = K_1 e^{-t/\tau} + K_2$$

\uparrow \uparrow
 transient steady state.

or

$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau} \quad (7.53), (2)$$

also our case, $i(\infty) = \frac{V_s}{R}$; $i(0) = 0$

$$\therefore i(t) = \frac{V_s}{R} - \frac{V_s}{R} e^{-t/\tau} = \frac{V_s}{R} [1 - e^{-t/\tau}] \quad \text{where } \tau = \frac{L}{R}.$$

$$i(t) = \begin{cases} 0 & t < 0 \\ \frac{V_s}{R} [1 - e^{-t/\tau}] & t > 0 \end{cases}$$

We can use this current sol'n to calculate the voltage
By KVL,


$$V_s u(t) = Ri(t) + v_o(t)$$

$$\Rightarrow v_o(t) = V_s u(t) - Ri(t)$$

\therefore for $t > 0$

$$v_o(t) = V_s - R \left(\frac{V_s}{R} - \frac{V_s}{R} e^{-t/\tau} \right) = + V_s e^{-t/\tau}$$
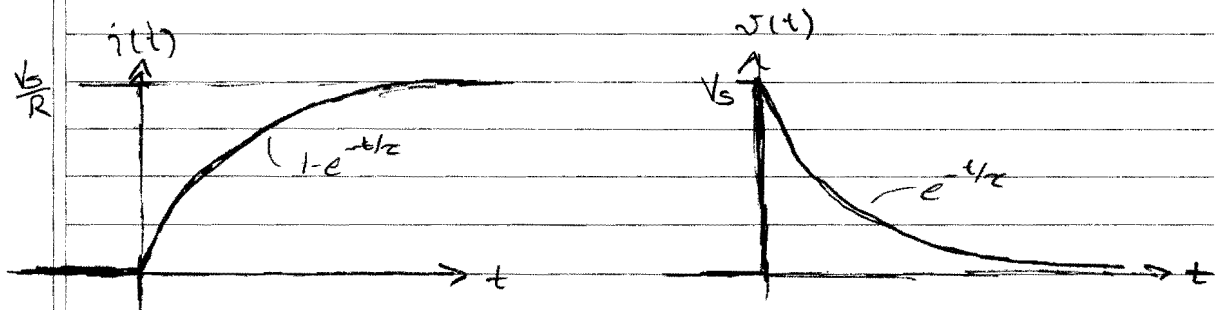
$$\therefore v_o(t) = \begin{cases} 0 & t < 0 \\ V_s e^{-t/\tau} & t > 0 \end{cases}$$



Let's do the same analysis, but now using
the Laplace Transform.