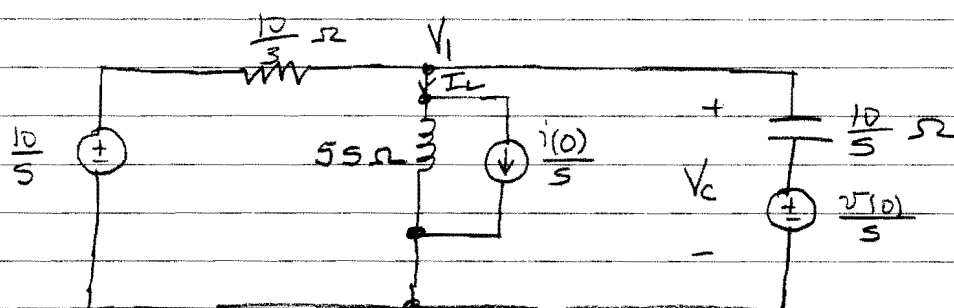


Example 16.4 Calculate $v_C(t)$ in the circuit below if at $t=0$, -1 A flows through the inductor and a 1 V exists across the capacitor.

The first step is to construct the equivalent s -domain electrical ckt noting that both L & C have initial conditions. Use Figs. 16.1 & 16.2:



Note that V_c is the voltage across $C + \frac{v_0}{s}$. $V_c = V_1$.

Using KCL at the V_1 node,

$$\frac{V_1 - \frac{10}{s}}{10/3} + \frac{V_1}{5s} + \frac{i(0)}{s} + \frac{V_1 - \frac{v(0)}{s}}{10/s} = 0 \quad (16.4.1)$$

$$\text{w/ } i(0) = -1 \text{ ; } v(0) = 1 \Rightarrow$$

$$\frac{3}{10} V_1 - \frac{3}{s} + \frac{V_1}{5s} - \frac{1}{s} + \frac{s}{10} V_1 - \frac{s}{10} = 0$$


$$\left(\frac{3}{10} + \frac{1}{5s} + \frac{s}{10}\right) V_1 = \frac{3}{s} + \frac{1}{s} + \frac{1}{2}$$

$$\frac{1}{10} (s^2 + 3s + 2) V_1 = \frac{4}{s} + \frac{1}{2}$$

$$\text{or } (s^2 + 3s + 2) V_1 = 40 + 5s$$

$$V_1 = \frac{40 + 5s}{(s+1)(s+2)} = \frac{A}{s+1} + \frac{B}{s+2}$$

P.F.E.

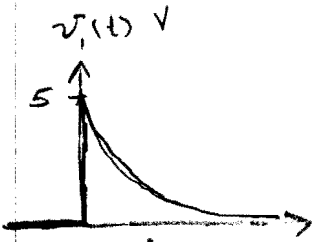

Referring to the original circuit, does this time domain response make sense?

Solving the P.F.E. gives $A = \frac{40-5}{1} = 35$

$$B = \frac{40-10}{-1} = -30$$

$$\therefore V_1 = \frac{35}{s+1} - \frac{30}{s+2}$$

$$\underline{v_1(t)} = \mathcal{L}^{-1}\{V_1\} = 35e^{-t}u(t) - 30e^{-2t}u(t)$$

At $t=0$, $v_1(0) = 35 - 30 = 5V$ ✓

Practice Problem 16.4 For the previous problem, determine the current through the inductor $\forall t > 0$.

We determined that $V_1 = \frac{35}{s+1} + \frac{30}{s+2} V$.

Then, referring to the s-domain circuit: $i(0) = -1A$

$$I_L = \frac{V_1}{5s} + \frac{i(0)}{s} = \frac{35}{5s(s+1)} - \frac{30}{5s(s+2)} - \frac{1}{s}$$

↑
initial condition.

From Table 15.1 $\frac{1}{s}F(s) \leftrightarrow \int_0^t f(x)dx$

$$i_L(t) = \int_0^t 7e^{-x} dx - \int_0^t 6e^{-2x} dx - u(t)$$

$$= \frac{7}{(-1)} e^{-x} \Big|_0^t - \frac{6}{(-2)} e^{-2x} \Big|_0^t - u(t)$$

$$= -7(e^{-t} - 1)^{u(t)} + 3(e^{-2t} - 1)^{u(t)} - u(t)$$

$$= (-7e^{-t} + 7 + 3e^{-2t} - 3 - 1)u(t)$$

Tricky:

$$\therefore i_L(t) = [3 - 7e^{-t} + 3e^{-2t}] u(t) \text{ A}$$


Check initial: find states

• at $t=0$, $i_L(t) = 3 - 7 + 3 = -1 \text{ A}$. $v = i(0)$


• at $t=\infty$? $i_L(t) = 3 \text{ A}$. Make sense?

Check: $i_r = i_L = \frac{10}{10/3} = 3 \text{ A}$ ✓ Yes.

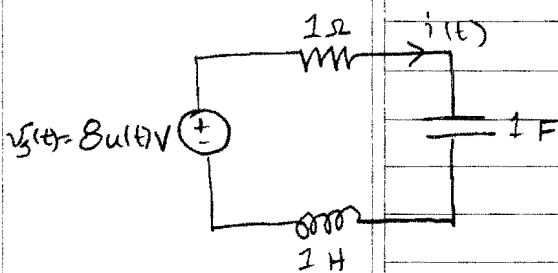Problem 16.12 Determine $i(t)$ in the circuit shown below



Equiv.
s-domain
ckt

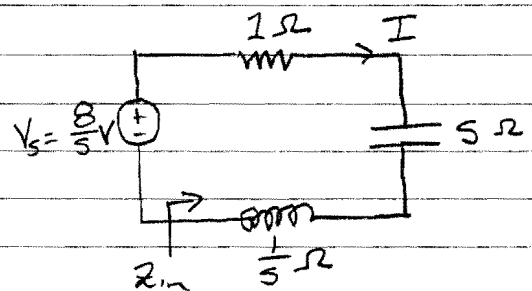

$$Z_{in} = 1 + s + \frac{1}{s}$$

$$\therefore I = \frac{V_s}{Z_{in}} = \frac{8/s}{1 + s + \frac{1}{s}} = \frac{8}{s^2 + s + 1}$$

Complete the square:
$$I = \frac{8}{\left(s + \frac{1}{2}\right)^2 + \frac{3}{4}}$$

$$\left(s + \frac{1}{2}\right)^2 = s^2 + \frac{s}{2} + \frac{s}{2} + \frac{1}{4}$$

With an eye towards the Laplace transform pair

$$e^{-at} \sin \omega t \xleftrightarrow{\omega} \frac{\omega}{(s+a)^2 + \omega^2}$$


then $\omega^2 = \frac{3}{4}$

$$I = 8 \frac{1}{\sqrt{3}} \frac{\sqrt{3}/2}{(5 + \frac{1}{2})^2 + (\frac{\sqrt{3}}{2})^2}$$

$$\Rightarrow i(t) = \mathcal{L}^{-1}\{I\} = \frac{16}{\sqrt{3}} e^{-\frac{t}{2}} \sin\left(\frac{\sqrt{3}}{2}t\right) u(t) \text{ A}$$


- Mathematica Plot
- why oscillations?
- why dampings?
- BZ spike
- Diff eq.
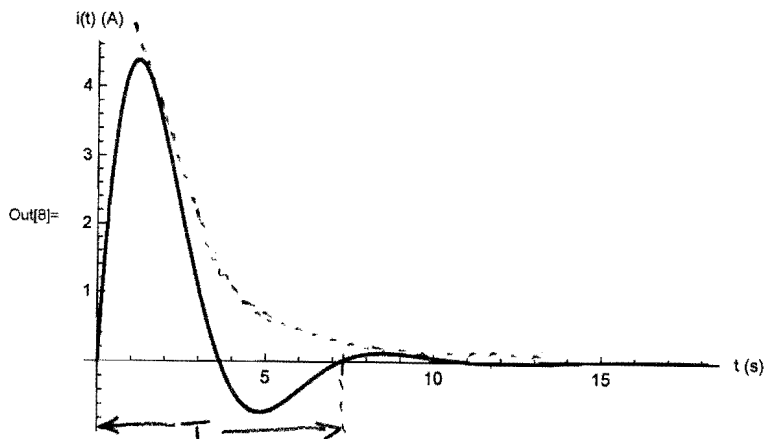
```
In[8]:= Plot[16 / Sqrt[3] * Exp[-t / 2] * Sin[Sqrt[3] / 2 * t],
  {t, 0, 5 * 2 * Pi / Sqrt[3]}, PlotRange -> All, AxesLabel -> {"t (s)", "i(t) (A)"}]
```




$$\omega = \frac{\sqrt{3}}{2} \Rightarrow T = \frac{2\pi}{\omega} = \frac{2\pi}{\sqrt{3}/2} = \frac{4\pi}{\sqrt{3}} = 7.26 \text{ s}$$

B2 Spice Simulation

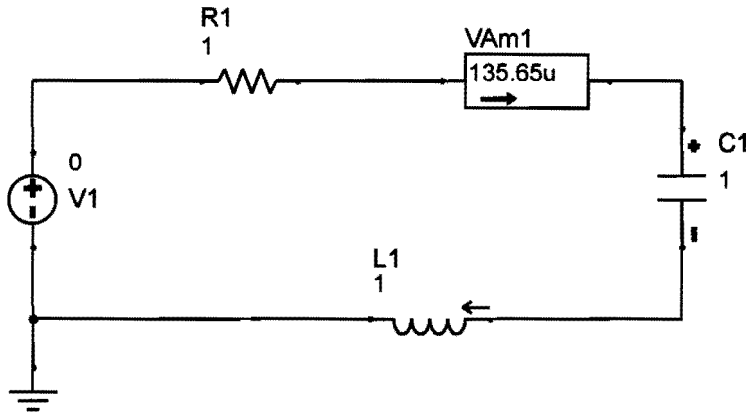

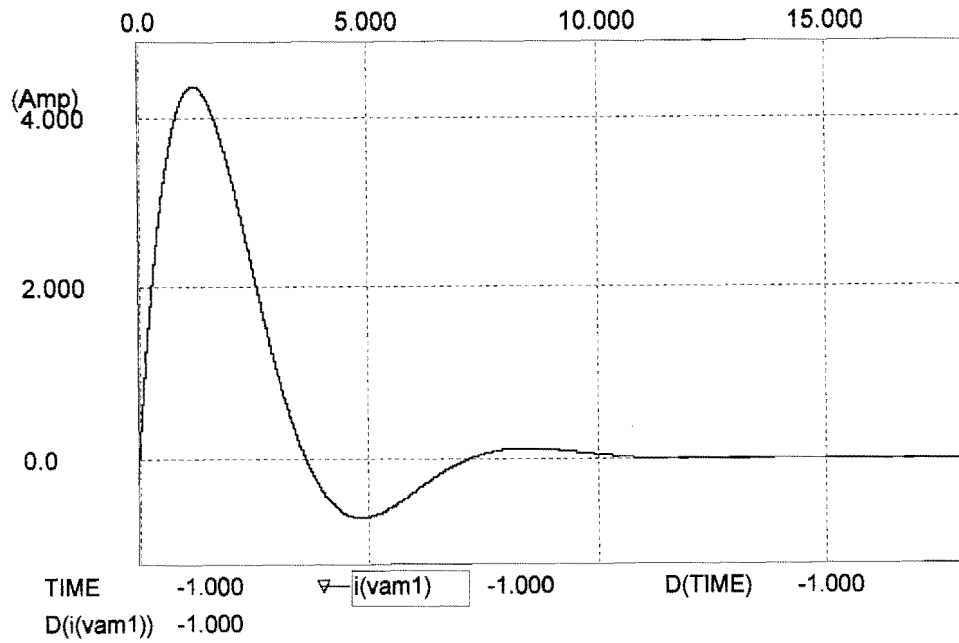Circuit simulation, Prob-Transient-2-Graph Time (s)



| |
|---------------|
| Title : |
| Description : |
| ID : |
| Designer : |
| Date : |

Chapter 6 of
the text :

Differential eqn. approach. What if we didn't use Laplace transform. How would we solve such a problem?

Form integro-differential eqn & solve.

$$\text{For } C: \quad v_C(t) = \frac{1}{C} \int_0^t i_C(\tau) d\tau + v_C(t_0) \quad (6.6)$$

$$\text{For } L: \quad v_L(t) = L \frac{di_L(t)}{dt} \quad (6.18)$$

By KVL:

$$v_S(t) = v_R(t) + v_C(t) + v_L(t)$$

For $t > 0$ & zero initial conditions

$$8 = 1 \cdot i(t) + \frac{1}{1} \int_0^t i(\tau) d\tau + 1 \cdot \frac{di(t)}{dt}$$

$$\text{or} \quad \frac{di(t)}{dt} + \int_0^t i(\tau) d\tau + i(t) = 8.$$

This is an integro-differential eqn. Difficult to solve.