


12.6 Balanced Delta-Wye Connection

Fig. 12.18.

Once again, we wish to solve for the line currents in the problem.

There are many ways to accomplish this analysis. We'll transform the Δ connected source to a wye source, then analyze each phase separately.

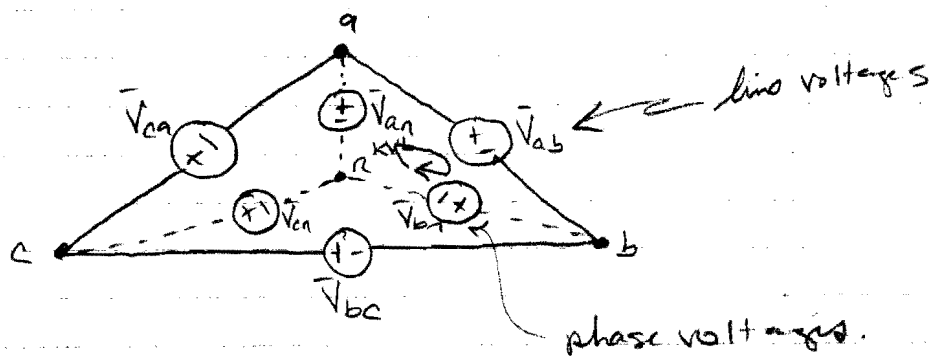The Δ connected source voltages can be related to the wye connected source voltages as sketched in Fig. 12.19:



We're given the line voltages to be

$$\bar{V}_{ab} = V_p \angle 0^\circ, \quad \bar{V}_{bc} = V_p \angle -120^\circ, \quad \bar{V}_{ca} = V_p \angle -240^\circ \quad (12.34)$$

KVL around loop above: $\bar{V}_{an} = \bar{V}_{ab} + \bar{V}_{bn}$ or $\bar{V}_{an} - \bar{V}_{bn} = \bar{V}_{ab}$ (1)

With positive abc sequence phasing, then $\bar{V}_{bn} = \bar{V}_{an} \angle -120^\circ$

$$\begin{aligned} \therefore \bar{V}_{an} - \bar{V}_{bn} &= \bar{V}_{an} - \bar{V}_{an} \angle -120^\circ = \bar{V}_{an} (1 - 1 \angle -120^\circ) = \bar{V}_{an} \left(1 + \frac{1}{2} + j\frac{\sqrt{3}}{2}\right) \\ &= \bar{V}_{an} \sqrt{3} \angle 30^\circ \end{aligned}$$

Solving \rightarrow (1): $\bar{V}_{an} \sqrt{3} \angle 30^\circ = \bar{V}_{ab} = V_p \angle 0^\circ$


$$\therefore \bar{V}_{an} = \frac{V_p}{\sqrt{3}} \angle -30^\circ \quad (12.38)$$

For positive ^{abc} phasing,

$$\bar{V}_{an} = \frac{V_p}{\sqrt{3}} \angle -30^\circ, \quad \bar{V}_{bn} = \frac{V_p}{\sqrt{3}} \angle -150^\circ, \quad \bar{V}_{cn} = \frac{V_p}{\sqrt{3}} \angle 270^\circ \quad (12.38)$$

With these important formulas, we can transform the Δ connected source into an equivalent Y connected one.

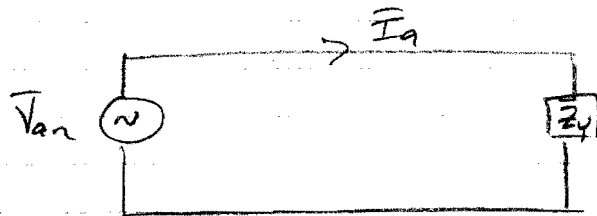For the a-phase, the equivalent ckt is in Fig. 12.20:



Therefore, the phase current is
$$\bar{I}_a = \frac{\bar{V}_{an}}{\bar{Z}_y} = \frac{V_p \angle -30^\circ}{\sqrt{3} \cdot \bar{Z}_y} \quad (12.39)$$

12.7 Power in a Balanced 3 ϕ System


Let's consider the power delivered to a balanced three phase load. We'll consider a Y -connected load.

To calculate instantaneous power we'll work with time domain voltages and currents, and we'll assume positive abc phasing sequence.

$$v_{AN} = \sqrt{2} V_p \cos(\omega t)$$

$$v_{BN} = \sqrt{2} V_p \cos(\omega t - 120^\circ)$$
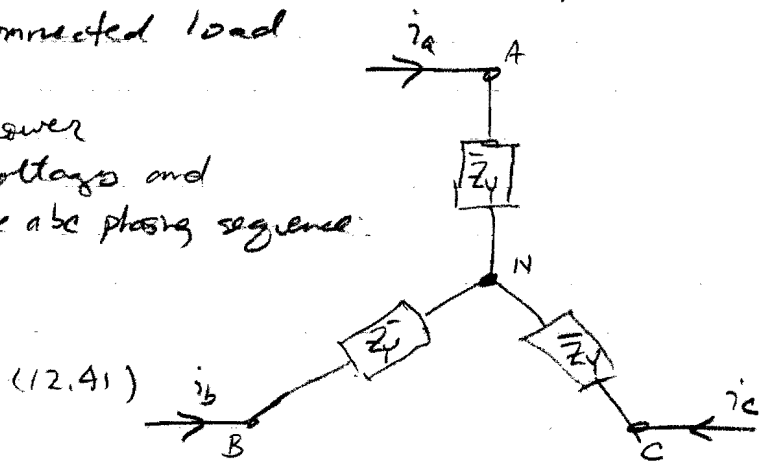
$$v_{CN} = \sqrt{2} V_p \cos(\omega t - 240^\circ)$$



where V_p is an RMS voltage.

If $Z_Y = Z \angle \theta$, then the line (= phase) currents are

$$i_a = \sqrt{2} I_p \cos(\omega t - \theta), \quad i_b = \sqrt{2} I_p \cos(\omega t - \theta - 120^\circ), \quad i_c = \sqrt{2} I_p \cos(\omega t - \theta - 240^\circ) \quad (12.42)$$

Notice we're not relating V_p to I_p as of yet.

The total instantaneous power delivered to the load is the sum of the instantaneous powers delivered to each Z_Y :

$$\begin{aligned} p^{(t)} &= P_a + P_b + P_c = v_{AN} \cdot i_a + v_{BN} \cdot i_b + v_{CN} \cdot i_c \quad (12.43) \\ &= 2V_p I_p \left[\cos(\omega t) \cdot \cos(\omega t - \theta) + \cos(\omega t - 120^\circ) \cos(\omega t - \theta - 120^\circ) \right. \\ &\quad \left. + \cos(\omega t - 240^\circ) \cos(\omega t - \theta - 240^\circ) \right] \end{aligned}$$

Using the trig id. $\cos A \cos B = \frac{1}{2} [\cos(A+B) + \cos(A-B)]$ (12.44)

Then:

$$\underbrace{\cos(\omega t)}_A \underbrace{\cos(\omega t - \theta)}_B = \frac{1}{2} \left[\underbrace{\cos(2\omega t - \theta)}_{A+B} + \underbrace{\cos(\theta)}_{A-B} \right]$$

$$\cos(\omega t - 120^\circ) \cos(\omega t - \theta - 120^\circ) = \frac{1}{2} \left[\cos(2\omega t - \theta - 240^\circ) + \cos(\theta) \right]$$

$$\cos(\omega t - 240^\circ) \cos(\omega t - \theta - 240^\circ) = \frac{1}{2} \left[\cos(2\omega t - \theta - 480^\circ) + \cos(\theta) \right]$$

These

Sub. into (2.43) gives

$$P^{(4)} = 2V_p I_p \cdot \frac{1}{2} \left[3 \cos(\theta) + \cos(2\omega t - \theta) + \cos(2\omega t - \theta - 240^\circ) + \cos(2\omega t - \theta - 480^\circ) \right] \quad (1)$$

Let's focus on these last three terms. With $\gamma = 2\omega t - \theta$:

$$\begin{aligned} & \cos(\gamma) + \cos(\gamma - 240^\circ) + \cos(\gamma - 120^\circ) \\ &= \cos(\gamma) + \cos(\gamma - 240^\circ) + \cos(\gamma + 240^\circ) \end{aligned} \quad (2)$$

Trig id's: $\cos(\alpha - \beta) = \cos\alpha \cos\beta + \sin\alpha \sin\beta$

$$\cos(\alpha + \beta) = \cos\alpha \cos\beta - \sin\alpha \sin\beta$$

$$\therefore \cos(\alpha - \beta) + \cos(\alpha + \beta) = 2 \cos\alpha \cos\beta$$

w/ $\alpha = \gamma$ in (2) ; $\beta = 240^\circ$, then (2) becomes

$$\cos(\gamma) + \cos(\gamma - 240^\circ) + \cos(\gamma + 240^\circ) = \cos\gamma + 2 \cos\gamma \underbrace{\cos(240^\circ)}_{=-1/2}$$

$$= \cos\gamma - \cos\gamma = \underline{\underline{0}}$$

Hence (1) becomes

$$\underline{p(t)} = V_p I_p \cdot 3 \cos \theta = \underline{3 V_p I_p \cos \theta} \quad (12.45)$$

Highly important result: this total instantaneous power delivered to all three loads doesn't vary w/ time! Can show this is the same result for a Δ connected balanced 3 ϕ load.

Since the instantaneous power $p(t)$ in (12.45) is independent of time, the time-averaged power delivered to the load P is equal to that:

$$P = 3 V_p I_p \cos \theta$$

While the real power delivered to each phase of the load, P_p , is simply one third of this since it is a balanced load:

$$P_p = \frac{P}{3} = V_p I_p \cos \theta \quad (12.46)$$

The associated reactive power per phase is then

$$Q_p = V_p I_p \sin \theta \quad (12.47)$$

Such that the apparent power per phase is

$$S_p = V_p I_p \quad (12.48)$$

and the complex power per phase is

$$\underline{S}_p = P_p + j Q_p = \underline{V}_p \underline{I}_p^* \quad (12.49)$$

power (12.46)

We can write the total apparent \hat{V} in a slightly different form

$$P = \sqrt{3} V_L I_L \cos \theta \quad (12.50)$$

where V_L & I_L are line voltage & current, respectively.

Where for a Y-Y connected load $I_L = I_p$ & $V_L = \sqrt{3} V_p$.

While for a Δ - Δ connected load $I_L = \sqrt{3} I_p$ & $V_L = V_p$

Similarly, the total reactive load power can be expressed as

$$Q = 3Q_p = 3V_p I_p \sin \theta = \sqrt{3} V_L I_L \sin \theta \quad (12.51)$$


Consequently, the total complex load power can be expressed as

$$\bar{S} = 3\bar{S}_p = 3\bar{V}_p \bar{I}_p^*$$

Alternatively,
$$\bar{S} = P + jQ = \sqrt{3} V_L I_L \angle \theta \quad (12.53)$$

↑
(12.50); (2.51)

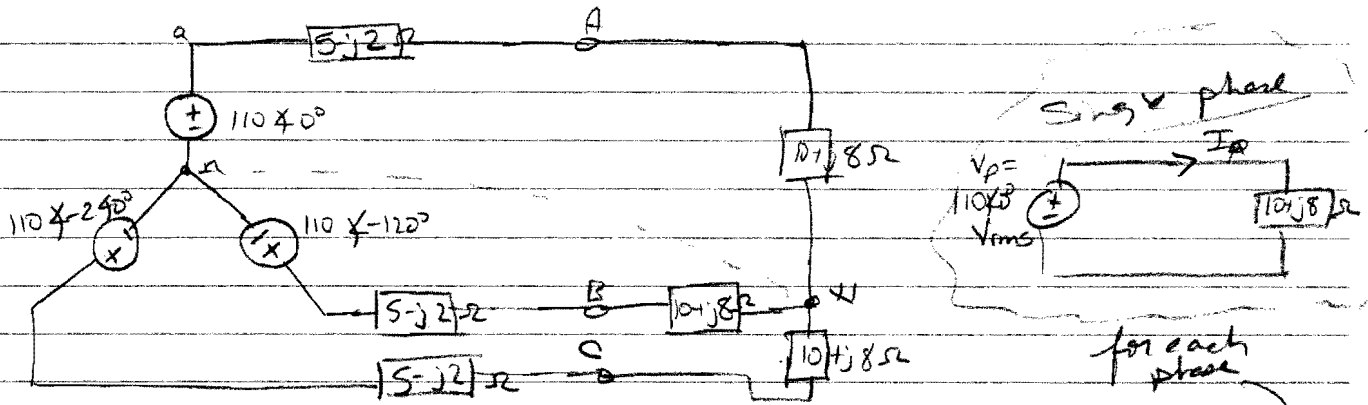Example 12.6 - Y-Y connected balanced 3P System of Example 12.2.



From Example 12.2, $\bar{V}_p = 110\angle 0^\circ \text{ V}_{rms}$; $I_p = 6.81\angle -21.8^\circ \text{ A}_{rms}$ ←

Determine the total average power, reactive power, and complex power supplied by the source, and delivered to the load.

The source complex power is

$$\begin{aligned} \bar{S}_S &= \underset{\substack{\uparrow \\ \text{Source}}}{-3} \bar{V}_p \bar{I}_p^* = -3 (110\angle 0^\circ \text{ V}_{rms}) \cdot (6.81\angle +21.8^\circ \text{ A}_{rms}) \\ &= -2086.59 - j834.57 \text{ VA} = \\ &= P_S \text{ total time avg. power supplied} = Q_S = \text{total reactive power supplied.} \end{aligned}$$

At the load

$$\bar{S}_L = 3 \bar{V}_{rms} \cdot \bar{I}_{rms}^* \quad \text{but} \quad \bar{V}_{rms} = \bar{I}_{rms} \bar{Z}_p$$

not line

$$\bar{S}_L = 3 \bar{I}_{rms} \bar{I}_{rms}^* \bar{Z}_p = 3 |\bar{I}_{rms}|^2 \bar{Z}_p$$

$$= 3 (6.81)^2 \cdot (10 + j8)$$

$$= 1391.28 + j1113.03 \text{ VA}$$

total time avg. power delivered to 3φ load

total reactive power delivered to load.

Notice that $\bar{S}_L \neq \bar{S}_L$. There is also complex power delivered to the line impedances, \bar{S}_l .

$$\begin{aligned}\bar{S}_l &= 3|\bar{I}_p|^2 Z_l = 3(6.8)^2 \cdot (5-j2) \\ &= 695.64 - j278.26 \text{ VA}\end{aligned}$$

Now, $\bar{S}_L + \bar{S}_l = 2086.92 + j834.77 \text{ VA} = -\bar{S}_S$, as expected.

Example 12.7

A three phase motor can be regarded as a balanced Δ connected load. Suppose a 3 ϕ motor draws 5.6 kW when the line voltage is 220 V and the line current is 18.2 A. Determine the power factor of the motor.

$$V_L = 220 \text{ Vrms} \quad \text{and} \quad I_L = 18.2 \text{ Arms}$$

$$\text{The apparent power } S = |\bar{S}| = \sqrt{3} V_L I_L \cos \theta$$

(12.53)

$$\therefore S = \sqrt{3} V_L I_L = \sqrt{3} (220)(18.2) = 6935.13 \text{ VA}$$

The real (time avg) power was given to be 5600 W.

$$\therefore \text{pf} = \cos \theta = \frac{P}{S} = \frac{5600}{6935.13} = \underline{\underline{0.8075}}$$

