


① Ex. 8.21

$$V_{BB} = 1.7V$$

$$I_B = \frac{V_{BB} - V_B}{R_B} = \frac{1.7 - 0.7}{10k} = 0.1mA$$

$$I_C = \beta I_B = 50 \times 0.1mA = 5mA, \quad V_C = V_{CC} - R_C I_C = 10 - (1k)(50mA) = 5V$$

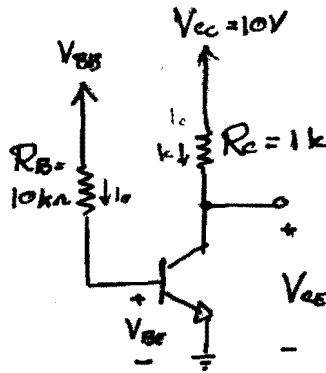
So $V_C > V_B$ Verifying that the transistor is operating in Active mode.



② In order to operate at the edge of saturation, R_C must be increased to make $V_{CE} = 0.3V$

AND
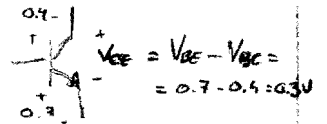
$$R_C = \frac{V_{CC} - V_{CE}}{I_C} = \frac{10 - 0.3}{5mA} = 1.94k\Omega$$



③ In order to operate in saturation mode, R_C must be increased so


$$V_{CE} = 0.2V \quad \text{and} \quad \beta_{forced} = 10$$

$$I_C = \beta_{forced} \times I_B = 10 \times 0.1mA = 1mA$$

$$R_C = \frac{V_{CC} - V_{CE}}{I_C} = \frac{10 - 0.2}{1mA} = 9.8k\Omega$$



② PROBLEM 6.48

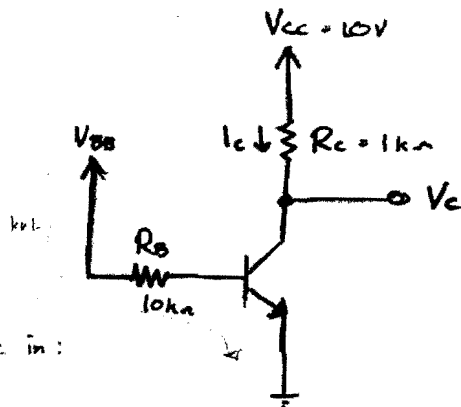

V_{BB} that make transistor operate in:

$$\beta = 50$$

Ⓐ Active mode with $V_c = 2V$,

$$I_C = \frac{V_{CC} - V_c}{R_C} = \frac{10 - 2}{1k} = 8 \text{ mA}$$

$$I_B = \frac{I_C}{\beta} = \frac{8 \text{ mA}}{50} = 0.16 \text{ mA}$$

$$V_{BB} = I_B R_B + V_{BE} = 0.16 \text{ mA} \times 10k\Omega + 0.7 = \underline{2.3V}$$

Ⓑ at edge of saturation

$$V_{CE} = 0.3V, \quad V_{BC} = 0.4V$$

$$I_C = \frac{V_{CC} - V_{CE}}{R_C} = \frac{10 - 0.3}{1k} = 9.7 \text{ mA}$$

$$I_B = \frac{I_C}{\beta} = \frac{9.7 \text{ mA}}{50} = 0.194 \text{ mA}$$

$$V_{BB} = I_B R_B + V_{BE} = 0.194 \text{ mA} \times 10k\Omega + 0.7 = \underline{2.64V}$$

Ⓒ in saturation with $\beta_{forced} = 10$ and

$$V_{CE} = 0.2V$$

$$I_C = \frac{V_{CC} - V_{CE}}{R_C} = \frac{10 - 0.2}{1k} = 9.8 \text{ mA}$$

$$I_B = \frac{I_C}{\beta_{forced}} = \frac{9.8 \text{ mA}}{10} = 0.98 \text{ mA}$$

$$V_{BB} = I_B R_B + V_{BE} = 0.98 \text{ mA} \times 10k\Omega + 0.7V = \underline{10.5V}$$

③ Problem 6.50

Assuming Saturation, $V_{CE} = 0.2V$

$$V_{CE} = V_E - V_C$$

$$0.2 = 5V - V_C$$


$$V_C = 4.8$$

$$I_C = \frac{V_C}{R_C} = \frac{4.8V}{1k} = 4.8mA$$

$$\text{KVL } 5 - V_{BE} - I_B \times R_B = 0 \rightarrow I_B = \frac{5 - V_{BE}}{R_B} = \frac{4.3}{10k} = 0.43mA$$

$$\beta_{forced} = \frac{I_C}{I_B} = \frac{4.8}{0.43} = \underline{11.2}$$

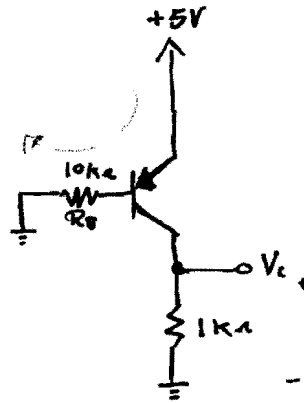which is $< \beta = 50$ so the transistor is
operating in Saturation mode.



$$\beta = 50$$

to operate in Edge Saturation

$$V_{CE} = 0.3V \quad \text{and} \quad I_C / I_B = \beta = 50$$

$$V_{CE} = V_E - V_C \quad , \quad V$$

$$0.3 = 5 - V_C \rightarrow V_C = 4.7V$$

$$I_C = \frac{V_C}{R_C} = 4.7mA$$

$$I_B = \frac{I_C}{\beta} = 0.094mA \quad , \quad V$$

$$R_B = \frac{V_B}{I_B} = \frac{4.3V}{0.094mA} = \underline{45.74k\Omega}$$

$$\text{Same } V_{BE} = V_E - V_B \rightarrow V_B = V_E - V_{BE} = 5 - 0.7 = 4.3V$$

④ PROBLEM 10.22

$f_T = 10 \text{ GHz}$ and $C_P = 0.1 \text{ pF}$ when operate at $I_C = 1.0 \text{ mA}$

What is C_X in this case, and find g_m . For $\beta = 120$ find r_π and f_β

$$f_T = \frac{g_m}{2\pi(C_X + C_P)}$$

$$g_m = \frac{I_C}{V_T} = \frac{0.1 \text{ mA}}{0.025 \text{ V}} = \underline{40 \text{ mA/V}}$$

$$10 \times 10^9 = \frac{40}{2\pi(C_X + 0.1 \times 10^{-12})} \quad \text{solve for } C_X.$$

$$C_X = \underline{0.54 \text{ pF}}$$

$$r_\pi = \frac{\beta}{g_m} = \frac{120}{40 \text{ mA/V}} = \underline{3 \text{ k}\Omega}$$

$$f_\beta = \frac{f_T}{\beta} = \frac{10 \times 10^9}{120} = \underline{83.3 \text{ MHz}}$$

⑤ PROBLEM 10.37

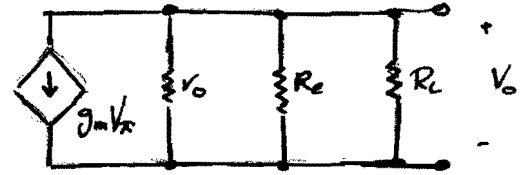
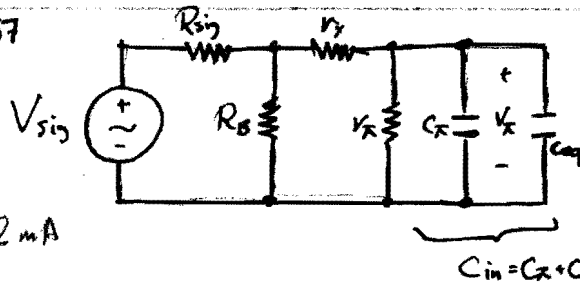


Fig. 10.9 (c)

$$I_E = 2 \text{ mA}$$

$$g_m = \frac{I_C}{V_T} = \frac{2 \text{ mA}}{0.025} = 80 \text{ mA/V}$$

$$r_x = \frac{\beta}{g_m} = \frac{100}{80 \text{ mA/V}} = 1.25 \text{ k}\Omega$$

$$r_o = \frac{V_A}{I_C} = \frac{100 \text{ V}}{2 \text{ mA}} = 50 \text{ k}\Omega$$

$$C_x + C_\mu = \frac{g_m}{\omega_T} = \frac{80 \times 10^{-3} \text{ A/V}}{2\pi \times 800 \times 10^6} = 16 \text{ pF}$$

$$C_\mu = 1 \text{ pF}, \quad C_x = 15 \text{ pF}$$

$$r_x = 50 \Omega$$

$$R_B = 50 \text{ k}\Omega, \quad R_C = 4 \text{ k}\Omega$$

$$\text{the new } A_m = - \frac{R_B}{R_B + R_{sig}} \times \frac{r_x}{r_x + r_x + (R_B \parallel R_{sig})} (g_m R_L')$$

$$\text{where } R_L' = r_o \parallel R_C \parallel R_L$$

$$= 50 \text{ k}\Omega \parallel 4 \text{ k}\Omega \parallel 5 \text{ k}\Omega = 2.13 \text{ k}\Omega$$

$$g_m R_L' = 80 \text{ mA/V} \times 2.13 \text{ k}\Omega = 170 \text{ V/V}$$

$$A_m = - \frac{50 \text{ k}\Omega}{50 \text{ k}\Omega + 5 \text{ k}\Omega} \times \frac{1.25 \text{ k}\Omega}{1.25 \text{ k}\Omega + 50 \Omega + (50 \parallel 5)} \times 170 = -33 \text{ V/V} \quad (-39 \text{ dB})$$

and

$$20 \log |A_m| = 30.4 \text{ dB}$$

↓ ($\approx 1.6 \text{ dB}$) Compared to the previous value of 39 V/V (32 dB), to determine f_H we have to find C_{in}

$$(10.58) \rightarrow C_{in} = C_x + C_\mu (1 + g_m R_L') = 15 + 1(1 + 170) = 186 \text{ pF}$$

$$R_{sig}' = r_x \parallel [r_x + (R_B \parallel R_{sig})] = 1.25 \parallel [0.05 + (50 \parallel 5)] = 980 \Omega$$

$$f_H = \frac{1}{2\pi C_{in} R_{in}} = \frac{1}{2\pi \times 186 \times 10^{-12} \times 0.98 \times 10^3} = 873 \text{ kHz} \quad (\text{Compared to } 754 \text{ kHz before})$$


$$GB = |A_m| f_H = 33 \times 873 = 28.8 \text{ MHz}$$

$$\text{boki. } GB = 39 \times 873 = 29.4 \text{ MHz}$$

Power dissipation increased by factor of 2

$$P_{dis} = \underbrace{V_{CE}}_{\text{unchanged}} \cdot I_C \uparrow \times 2$$

⑥ PROBLEM 10.37

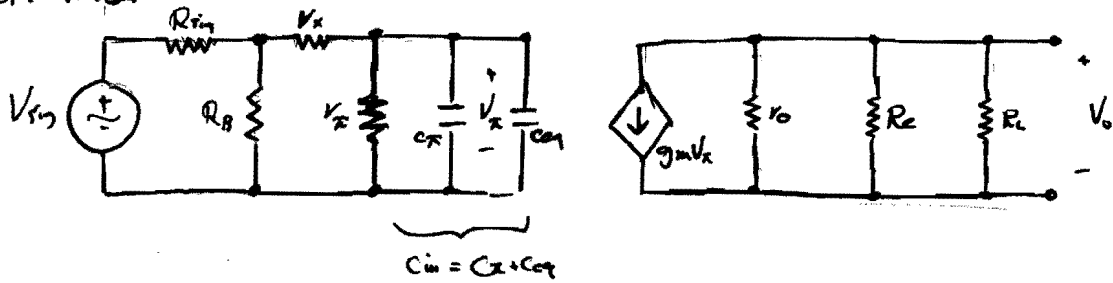

$$A_m = - \frac{R_B}{R_B + R_{sig}} \frac{r_x}{r_x + r_x + (R_{sig} \parallel R_B)} g_m R_L' \quad (10.54)$$

FOR $R_B \gg R_{sig}$, $r_x \ll R_{sig}$, $R_{sig} \gg r_x$

$$A_m \approx - \frac{r_x}{R_{sig}} g_m R_L' = - \beta R_L' / R_{sig}$$

⑦

$$C_{in} = C_x + (g_m R_L' + 1) C_\mu \quad (10.58)$$

$$g_m R_L' \gg 1 \quad \text{and} \quad g_m R_L' C_\mu \gg C_x$$

$$(10.57) \quad C_{in} \approx g_m R_L' C_\mu, \quad f_H = \frac{1}{2\pi C_{in} R_{sig}'}$$

$$\text{where } R_{sig}' = r_x \parallel [r_x + (R_B \parallel R_{sig})]$$

$$\approx r_x \parallel R_{sig} \approx r_x$$

$$\text{So } f_H = \frac{1}{2\pi g_m R_L' C_\mu r_x}, \quad \beta = g_m r_x \quad \rightarrow f_H = \frac{1}{2\pi C_\mu \beta R_L'}$$

⑧

$$GB = |A_m| f_H = \beta \frac{R_L'}{R_{sig}} \frac{1}{2\pi C_\mu \beta R_L'} = \frac{1}{2\pi C_\mu R_{sig}}$$