
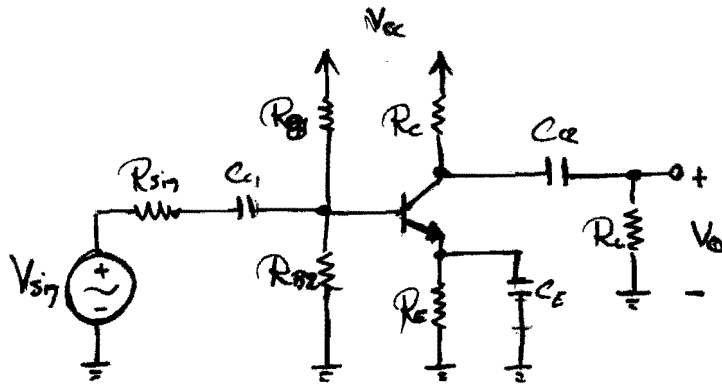


(11.1)

PROBLEM (10.38)

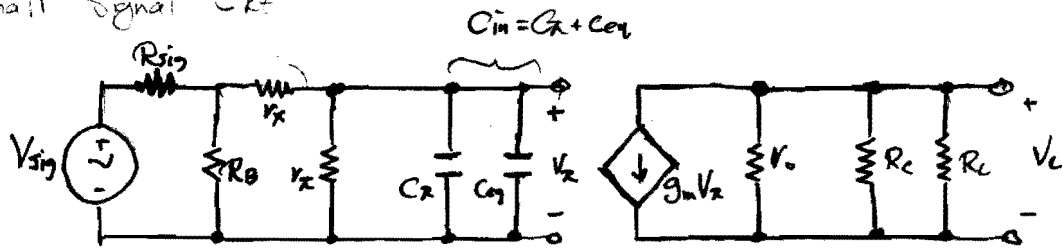

Small signal ckt



$$GB = |A_M| f_H = \beta \frac{R_i'}{R_{sig}} \frac{1}{2\pi C_{in} \beta R_i'} = \frac{1}{2\pi C_{in} R_{sig}} = \frac{1}{2\pi \times 1 \times 10^{-12} \times 25 \times 10^3} = 6.37 \text{ MHz}$$

for $I_c = 1 \text{ mA}$ and $\beta = 100$

(i) $R_i' = 25 \text{ k}\Omega$, $A_M = -\beta \frac{R_i'}{R_{sig}} = -100 \times \frac{25 \text{ k}}{25 \text{ k}} = -100 \text{ V/V}$

$$GB = |A_M| f_c \rightarrow f_c = \frac{GB}{|A_M|} = \frac{6.37 \text{ MHz}}{100} = 63.7 \text{ kHz}$$

(ii) $R_i' = 2.5 \text{ k}\Omega$, $A_M = -\beta \frac{R_i'}{R_{sig}} = -100 \times \frac{2.5 \text{ k}}{25 \text{ k}} = -10 \text{ V/V}$

$$f_c = \frac{GB}{|A_M|} = \frac{6.37 \text{ MHz}}{10} = 637 \text{ kHz}$$


if midband gain is unity

$$f_H = GB = 6.37 \text{ MHz}$$

This is obtained when R_i' is

$$1 = 100 \times \frac{R_i'}{25}$$

$$R_i' = 0.25 \text{ k} = 250 \Omega$$

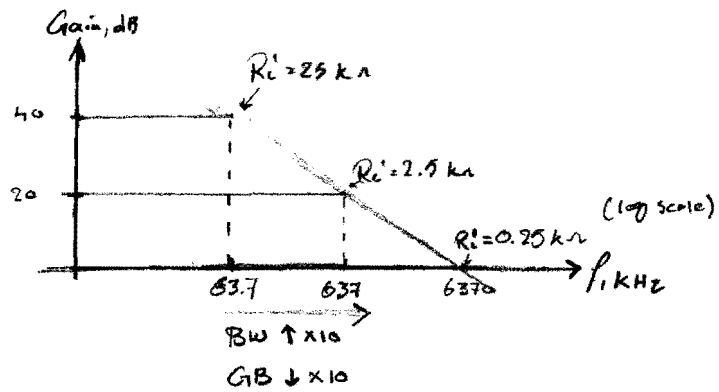

$GB = B$ is constant

11.2 PROBLEM (10.39)


$$R_{sig} = 10 \text{ k}\Omega, R_B = 68 \text{ k}\Omega, R_{B2} = 27 \text{ k}\Omega$$

$$R_C = 2.2 \text{ k}\Omega, R_E = 4.7 \text{ k}\Omega$$


$$\beta = 200, f_T = 1 \text{ GHz}$$

$$C_P = 0.8 \text{ pF},$$

$$I_C = 0.8 \text{ mA}$$

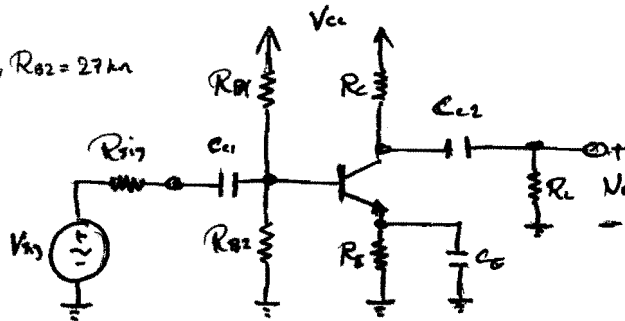

(Fig 10.9 (a))

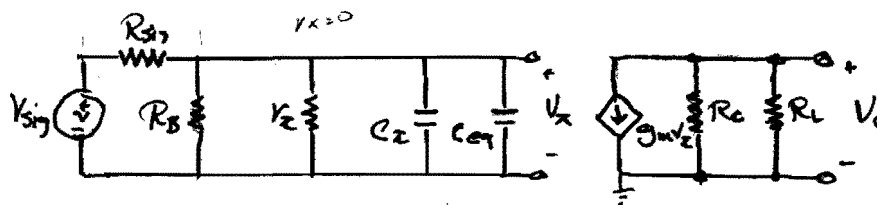

$$R_B = R_{B1} \parallel R_{B2} = 68 \text{ k}\Omega \parallel 27 \text{ k}\Omega = 19.3 \text{ k}\Omega$$

$$g_m = \frac{I_C}{V_T} = \frac{0.8 \text{ mA}}{0.025 \text{ V}} = 32 \text{ mA/V}$$

$$r_x = \frac{\beta}{g_m} = \frac{200}{32 \text{ mA/V}} = 6.25 \text{ k}\Omega$$

$$R_{sig} = r_x \parallel R_B \parallel R_{sig} = 6.25 \text{ k}\Omega \parallel 19.3 \text{ k}\Omega \parallel 10 \text{ k}\Omega = 3.2 \text{ k}\Omega$$

$$(10.54) \quad A_M = - \frac{R_B}{R_B + R_{sig}} \frac{r_x}{r_x + (R_{sig} \parallel R_B)} g_m R_L$$

when $r_x = 0$

$$= - \frac{19.3 \text{ k}}{19.3 \text{ k} + 10 \text{ k}} \frac{6.25 \text{ k}}{6.25 \text{ k} + (10 \text{ k} \parallel 19.3 \text{ k})} \times 32 \text{ mA/V} \times 3.2 \text{ k} = -32.8 \text{ V/V}$$

$$f_T = \frac{g_m}{2\pi(C_x + C_P)} \quad \text{--- } f_T \text{ given, solve for } (C_x + C_P) = \frac{g_m}{2\pi \cdot f_T} = \frac{32 \times 10^3}{2\pi \cdot 10^9}$$

$$\therefore (C_x + C_P) = 5.1 \text{ pF} \quad \text{--- with } C_P = 0.8 \text{ pF} \rightarrow C_x = 5.1 \text{ pF} - 0.8 \text{ pF} = 4.3 \text{ pF}$$

$$(10.58) \quad C_{in} = C_x + (g_m R_L + 1) C_P = 4.3 \text{ pF} + (32 \text{ mA/V} \times 3.2 \text{ k} + 1) \times 0.8 \text{ pF} = 87 \text{ pF}$$

$$(10.57) \quad f_H = \frac{1}{2\pi C_{in} R_{sig}} = \frac{1}{2\pi \times 87 \times 10^{-12} \times 3.2 \text{ k}} = 572 \text{ kHz}$$

11.3 PROBLEM (5.14)

$$t_{ox} = 6 \text{ nm}, \quad \mu_n = 460 \text{ cm}^2/\text{V}\cdot\text{s},$$

$$V_t = 0.5 \text{ V}, \quad W/L = 10, \quad C_{ox} = \frac{C_{ox}}{L_{ox}} \quad (5.3) \quad \rightarrow \epsilon_{ox} = 3.9 \epsilon_0$$

$$(5.12b) \quad k_n = \mu_n C_{ox} \frac{W}{L} = 460 \times 10^4 \times \frac{3.9 \times 8.854 \times 10^{-12}}{6 \times 10^{-9}} = 2.645 \text{ mA/V}^2$$

$$(a) \quad V_{GS} = 2.5 \text{ V} \quad \text{and} \quad V_{DS} = 1 \text{ V} \quad \rightarrow \quad V_{GS} > V_t \quad (2.5 > 0.5)$$

$$V_{OV} = V_{GS} - V_t = 2 \text{ V} \quad \rightarrow \quad V_{DS} < V_{OV} \quad \rightarrow \quad \text{triode region}$$

$$(5.16) \quad I_D = \underbrace{k_n \frac{W}{L}}_{= k_n} \left[V_{DS} V_{OV} - \frac{1}{2} V_{DS}^2 \right] = 2.645 \left[1 \times 2 - \frac{1}{2} \times 1 \right] = \underline{4 \text{ mA}}$$

Triode

(b)

$$V_{GS} = 2 \text{ V} \quad \text{and} \quad V_{DS} = 1.5 \text{ V} \quad \rightarrow \quad V_{GS} > V_t \quad (2 > 0.5)$$

$$V_{OV} = V_{GS} - V_t = 2 - 0.5 = 1.5 \text{ V}$$

$$\text{Thus, } V_{DS} = V_{OV} \rightarrow \text{Saturation region}$$

$$(5.20) \quad I_D = \frac{1}{2} k_n \left(\frac{W}{L} \right) \underbrace{(V_{GS} - V_t)^2}_{= V_o^2} = \frac{1}{2} \times 2.645 \times 1.5^2 = \underline{3 \text{ mA}}$$

(c)

$$V_{GS} = 2.5 \text{ V} \quad \text{and} \quad V_{DS} = 0.2 \text{ V} \quad \rightarrow \quad V_{GS} > V_t \quad (2.5 > 0.5)$$

$$V_{OV} = 2.5 - 0.5 = 2 \text{ V}$$

$$(5.16) \quad V_{DS} < V_{OV} \rightarrow \text{triode region}$$

$$I_D = k_n \left[V_{DS} V_{OV} - \frac{1}{2} V_{DS}^2 \right] = 2.645 \left[0.2 \times 2 - \frac{1}{2} \times 0.2^2 \right] = \underline{1 \text{ mA}}$$

(d)

$$V_{GS} = V_{DS} = 2.5 \text{ V} \quad \rightarrow \quad V_{GS} > V_t$$

$$V_{OV} = 2.5 - 0.5 = 2 \text{ V}, \quad \rightarrow \quad V_{DS} > V_{OV} \rightarrow \text{Saturation region}$$

$$(5.20) \quad I_D = \frac{1}{2} k_n V_{OV}^2 = \frac{1}{2} \times 2.645 \times 2^2 = \underline{5.3 \text{ mA}}$$

11.4 Problem (5.18)

$$V_{tn} = 0.5V, \quad \beta_n = 1.6 \text{ mA/V}^2 = k_n' \left(\frac{W}{L}\right), \quad I_D = 50 \mu\text{A}$$

$$(5.20) \quad I_D = \frac{1}{2} k_n' \left(\frac{W}{L}\right) \underbrace{(V_{gs} - V_t)^2}_{= V_{ov}^2} \Rightarrow 50 \mu\text{A} = \frac{1}{2} \times 1.6 \times 10^{-3} \times V_{ov}^2$$

$$\therefore V_{ov} = 0.25V \text{ and } V_{DS} \gg 0.25V$$

for saturation $V_{DS \min} = 0.25V$

at min V_{DS} :

$$V_{GS} - V_t = 0.25, \quad \rightarrow V_{GS} = V_t + 0.25 = \underline{0.75V}$$

for $I_D = 200 \mu\text{A}$

$$\text{Using (5.20)} \quad 200 \mu\text{A} = \frac{1}{2} \times 1.6 \times 10^{-3} \times V_{ov}^2 \rightarrow V_{ov} = 0.5 \text{ and } V_{DS} \gg 0.5$$

for saturation $V_{DS \min} = 0.5V$

at min V_{DS} :

$$V_{GS} - V_t = 0.5V \rightarrow V_{GS} = V_t + 0.25 = 0.5 + 0.5 = \underline{1V}$$

(1.5) Problem (5.21)

In triode region $V_{GS} > V_t$ & $V_{DS} < V_{GS} - V_t$

$$(5.16) \quad I_D = \underbrace{\mu_n \left(\frac{W}{L}\right)}_{K_n} \left[(V_{GS} - V_t)V_{DS} - \frac{1}{2}V_{DS}^2 \right]$$

$$\text{if } \frac{1}{2}V_{DS}^2 \ll (V_{GS} - V_t)V_{DS}$$

$$I_D \approx \mu_n (V_{GS} - V_t)V_{DS} \quad \text{"Linear resistance region"}$$

$$\text{case 1} \quad 25 \mu\text{A} = K_n (1 - V_t) \times 0.05 \quad \text{--- (1)}$$

$$\text{case 2} \quad 50 \mu\text{A} = K_n (1.5 - V_t) \times 0.05 \quad \text{--- (2)}$$

by dividing Eq (2) by Eq (1)

$$2 = \frac{1.5 - V_t}{1 - V_t} \quad \longrightarrow \quad \underline{V_t = 0.5 \text{ V}}$$

$$\text{Substituting } V_t \text{ in Eq. 1} \quad 25 \mu\text{A} = K_n \times 0.5 \times 0.05 \quad \longrightarrow \quad K_n = 1000 \mu\text{A/V}$$

$$\text{for } K_n = 50 \mu\text{A/V}^2 \quad \longrightarrow \quad \frac{W}{L} = 20$$

$$\text{For } V_{GS} = 2\text{V and } V_{DS} = 0.1\text{V} \quad \longrightarrow \quad \begin{array}{l} V_{GS} > V_t \\ (2 > 0.5) \end{array} \quad \& \quad \begin{array}{l} V_{GS} - V_t = 1.5 \\ \therefore V_{DS} < V_{GS} - V_t \end{array} \quad \longrightarrow \quad \text{triode}$$

$$(5.16) \quad \begin{aligned} I_D &= K_n \left[(V_{GS} - V_t)V_{DS} - \frac{1}{2}V_{DS}^2 \right] \\ &= 1 \left[(2 - 0.5) \times 0.1 - \frac{1}{2} \times 0.1^2 \right] = \underline{145 \mu\text{A}} \end{aligned}$$

$$\text{For } V_{GS} = 2\text{V, Pinch-off will occur for } V_{DS} = V_{GS} - V_t = 2 - 0.5 = 1.5\text{V}$$

the drain current will be

$$(5.20) \quad \begin{array}{l} \text{for saturation} \\ I_D = \frac{1}{2} K_n (V_{GS} - V_t)^2 = \frac{1}{2} \times 1 \times (2 - 0.5)^2 = \underline{1.125 \mu\text{A}} \end{array}$$

(11.6) PROBLEM (5.22)

$$V_{OS} \leq V_{AS} - V_t$$

$$\text{For } V_{AS} = 1.0V \text{ to } 1.8V \text{ and } V_t = 0.4V$$


$$\text{For max } V_{OS} \text{ use } V_{AS} = 1V$$

$$V_{OS} \leq 1 - 0.4 \quad \text{so } V_{OS|_{\max}} = \underline{0.6V}$$

(1.7)

PROBLEM (5.28)

$$V_t = 0.4V$$

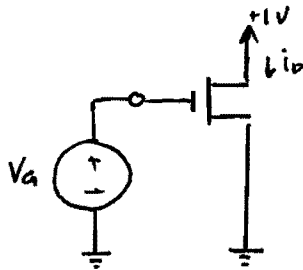

Cutoff - Saturation boundary is determined by $V_{GS} = V_t$

$\Rightarrow V_{GS} = 0.4V$ at the boundary

The Saturation - triode boundary is determined by

$$V_{GD} = V_t \quad \text{and} \quad V_{DS} = V_{DD} = 1V \quad \text{and since}$$


$$V_{GS} = V_{GD} + V_{DS}, \text{ one has}$$

$$V_{GS} = 0.4 + 1.0 = 1.4V \text{ at the boundary}$$

$$\text{Cutoff} \quad i_D \frac{L}{k_n' W} = 0 \quad 0 \leq V_{GS} \leq 0.4V$$

$$\text{Saturation} \quad i_D \frac{L}{k_n' W} = \frac{(V_{GS} - 0.4)^2}{2} \quad 0.4 \leq V_{GS} \leq 1.4V$$

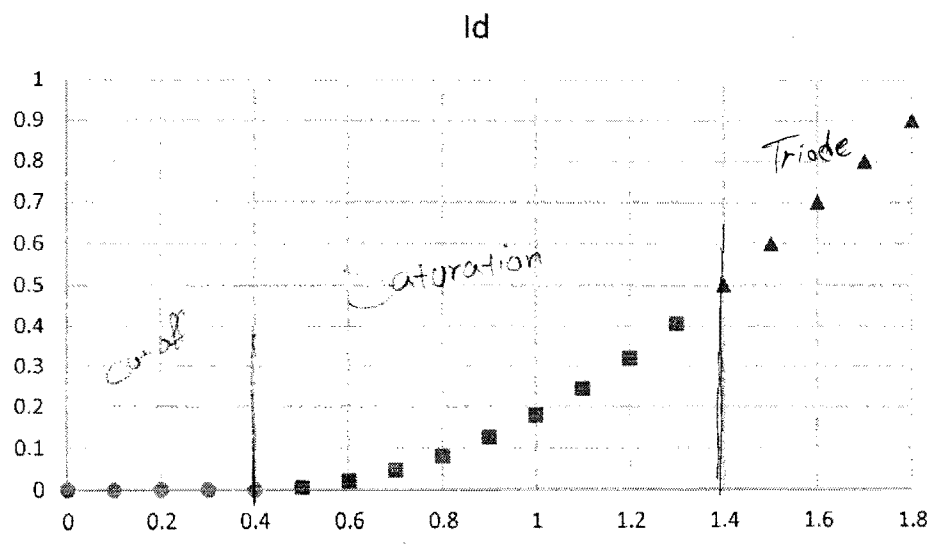
$$\text{Triode} \quad i_D \frac{L}{k_n' W} = V_{GS} - 0.9 \quad 1.4 \leq V_{GS} \leq 1.8V$$



11.8 Problem (5.41)

Refer to Table 5.2

And Lecture 27

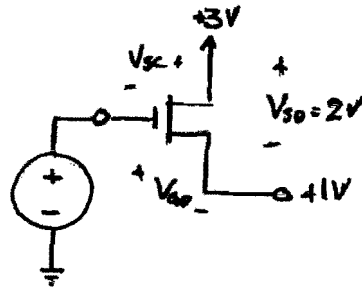

For induced channel

$$V_{GS} > |V_{th}|$$

$$= V_S - V_G = 3 - V_G \rightarrow V_G \text{ range from } 3 \text{ to } 0 \text{ V}$$

$$\bullet V_G \text{ from } 3 \rightarrow 2.5 \text{ V} : V_{GS} \leq |V_{th}| \quad \times^{10} \text{ Cutoff}$$

\bullet At $V_G = 2.5 \text{ V}$, $V_S - V_G = 3 - 2.5 > |V_{th}|$ \times has induce channel

$$\therefore V_{SD} = 3 - 1 = 2 \text{ V} \quad \# \quad V_{SD} > V_{GS} - |V_{th}| \rightarrow (2 > 0.5 - 0.5) \text{ Saturation}$$

As V_G decrease from 2.5V to 0.5V \times^{10} stay saturated


\bullet At $V_G = 0.5 \text{ V}$, $V_{GS} - |V_{th}| = 2 \text{ V} \therefore V_{SD}$ is no longer greater than $V_{GS} - |V_{th}|$

inside $V_{SD} \leq V_{GS} - |V_{th}|$ triode region

11.9-1) Problem (5.43).a

(a) $V_i = V_{DS} = V_{GS} = 1V$

After adding R

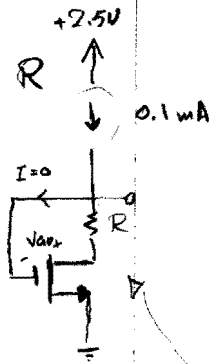


for saturation $V_{GD} \leq V_t$

$V_{GD} = I \cdot R \leq V_t$

$I \cdot R_{max} = V_t \rightarrow R_{max} = \frac{V_t}{I} = \frac{0.5V}{0.1mA} = 5k\Omega$


Now add R_s

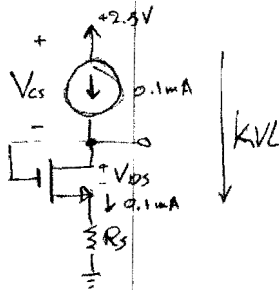


$2.5 = V_{GS} + V_{DS} + I R_{s,max}$

$2.5 = 0.5 + 1 + I R_{s,max}$

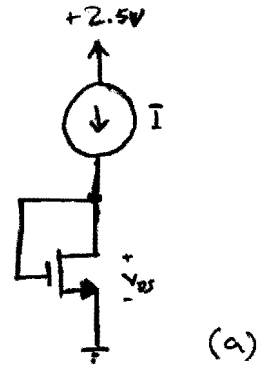$I R_{s,max} = 2.5 - 1.5 \rightarrow R_{s,max} = \frac{1V}{0.1mA} = 10k\Omega$




CONT (11.9) PROBLEM (5.43). C

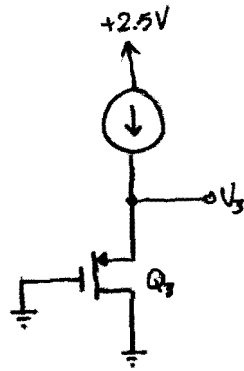

$$c) V_3 = V_{SD} = V_{SG} = 1V$$

Adding R

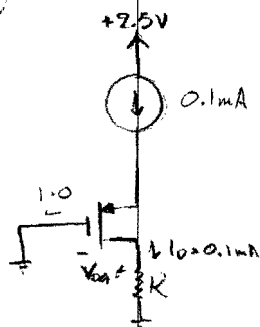


for saturation

$$V_{DG} \leq |V_{tp}|$$

$$I_D R = V_D - V_G \leq |V_{tp}|$$

$$I_{Dmax} = |V_{tp}| = 0.5 \rightarrow R$$

$$\therefore R_{max} = \frac{0.5V}{0.1mA} = \underline{5k\Omega}$$

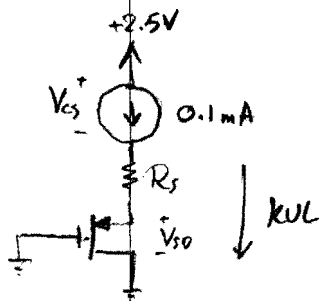Adding R_S 

by kvl

$$2.5 = V_{GS} + I R_S + V_{SD}$$


$$2.5 = 0.5 + I R_{Smax} + 1$$

$$I R_{Smax} = 2.5 - 0.5 - 1 = 1V$$

$$R_{Smax} = \frac{1V}{I} = \frac{1V}{0.1mA} = \underline{10k\Omega}$$

(11.10)

PROBLEM (5.44)

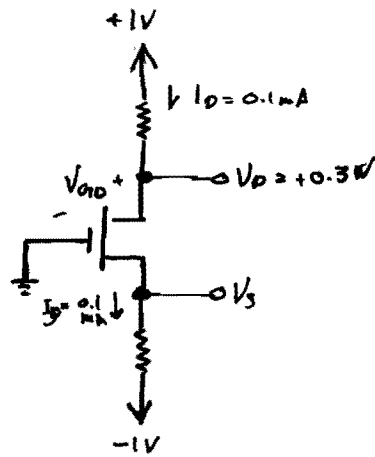

Assume $V_{GS} > V_t$ for induced
channel

Since $V_{GS} > 0$ the MOSFET is in saturation

CHECK
*

$$V_{GD} = V_G - V_D = 0 - 0.3 = -0.3V < V_t$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_{OV}^2$$

$$0.1 = \frac{1}{2} \times 0.4 \times \frac{5}{0.4} \times V_{OV}^2 \rightarrow V_{OV} = 0.2V$$

$$V_{GS} = V_t + V_{OV} = 0.5 + 0.2 = 0.7 \quad \text{CHECK} \quad * \quad V_{GS} = V_G - V_S = 0 - (-0.7) = 0.7 > V_t \text{ induced channel}$$

$$V_S = 0 - V_{GS} = -0.7V$$

$$R_S = \frac{V_S - (-1)}{I_D} = \frac{-0.7 + 1}{0.1mA} = 3k\Omega$$

$$R_D = \frac{1 - V_D}{I_D} = \frac{1 - 0.3}{0.1mA} = \frac{0.7}{0.1mA} = 7k\Omega$$