

## **EE 320 – *Electronics I***

### **Homework #12**

10 points

*Date Assigned:* 11/13

*Date Due:* 11/17

12.1 Text problem 7.25

12.2 Text problem 7.26 The amplifier circuit is shown in Fig. 7.4(a).

12.3 Text problem 7.30

12.4 Text problem 7.31

12.5 Text problem 7.33

12.6 Text problem 7.92

12.7 Text problem 7.97