

13.1 PROBLEM 7.103

$$I_D = \frac{1}{2} k_n' V_{ov}^2$$

$$1 \text{ mA} = \frac{1}{2} \times 8 \text{ mA/V}^2 \times V_{ov}^2$$

$$V_{ov} = \underline{0.5 \text{ V}}$$

When $v_o < V_{ov}$ ←

$$v_o = V_{ov} + 2$$

$$v_o = \underline{2.5 \text{ V}}$$

Since $|I_{G1}| \ll I_D$

$$R_{D1} \approx \frac{V_{DD} - v_o}{I_D} = \frac{5 - 2.5}{1} = \underline{2.5 \text{ k}\Omega}$$

$$V_{GS} = V_{t1} + V_{ov} = 0.8 + 0.5 = 1.3 \text{ V}$$

$$\text{So } V_{R_{G2}} = 1.3 \text{ V} \quad \text{and} \quad V_{R_{G1}} = 2.5 - 1.3 = 1.2 \text{ V}$$

that mean $R_{G2} > R_{G1}$ because $I_{G1} = I_{G2}$

$$\frac{V_D - V_{G1}}{R_{G1}} = \frac{V_{G1}}{R_{G2}} \rightarrow R_{G1} = R_{G2} \cdot \frac{V_D - V_{G1}}{V_{G1}}$$



$$R_{G1} = R_{G2} = \frac{2.5 - 1.3}{1.3} \quad \text{if } R_{G2} \text{ selected to be } 22 \text{ M}\Omega$$

$$\frac{R_{G1}}{R_{G2}} = \frac{1.2 \text{ V}}{1.3 \text{ V}}$$

$$R_{G1} = \underline{20.3 \text{ M}\Omega}$$

Specifying all resistors to two significant digits
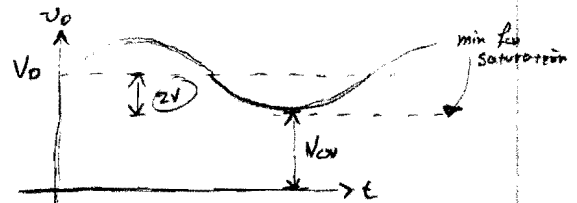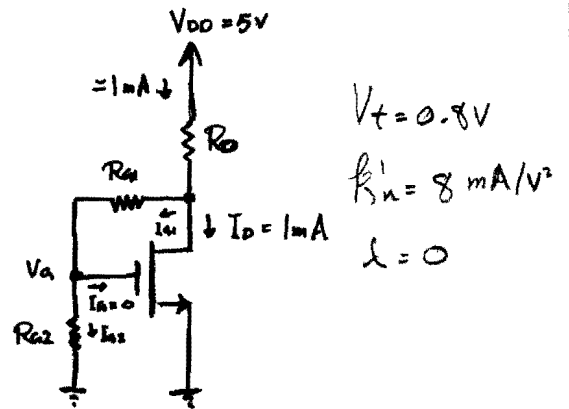
$$R_D = 2.5 \text{ k}\Omega, \quad R_{G1} = 20 \text{ M}\Omega, \quad R_{G2} = 22 \text{ M}\Omega$$



For Saturation $v_{GS} < V_{t1}$ or $v_{GS} - v_{DS} < V_{t1}$

$$v_o > v_{GS} - V_{t1} = V_{ov}$$

$$v_o \neq V_{ov} + 2$$

13.2 PROBLEM 7.121

(a)

$R_{in} \text{ at gate} = R_G = 10 \text{ M}\Omega$

$I_D = \frac{1}{2} K_n V_{ov}^2$

$0.4 = \frac{1}{2} \times 5 \text{ mA/V}^2 \times V_{ov}^2 \rightarrow \underline{V_{ov} = 0.4 \text{ V}}$

$V_G = 0 \rightarrow V_S = -V_{GS}$

where $V_{ov} = V_{GS} - V_t \therefore V_{GS} = V_{ov} + V_t$

$V_{GS} = V_t + 0.4 = 0.8 + 0.4 = \underline{1.2 \text{ V}} \rightarrow V_S = \underline{-1.2 \text{ V}}$

$R_S = \frac{-1.2 - (-5)}{0.4 \text{ mA}} = \underline{9.5 \text{ k}\Omega}$

For Saturation, minimum drain Voltage must be limited to $V_G - V_t = 0 - 0.8 = -0.8 \text{ V}$

so negative signal swing must have $V_D = 0 \text{ V}$

$R_D = \frac{5 - V_D}{I_D} = \frac{5 - 0}{0.4 \text{ mA}} = \underline{12.5 \text{ k}\Omega}$

(b)

$g_m = \frac{2I_D}{V_{ov}} = \frac{2 \times 0.4 \text{ mA}}{0.4 \text{ V}} = \underline{2 \text{ mA/V}}$



$r_o = \frac{V_A}{I_D} = \frac{40}{0.4} = \underline{100 \text{ k}\Omega}$

(c) if \bar{z} connected to ground, circuit become CS amplifier.

$A_{v0} = -\frac{V_y}{V_{sig}} = \frac{R_G}{R_G + R_{sig}} \times -g_m (r_o \parallel R_D \parallel R_L)$

$= -\frac{10 \text{ k}}{10 + 1 \text{ k}} \times 2 (100 \text{ k} \parallel 12.5 \text{ k} \parallel 10 \text{ k})$
 $= \underline{-9.6 \text{ V/V}}$

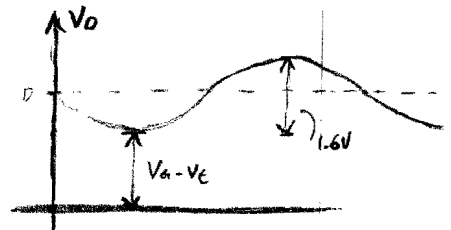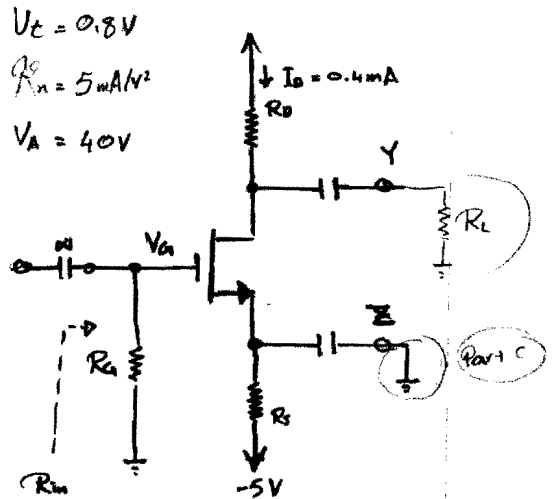
$V_t = 0.8 \text{ V}$
 $K_n = 5 \text{ mA/V}^2$
 $V_A = 40 \text{ V}$



In saturation $V_{GD} < V_t$

$V_G - V_D < V_t \rightarrow V_D > V_G - V_t \neq V_{ov}$
 $\therefore V_D > 0 - 0.8 + 0.8 = 0$

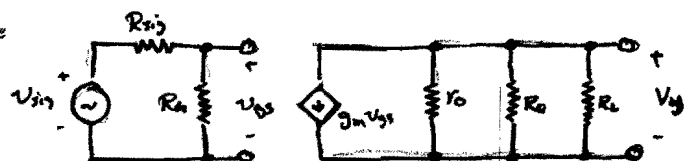because $V_{GS} \neq V_{GS}$ in this problem.



$V_y = -g_m V_{GS} (r_o \parallel R_D \parallel R_L)$

$V_{GS} = V_{sig} \cdot \frac{R_G}{R_G + R_{sig}}$

13.3 Problem 8.43

(a)

$$\bar{I}_D = 200 \mu\text{A}$$


$$I_D = \frac{1}{2} K_n' \left(\frac{W}{L}\right) V_{ov}^2$$

$$200 \mu\text{A} = \frac{1}{2} \times 2 \text{ mA/V}^2 \times V_{ov}^2$$

$$\text{Solve for } V_{ov} = \underline{0.45 \text{ V}}$$

$$V_{as} = V_L + V_{ov} = 0.5 + 0.45 = \underline{0.95 \text{ V}}$$

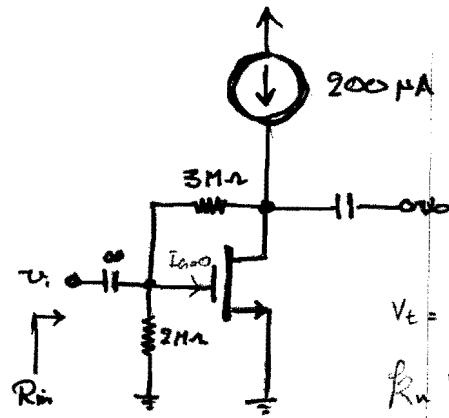
$$I_R = \frac{V_{as}}{2 \text{ M}} = 0.475 \mu\text{A} \quad \text{which is}$$



$$V_L = 0.5 \text{ V}$$

$$K_n' \frac{W}{L} = 2 \text{ mA/V}^2$$

$$V_A = 20 \text{ V}$$

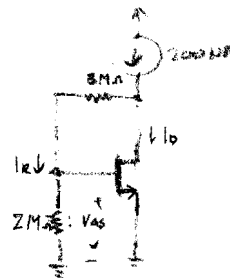(b) Replacing the MOSFET with its hybrid- π

A KCL equation at the output node yields

$$\frac{v_o}{r_o} + g_m v_{gs} + \frac{v_o - v_i}{R_{a2}} = 0, \quad \text{where } v_{gs} = v_i$$

$$v_o \left(\frac{1}{r_o} + \frac{1}{R_{a2}} \right) = -v_i \left(g_m - \frac{1}{R_{a2}} \right)$$

$$\frac{v_o}{v_i} = - \left(g_m - \frac{1}{R_{a2}} \right) (r_o \parallel R_{a2})$$


$$g_m = \frac{2I_D}{V_{ov}} = \frac{2 \times 0.2}{0.45} = 0.894 \text{ mA/V}$$

$$r_o = \frac{V_A}{I_D} = \frac{20}{0.2} = 100 \text{ k}\Omega$$

$$\frac{v_o}{v_i} = - \left(0.894 - \frac{1}{3000} \right) \times (100 \parallel 3000) = \underline{-86.1 \text{ V/V}}$$

to obtain maximum negative signal swing, first determine the dc voltage at the output

$$V_o = I_R (2 \text{ M}\Omega + 3 \text{ M}\Omega) = 0.475 \mu\text{A} \times 5 \text{ M}\Omega = \underline{2.375 \text{ V}}$$

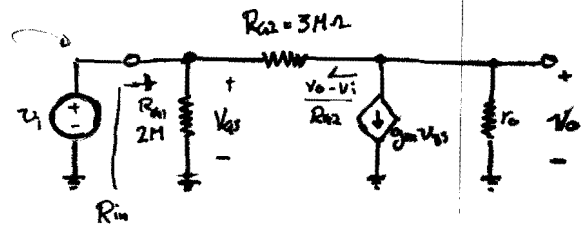

Cont. 13.3 Cont PROBLEM 8.43

$$V_{GD} \leq V_t \rightarrow V_G - V_D \leq V_t \text{ or } V_D \geq V_G - V_t$$

The MOSFET in Saturation limit $V_{D|\min} = -V_G - V_t$

↑
max abs

$$V_{G|\max} = 0.5 + V_{D|\min}$$


$$V_{GS} + |\hat{v}_i| = 0.5 + V_{DS} - |\hat{v}_o|$$

$$0.95 + \frac{|\hat{v}_o|}{|A_v|} = 0.5 + 2.375 - |\hat{v}_o|$$


$$|\hat{v}_o| = \frac{0.5 + 2.375 - 0.95}{1 + \frac{1}{|A_v|}}$$

Substituting $|A_v| = 86.5 \rightarrow |\hat{v}_o| = \underline{1.9V}$

$$|v_i| = \frac{|\hat{v}_o|}{|A_v|} = \frac{1.9}{86.5} = \underline{22mV}$$

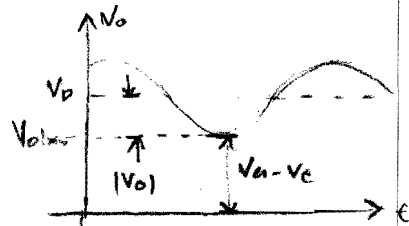

13.4 Problem 8.44

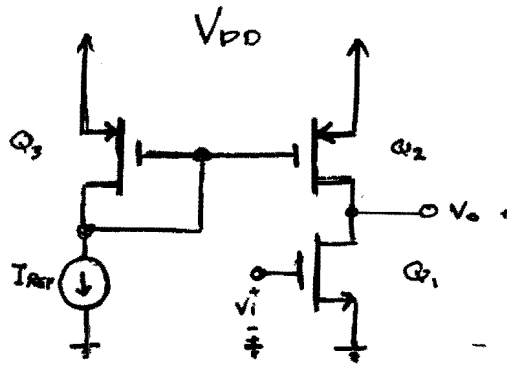

$$I_{D1} = I_{D2}$$

$$R_o = 100 \text{ k}\Omega = r_{o1} \parallel r_{o2}$$

$$r_{o1} = r_{o2} = \frac{|V_A|}{I_D} = \frac{5}{I_{REF}}$$

$$100 \text{ k} = \frac{1}{2} \times \frac{5}{I_{REF}}$$

$$-V_o = -g_{m1} V_{gs1} (r_{o1} \parallel r_{o2})$$

$$V_{gs1} = V_i$$

$$A_V = \frac{V_o}{V_i} = -g_{m1} (r_{o1} \parallel r_{o2})$$

$$\text{given } -40 = -g_{m1} \times 100 \longrightarrow g_{m1} = 0.4 \text{ mA/V}$$

but

$$g_{m1} = \sqrt{\frac{\mu_n C_{ox}}{2} \left(\frac{W}{L}\right)_1 I_{D1}} \quad I_{REF}$$

$$0.4 \text{ mA/V} = \sqrt{2 \times 0.4 \left(\frac{W}{L}\right)_1 \times 0.025} \implies \left(\frac{W}{L}\right)_1 = 8$$

$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 V_{ov1}^2$$

$$25 = \frac{1}{2} \times 400 \times 8 \times V_{ov1}^2 \longrightarrow V_{ov1} = 0.125 \text{ V}$$

if \$Q_2\$ and \$Q_3\$ are operated at \$|V_{ov}| = 0.125 \text{ V}\$


$$I_{D2} = I_{D3} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_{2,3} |V_{ov}|^2$$

$$= \frac{1}{2} \times 100 \times \left(\frac{W}{L}\right)_{2,3} \times 0.125^2$$

$$\left(\frac{W}{L}\right)_{2,3} = 32$$

13.5

PROBLEM 8.45

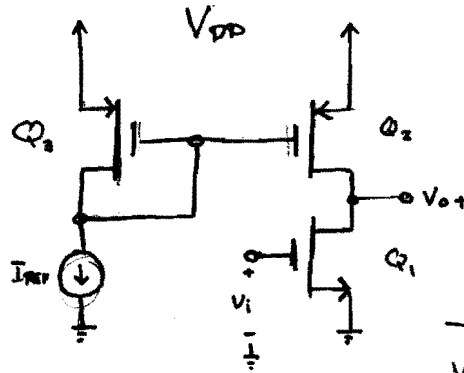

From 8.16(d)

in Region III is almost linear region of transfer characteristic.

$$V_{IA} = 0.89 \text{ V and } V_{IB} = 0.935 \text{ V}$$


A Maximum output signal swing is achieved by biasing Q_1 at middle of this range

$$V_{I1} = \frac{V_{IA} + V_{IB}}{2} = 0.913 \text{ V}$$


The Peak to Peak amplitude at the output will be

$$(V_{OA} - V_{OB}) = 2.47 - 0.335 = \underline{2.135 \text{ V}}$$
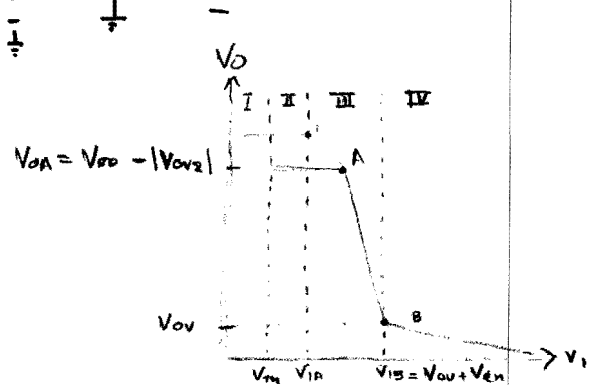
$$\text{Peak amplitude} = \frac{1}{2} (2.135) = \underline{1.07 \text{ V}}$$



13.6 Ex 8.8

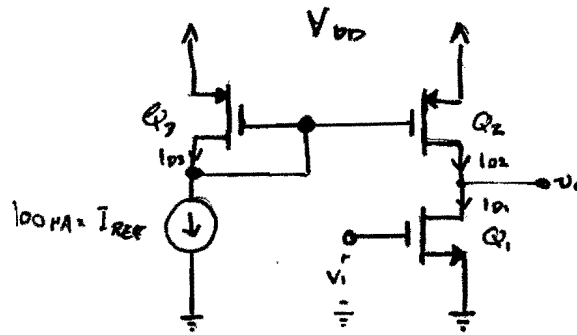

Since Q_2 and Q_3 have the same $\frac{W}{L}$ and R_F so $I_{D3} = I_{D2} = I_{REF}$ and

$$I_{D1} = I_{D2} = I_{REF} = 100 \mu\text{A}$$


$$\frac{W}{L} = \frac{7.2 \mu\text{m}}{0.36 \mu\text{m}}$$

From (7.41) $g_{m1} = \sqrt{2K_n' \left(\frac{W}{L}\right) \sqrt{I_{D1}}}$

$$= \sqrt{2 \cdot (387 \mu\text{A/V}^2) \left(\frac{7.2}{0.36}\right) (100 \mu\text{A})} = \underline{1.24 \text{ mA/V}}$$

From (7.37) $r_{O1} = \frac{|V_{AN}'| L_1}{I_{D1}} = \frac{5 \text{ V}/\mu\text{m} (0.36 \mu\text{m})}{0.1 \text{ mA}} = \underline{18 \text{ k}\Omega}$

$$r_{O2} = \frac{|V_{DP}'| L_2}{I_{D2}} = \frac{6 \text{ V}/\mu\text{m} (0.36 \mu\text{m})}{0.1 \text{ mA}} = \underline{21.6 \text{ k}\Omega}$$

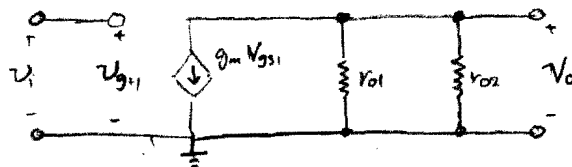


$$v_O = -g_{m1} v_{gs1} \cdot (r_{O1} \parallel r_{O2}), \quad v_{gs1} = v_i$$

$$\therefore A_V = \frac{v_O}{v_i} = -g_{m1} (r_{O1} \parallel r_{O2})$$

$$= - (1.24 \text{ mA/V}) (18 \text{ k}\Omega \parallel 21.6 \text{ k}\Omega)$$

$$= \underline{-12.2 \text{ V/V}}$$

13.7 Problem 8.52

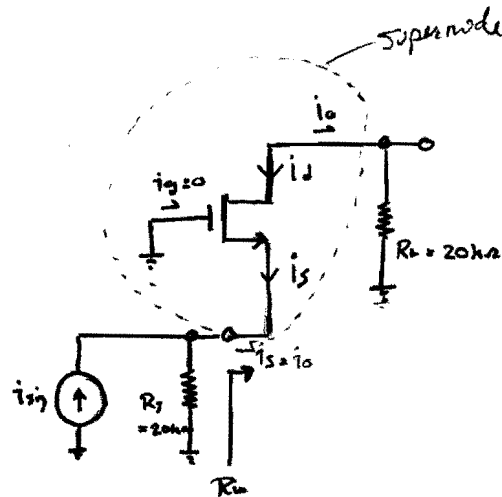

CG Amplifiers

$$g_m = 2 \text{ mA/V}$$

$$r_o = 20 \text{ k}\Omega$$

From (8.53)

$$R_{in} = \frac{r_o + R_L}{1 + g_m r_o} = \frac{20\text{k} + 20\text{k}}{1 + 2 \text{ mA/V} \times 20\text{k}} = \underline{980 \Omega}$$

Since $i_s = i_o$ From Supermode

$$\frac{i_o}{i_{sig}} = \frac{R_s}{R_s + R_{in}} = \frac{20\text{k}}{20\text{k} + 980} = \underline{0.95 \text{ A/A}}$$

if R_L is increase by factor of 10, $R_{in} = \frac{20\text{k} + 200\text{k}}{1 + 2 \text{ mA/V} \times 20\text{k}} = \underline{5.37 \text{ k}\Omega}$

and current gain become

$$\frac{i_o}{i_{sig}} = \frac{20\text{k}}{20\text{k} + 5.37} = \underline{0.79 \text{ A/A}}$$

When R_L increase by factor of 10, current gain decrease, by -17%. This indicates that the CG amplifier function as an effective current buffer.