

EE 320 – Electronics I


Homework #14

10 points

Date Assigned: 11/27


Date Due: 12/4

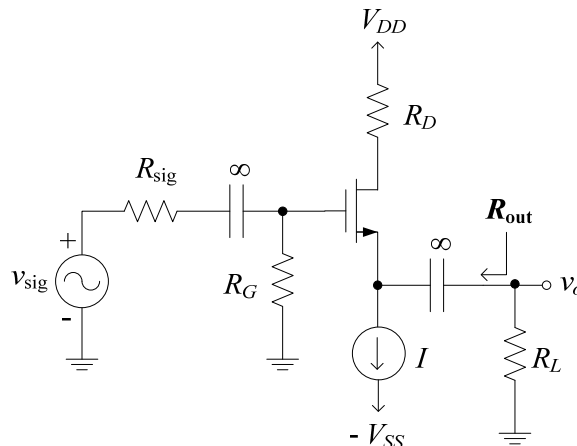- 14.1 Text problem 7.120
- 14.2 Text problem 7.121 Parts (d) and (e) only.
- 14.3 Determine an algebraic expression for the small-signal AC output resistance R_{out} of the amplifier shown below. What is the value of R_{out} for the component values used in Example N36.1 in the notes? Comment on the efficacy of the bypass capacitor used in Example N36.1.



- 14.4 Consider a CG amplifier for which $k_n' = 160 \mu\text{A}/\text{V}^2$, $\lambda = 0.1 \text{ V}^{-1}$, $W/L = 50 \mu\text{m}/0.5 \mu\text{m}$, $\chi = 0.2$, $I = 0.5 \text{ mA}$, and $R_L = R_{sig} = r_o$. Calculate g_m , g_{mb} , r_o , R_{out} , R_{in} , A_v , and G_v . If the amplifier is instead fed by a current source i_{sig} having a source (Norton) impedance $R_{sig} = r_o$, calculate G_i .
- 14.5 In the CG amplifier shown below, Q_2 and Q_3 are matched, $k_n'(W/L)_n = k_p'(W/L)_p = 4 \text{ mA}/\text{V}^2$, and all transistors have $|V_t| = 0.8 \text{ V}$ and $|V_A| = 20 \text{ V}$. Transistor Q_1 has $\chi = 0.2$. The input v_{sig} is a small sinusoidal signal with no DC component.
- Neglecting the effects of V_A , calculate the DC drain current of Q_1 and the required value of V_{BIAS} .
 - Determine the values of g_{m1} , g_{mb1} , and r_o for all transistors.

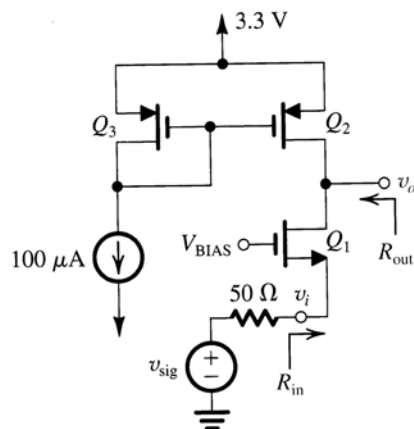- (c) Determine the value of R_{in} .
- (d) Determine the value of R_{out} .
- (e) Calculate the voltage gains A_v and G_v .
- (f) Calculate how large v_{sig} can be (peak-to-peak) while maintaining saturation mode operation for Q_1 and Q_2 .



14.6 Text problem 14.24

14.7 Text exercise 14.6

14.8 Text exercise 14.7

14.9 Text problem 14.31