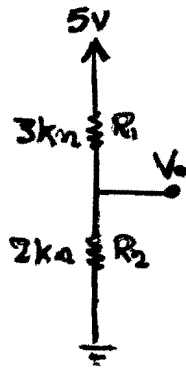


PROBLEM 1.7

Using Voltage divider

With exact values:


$$V_o = \frac{R_2}{R_1 + R_2} \cdot V_i$$

$$= \frac{2000}{3000 + 2000} \times 5V = \underline{\underline{2V}}$$

With 5% tolerance, one time with  $(R_1 + 5\%$  and  $R_2 - 5\%)$  for  $V_{min}$   
and another time with  $(R_1 - 5\%$  and  $R_2 + 5\%)$  for  $V_{max}$

$$V_{min} = \frac{2000(0.95)}{3000(1.05) + 2000(0.95)} = \underline{\underline{1.881V}}$$

$$V_{max} = \frac{2000(1.05)}{3000(0.95) + 2000(1.05)} = \underline{\underline{2.121V}}$$

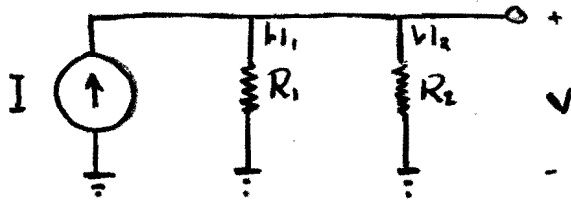Problem 1.10

$$V = I \cdot R_{eq}$$

$$R_{eq} = (R_1 \parallel R_2)$$

$$= \frac{R_1 \times R_2}{R_1 + R_2}$$


$$V = I \cdot \frac{R_1 \times R_2}{R_1 + R_2}$$

Voltage across two Resistor is the same so.


$$I_1 = V \cdot \left(\frac{1}{R_1}\right) = I \cdot \frac{R_1 \times R_2}{R_1 + R_2} \times \frac{1}{R_1} = I \cdot \frac{R_2}{R_1 + R_2}$$

$$I_2 = V \cdot \left(\frac{1}{R_2}\right) = I \cdot \frac{R_1 \times R_2}{R_1 + R_2} \times \frac{1}{R_2} = I \cdot \frac{R_1}{R_1 + R_2}$$


Problem 1.14

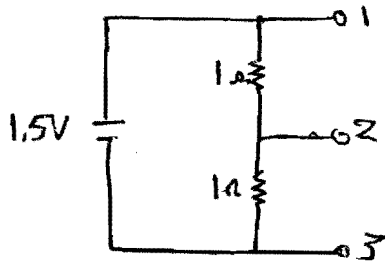


Thevenin Theorem

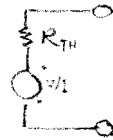

Ⓐ 1 AND 2

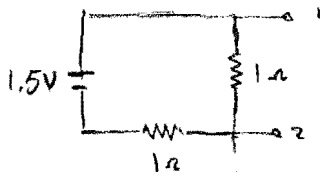


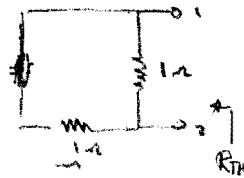To find  $R_{TH}$ , Short the Voltage Source





$$R_{TH} = (1 \parallel 1) = \frac{1 \cdot 1}{1+1} = 0.5 \Omega$$

$$V_{1,2} = 1.5 \cdot R_{TH} = 0.75 V$$

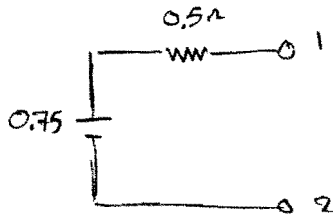



Ⓑ 2 AND 3

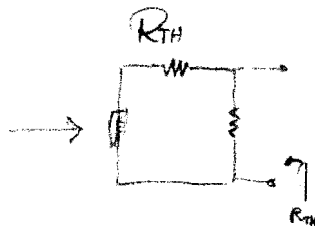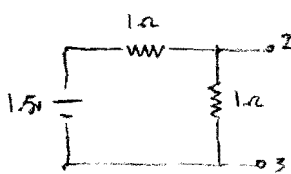

$$R_{TH} = \frac{1 \cdot 1}{1+1} = 0.5 \Omega$$


$$V_{TH} = 1.5 \cdot R_{TH} = 0.75 V$$

Ⓒ 1 AND 3

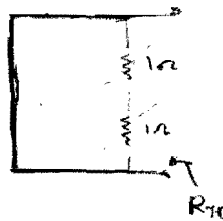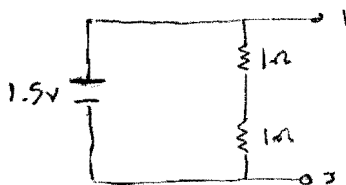


$R_{TH} = 0 \Omega$ , When we Short Voltage Source, the Resistors get Shorted


$$V_{TH} = 1.5 V$$

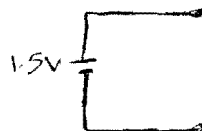


Problem 1.15

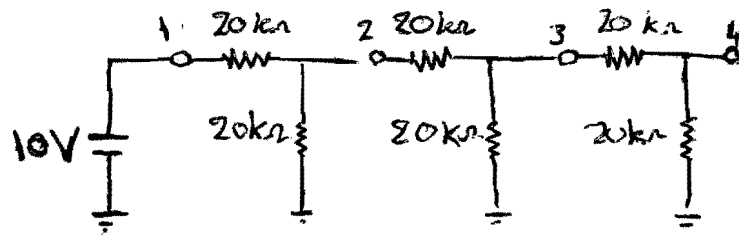

② and ground

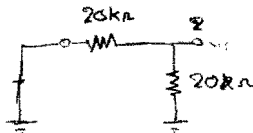

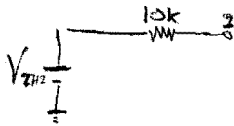
$$R_{TH2} = (20k \parallel 20k) = \frac{20k \times 20k}{20k + 20k} = 10k\Omega$$




$$V_{TH2} = 10 \cdot \frac{20k}{20k + 20k} = 5V$$

(Voltage divider)


③ and ground

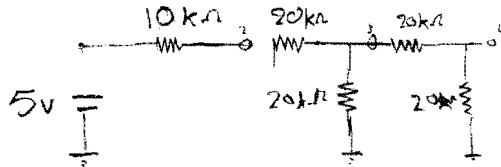

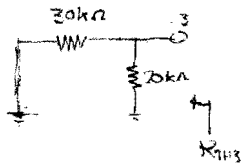
$$R_{TH3} = (30k\Omega \parallel 20k\Omega) = \frac{30k \times 20k}{30k + 20k} = 12k\Omega$$



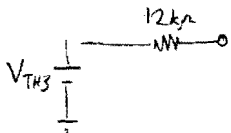
$$V_{TH3} = 5 \cdot \frac{20k}{30k + 20k} = 2V$$



④ ADD Ground

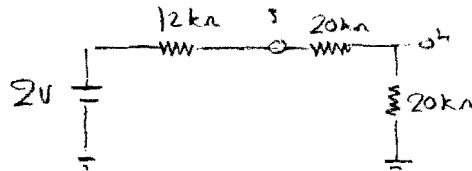

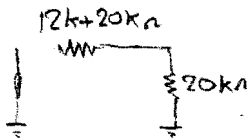
$$R_{TH4} = (32k\Omega \parallel 20k\Omega) = \frac{32k \times 20k}{32k + 20k} = 12.31k\Omega$$



$$V_{TH4} = 2 \cdot \frac{20k}{32k + 20k} = 0.769V$$

Node ④ + 3kΩ

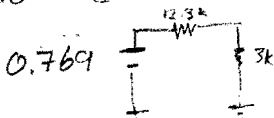


$$I = 0.769 \times \frac{1}{12.31k + 3k} = 0.0503mA$$

Problem 1.17

$I_5 = ?$

$V_5 = ?$

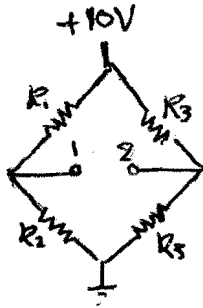

$R_1 = 1 \text{ k}\Omega$



$R_2 = 1.2 \text{ k}\Omega$

$R_3 = 9.1 \text{ k}\Omega$


$R_4 = 11 \text{ k}\Omega$

$R_5 = 2 \text{ k}\Omega$

TH (1)

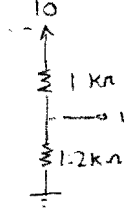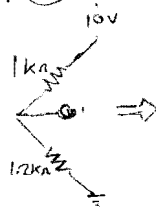





TH

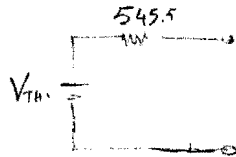

$R_{TH1} = \frac{1 \text{ k} \times 1.2 \text{ k}}{1 \text{ k} + 1.2 \text{ k}} = 545.5 \Omega$


$V_{TH1} = 10 \cdot \frac{1.2 \text{ k}}{1 \text{ k} + 1.2 \text{ k}} = 5.455 \text{ V}$

TH (2)

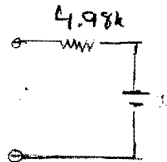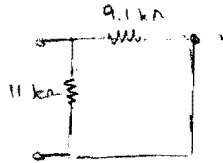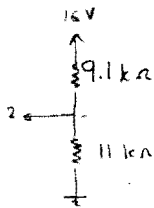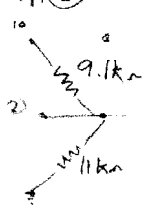

$R_{TH2} = \frac{9.1 \text{ k} \cdot 11 \text{ k}}{9.1 \text{ k} + 11 \text{ k}} = 4.98 \text{ k}\Omega$

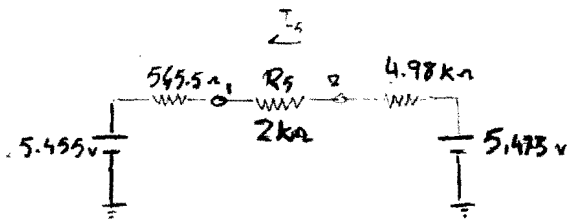$V_{TH2} = 10 \cdot \frac{11 \text{ k}}{9.1 \text{ k} + 11 \text{ k}} = 5.473 \text{ V}$



$I_5 = \frac{5.473 - 5.455}{545.5 + 2 \text{ k} + 4.98 \text{ k}} = 2.404 \mu\text{A}$

$V = I \cdot R_5 = 4.808 \text{ mV}$