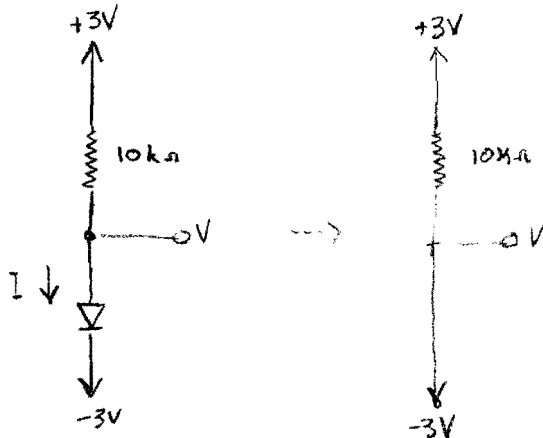


PROBLEM 4.2


(a)



$$V = \underline{-3V}$$

$$I = \frac{3 - (-3)}{10k} = \underline{0.6 \text{ mA}}$$


(b)

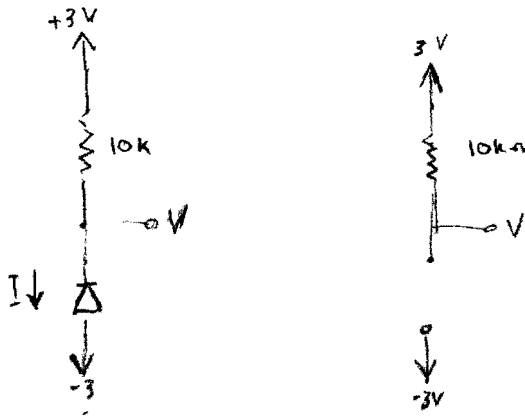

$$V = \underline{3V}$$

$$I = \underline{0 \text{ A}}$$


(c)

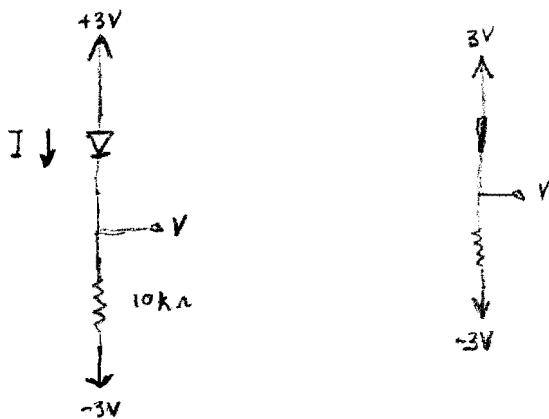

$$V = \underline{3V}$$

$$I = \frac{3 - (-3)}{10k} = \underline{0.6 \text{ mA}}$$

(d)


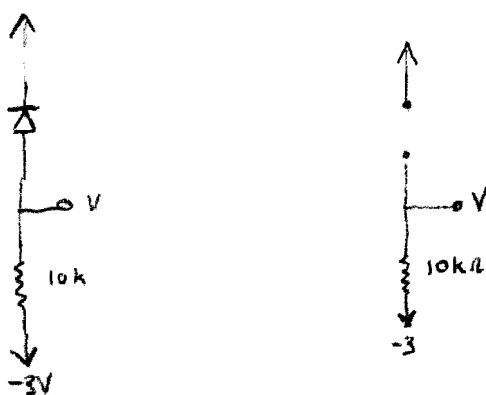


$$V = \underline{-3V}$$

$$I = \underline{0 \text{ A}}$$

## PROBLEM 4.3

(a)

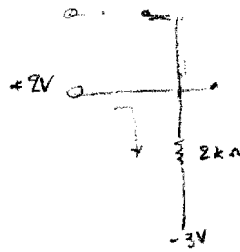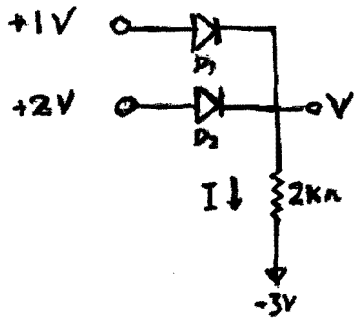



$$\frac{2 - (-3)}{2 \text{ k}\Omega} > \frac{1 - (-3)}{2 \text{ k}\Omega}$$

So  $D_1$  is CutoffAND  $D_2$  is Conducting

$$V = \underline{2V}$$

$$I = \frac{2 - (-3)}{2 \text{ k}} = \underline{2.5 \text{ mA}}$$

(b)

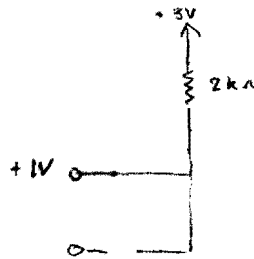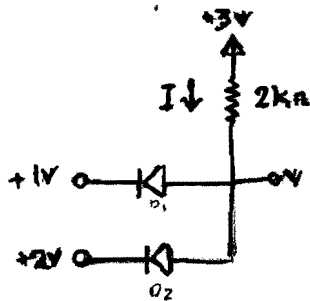

$$V = \underline{1V}$$


 $D_1$  is Conducting

$$I = \frac{3 - 1}{2 \text{ k}} = \underline{1 \text{ mA}}$$

 $D_2$  is Cutoff


Problem 4.4  $V_i$  is 1 kHz, 1 V<sub>peak</sub> Sin wave

(a)

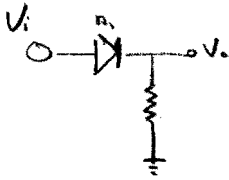

$V_{p+} = 5V$


$V_{p-} = 0V$

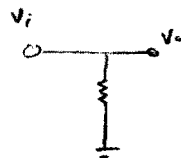



When  $V_i > 0$




When  $V_i < 0$

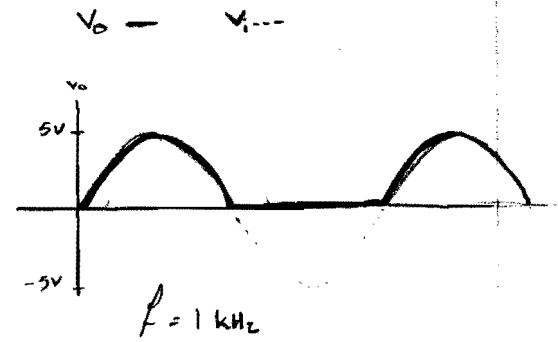


(b)

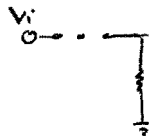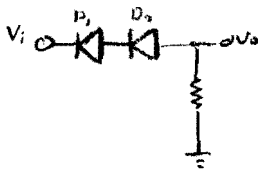



$V_{p+} = 0V$

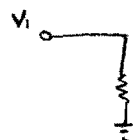


$V_{p-} = -5V$

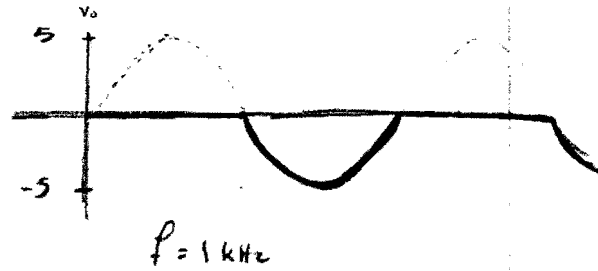


(c)

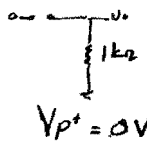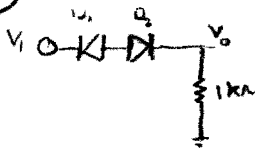



$V_{p+} = 0V$

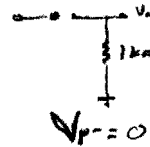

$V_{p-} = 0V$

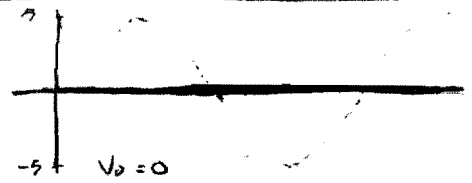


(d)

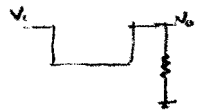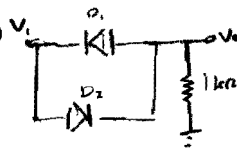


$V_{p+} = 5V$




$V_{p-} = -5V$

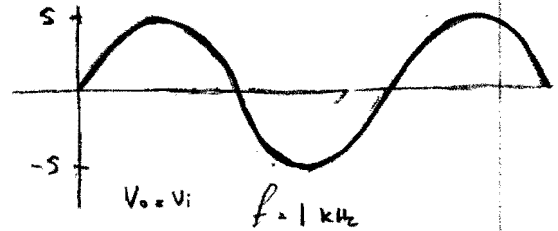


(e)

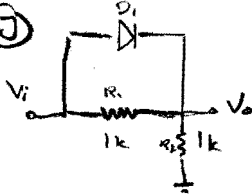

$V_{p+} = 5V$

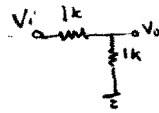


$V_{p-} = V_i \frac{R_2}{R_1 + R_2} = -2.5V$

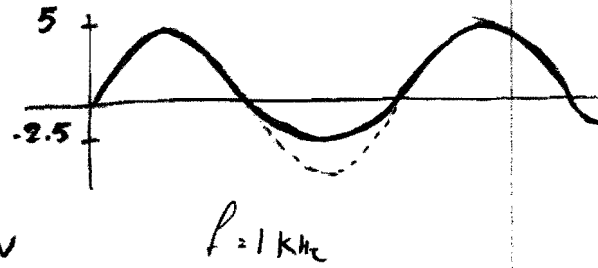


PROBLEM 4.9

(a)

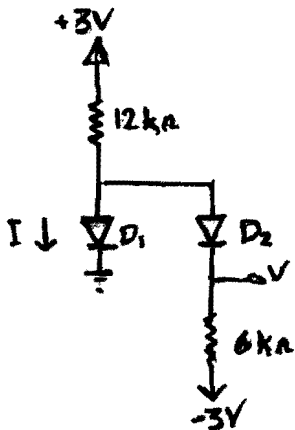

if we assume that both  $D_1$  and  $D_2$  are conducting

then

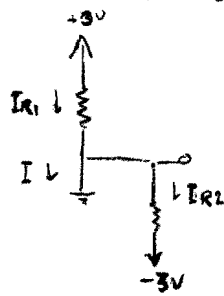

$$V_o = 0V$$


$$I_{R2} = \frac{0 - (-3)}{6k\Omega} = 0.5mA$$

$$I_{R1} = \frac{3 - 0}{12k\Omega} = 0.25mA$$


making  $I = -0.25mA$

and that is not right, because current

can't be generated from ground!

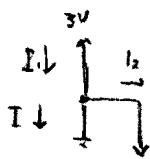

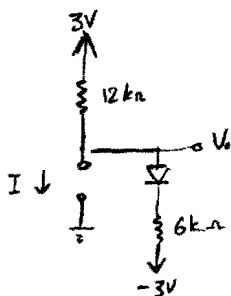if  $D_1$  is conducting and  $D_2$  is off





$$I = 0, \quad I_{R1} = I_{R2} = 0.33mA$$

$$V_o = 3 \times \frac{6}{12+6} + (-3) \times \frac{12}{12+6}$$



$$= -1V$$

$$I = 0$$

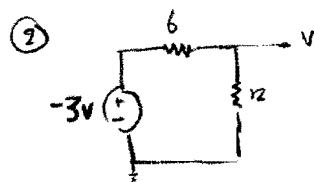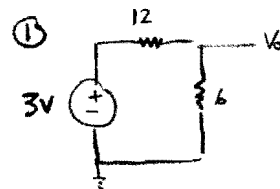

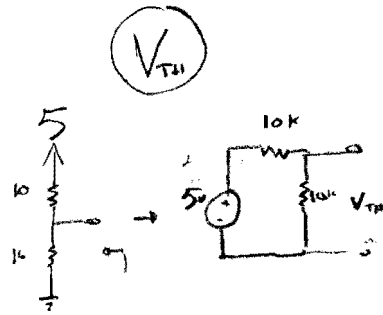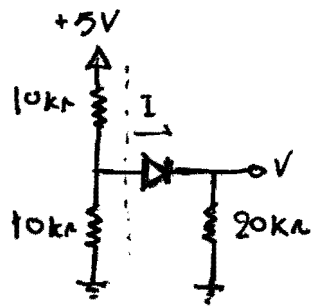
## PROBLEM 4.10 .a


Utilize Thevenin's theorem to simplify the circuits


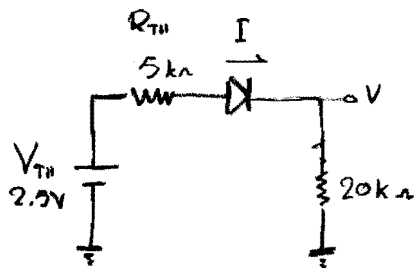
$$V_{TH} = 5 \times \frac{10}{10 + 10} = \underline{2.5V}$$



$R_{TH}$

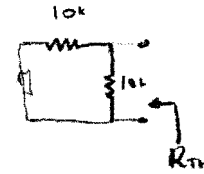

$$R_{TH} = (10 // 10) = \frac{10 \times 10}{10 + 10} = \underline{5k\Omega}$$

$$I = \frac{2.5V}{5k + 20k} = \underline{0.1mA}$$

$$V = 0.1 \times 20 = \underline{2V}$$

## Problem 4.19

A diode for which the forward voltage drop is 0.7V at 1mA is operated at 0.5V. What is the value of the current?

$$V_0 = 0.7V$$

$$V_2 - V_1 = nV_T \ln\left(\frac{I_2}{I_1}\right) \Rightarrow \frac{I_2}{I_1} = e^{\frac{V_2 - V_1}{nV_T}}$$

(4.1)

$$I_1 = I_s e^{0.7/V_T} = 10^{-3}$$

$$I_2 = I_s e^{0.5/V_T}$$

$$0.5 - 0.7 = n(25mV) \ln\left(\frac{I_2}{10^{-3}}\right) \Rightarrow$$

$$\left(\frac{-0.2}{25mV}\right) = \ln\left(\frac{I_2}{10^{-3}}\right)$$

$$e^{\frac{-0.2}{0.025}} = I_2/10^{-3}$$

$$I_2 = \underline{0.3355 \mu A}$$

← Very small, as expected,

$$\text{For } 0.65V \text{ ; } n=1, \quad \frac{I_2}{I_1} = e^{\frac{V_2 - V_1}{nV_T}}$$

$$\text{or } I_2 = I_1 e^{\frac{V_2 - V_1}{nV_T}} = 0.001 e^{\frac{0.65 - 0.7}{1.25 \times 10^{-3}}}$$

$$I_2 = \underline{0.135 mA}$$

↑ much larger than 0.3355 μA, but still not approaching 1 mA yet. Just 0.05V more forward bias and current will increase substantially.

## Problem 4.23

Three identical diodes  $I_s = 10^{-14} \text{ A}$ , find  $I$  required to obtain an  $V_0 = 2.0 \text{ V}$ .

if current of  $1 \text{ mA}$  is drawn away from the output terminal by load what is the change in output voltage.


So  $V_0 = 2 \rightarrow V_0 = V_D/3 = 0.6667 \text{ V}$

(4.1)

$$I_D = I_s e^{V_D/V_T} \quad I_s = 10^{-14} \text{ Saturation current}$$

$$V_T = 25 \text{ mV Thermal Voltage}$$
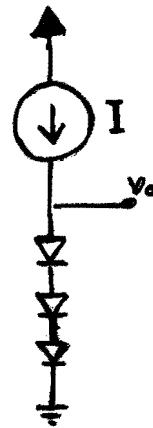
$$I_D = 10^{-14} \times e^{\frac{(2/3)}{25 \times 10^{-3}}} = 0.00386 \text{ A OR } \underline{3.812 \text{ mA}}$$



$$I_{D_{\text{new}}} = I_D - 1 \text{ mA} = 2.812 \text{ mA}$$

$$2.812 = 10^{-14} e^{\frac{V_D}{25 \text{ mV}}} \quad (x 10^{14})$$


$$\ln(2.812 \times 10^{14}) = \frac{V_{D_{\text{new}}}}{25 \text{ mV}}, \quad V_{D_{\text{new}}} = \ln(2.812 \times 10^{14}) \times \frac{25}{1000} = 0.6591 \text{ V}$$

$$V_{0_{\text{new}}} = 3 \times V_D = \underline{1.977 \text{ V}}$$

$$\text{Change in } V_0 = 1.977 - 2 = \underline{-22 \text{ mV}}$$
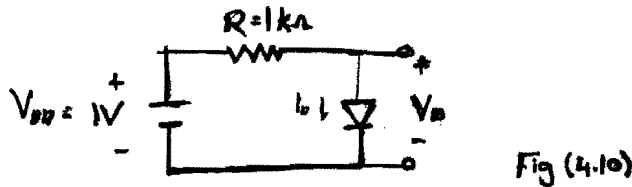
## Problem 4.35

Find  $I_D$  and  $V_D$  of diode using iterative-analysis  $V_{DD} = 1V$ ,  $R = 1k\Omega$   
and  $I_S = 10^{-15} A$



$$I_S = 10^{-15} A = 10^{-12} mA$$

Use the

$$\textcircled{1} V_D = 0.7V, \quad I_D = \frac{1 - 0.7}{1k} = 0.3mA$$

$$\textcircled{2} V_D = V_T \ln\left(\frac{I_D}{I_S}\right) = 0.025 \ln\left(\frac{0.3}{10^{-12}}\right) = 0.66067V$$

$$I_D = \frac{1 - 0.6607}{1k} = 0.3393 mA$$

$$\textcircled{3} V_D = 0.025 \ln\left(\frac{0.3393}{10^{-12}}\right) = 0.66375V$$

$$I_D = \frac{1 - 0.66375}{1k} = 0.3362 mA$$

$$\textcircled{4} V_D = 0.025 \ln\left(\frac{0.3362}{10^{-12}}\right) = 0.6635V$$

$$I_D = \frac{1 - 0.6635}{1k} = 0.3365 mA$$

$$\textcircled{5} V_D = 0.025 \ln\left(\frac{0.3365}{10^{-12}}\right) = 0.6635V$$

```
in[72]= ClearAll[VDD, R, IS, n, VD, Vt, ID]
```

```
VDD := 1.
```

```
R := 1000.
```

```
IS := 10-15
```

```
n := 1.
```

```
Vt := 0.025
```

```
FindRoot[{{ID == IS Exp[VD/(n Vt)], ID == (VDD - VD)/R}, {{VD, 0.7}, {ID, 0.001}}]
```

```
Out[78]= {VD -> 0.663543, ID -> 0.000336457}
```

using Mathematica

← exact answers.