

① PROBLEM 3.1'

From the graph below

when $i_D = 10 \mu A$, $V_D = 0.8V$

when $i_D = 1 \mu A$, $V_D = 0.7V$

$$\text{slope} = \frac{10 - 1}{0.8 - 0.7} = \underline{\underline{90 \text{ mA/V}}}$$


$$r_D = \frac{1}{\text{slope}} = \frac{1}{90 \times 10^{-3}} = \underline{\underline{11.11 \Omega}}$$

$$i_D = \frac{V_D - V_{D0}}{r_D} \Rightarrow V_{D0} = V_D - r_D \cdot i_D$$

$$V_{D0} = 0.8 - (11.11)(10 \times 10^{-3}) = \underline{\underline{0.6889V}}$$

$$\begin{aligned} V_D &= V_{D0} + i_D r_D \\ \Rightarrow V_{D0} &= V_D - i_D r_D \end{aligned}$$


close to plot

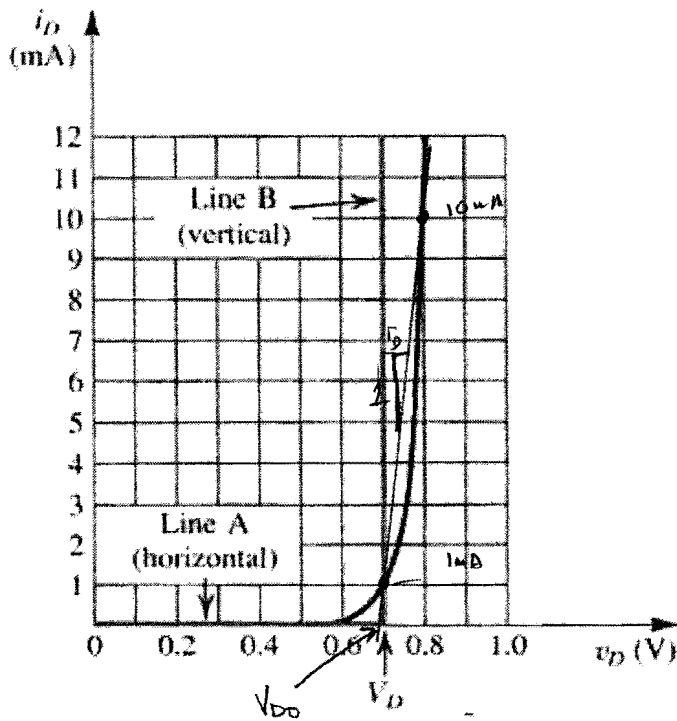

② Problem 3.2'

From Fig. 1 on Lecture 3 note, draw the load line corresponding to an external circuit consisting of a 0.9V Voltage source and a 100Ω Resistor. Calculate the diode Voltage and the loop current, Using

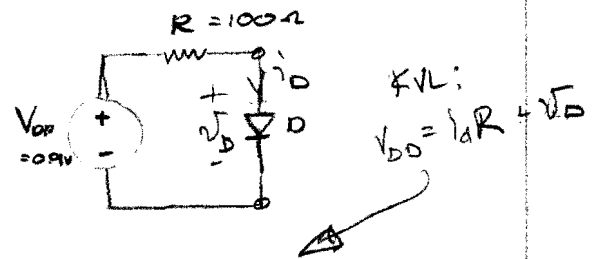- Ⓐ the actual diode characteristics
- Finding the intersection between the load line and the exponential curve.




Slope = $\frac{1}{100\Omega}$, load line: $i_D = I_D \left(\frac{1}{R} \right) + \frac{V_{DD}}{R}$, $i_D(V_{D=0}) = \frac{V_{DD}}{R} = \frac{0.9}{100} = 9\text{mA}$

$V_D \approx \underline{0.73}$ $I_D \approx \underline{1.7\text{mA}}$

- Ⓑ the two-segment model shown

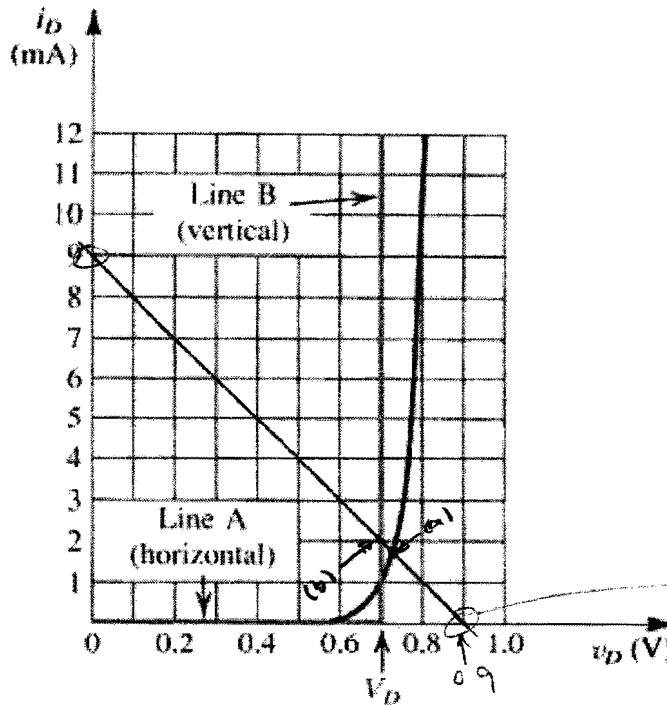Finding the intersection between the load line and vertical line




$V_D \approx \underline{0.7\text{V}}$
 $I_D = \underline{2.0\text{mA}}$
 $V_{DD} = I_D R + V_D$
 When $I_D = 0 \Rightarrow V_D = V_{DD} = 0.9\text{V}$

③ Problem 3.3'

Calculate r_D and V_{D0} the elements of the battery plus - resistor model for which the straight line intersects the diode exponential characteristic at $0.1 \times$ and $10 \times$ the specified diode current:

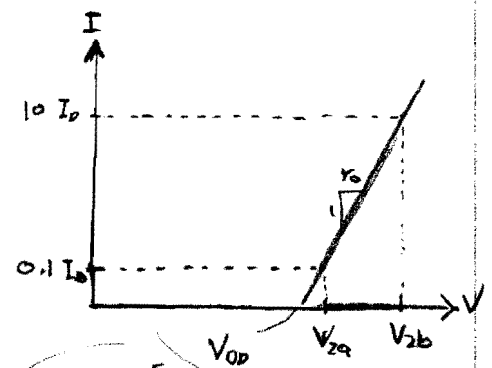Given: the straight line intersects the diode exponential curve at $0.1 \times$ and $10 \times$ the specified diode current.



x Using (7.5)

$$V_2 - V_1 = 2.3 n V_T \log_{10} \left(\frac{I_2}{I_1} \right)$$

$$V_2 = 2.3 n V_T \log_{10} \left(\frac{I_2}{I_1} \right) + V_1$$

$$I_D = I_S e^{\frac{V_D}{nV_T}}$$

$$\frac{I_1}{I_2} = e^{\frac{V_1 - V_2}{nV_T}} \Rightarrow \ln \left(\frac{I_1}{I_2} \right) = \frac{V_1 - V_2}{nV_T}$$

$$V_1 - V_2 = nV_T \ln \left(\frac{I_1}{I_2} \right)$$

$$V_2 = V_1 + nV_T \ln \left(\frac{I_2}{I_1} \right)$$

For $0.1 \times$

$$I_D = 0.1 I_0, I_1 = I_0, I_2 = i_0, V_1 = 0.7 \text{ V}$$

$$V_{2a} = 2.3 (0.025) \log_{10} \left(\frac{0.1 I_0}{I_0} \right) + 0.7 = \underline{0.6425 \text{ V}}$$

For $10 \times$

$$I_D = 10 I_0, I_1 = I_0, I_2 = i_0, V_1 = 0.7 \text{ V}$$

$$V_{2b} = 2.3 (0.025) \log_{10} \left(\frac{10 I_0}{I_0} \right) + 0.7 = \underline{0.7575 \text{ V}}$$

Since

(i) V_{2a} and V_{2b} are independent of I_0

(ii) $V_p = 0.7$ and $n = 1$ in Part a, b, and c.

(iii) the same relation ($0.1 \times$ and $10 \times$) are needed for Part a, b, and c.

③ Cont. Problem 3.3'

$$r_D = \left[\frac{I_D(10-0.1)}{V_{2b} - V_{2a}} \right]^{-1} = \frac{0.115}{9.9} \left(\frac{1}{I_D} \right)$$

$$\underline{r_D = \frac{0.01162}{I_D}}$$

$$\begin{aligned} V_{20} &= V_D - I_D r_D = V_{2a} - 0.1 I_D \left(\frac{0.01162}{I_D} \right) \\ &= 0.6425 - 0.1 (0.01162) \\ &= \underline{0.6413 \text{ V}} \end{aligned}$$

V_{20} independent of I_D
So it will be the same
for part a, b and c.


$$\textcircled{a} \quad r_D = \frac{0.01162}{0.001} = \underline{11.62 \Omega}$$

$$\textcircled{b} \quad r_D = \frac{0.01162}{1} = \underline{0.01162 \Omega}$$

$$\textcircled{c} \quad r_D = \frac{0.01162}{10 \times 10^{-6}} = \underline{1.162 \text{ k}\Omega}$$

4) Problem 4.40

(a)

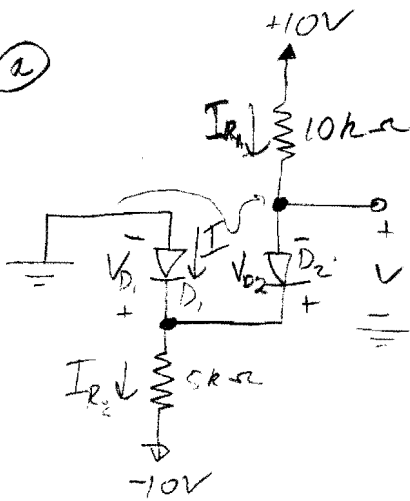

Refer to Example 4.2

Find the value of I and V in the circuits
Assume $V_D = 0.65V$ If both D_1 and D_2 are conducting

$$I_{R1} = \frac{10 - V}{10k} = \frac{10 - (+0.65 - 0.65)}{10k} = \underline{\underline{1mA}}$$

$$V = 0V$$


$$V_{D1} = V_{D2} = \underline{\underline{-0.65V}}$$

$$I_{R2} = \frac{-0.65 - (-10)}{5k} = \underline{\underline{1.87mA}}$$

$$\underline{\underline{I}} = 1.87 - 1 = \underline{\underline{0.87mA}}$$

4) cont. problem 4.40

⑥ Now, interchange the two resistors and reanalyze:

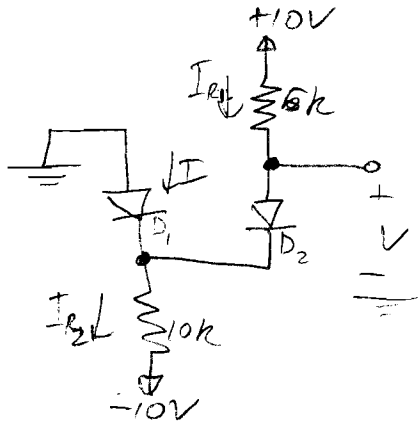Both D_1 and D_2 conducting

$$V = 0V$$

$$I_{R_1} = \frac{10 - 0}{5k} = 2mA$$

$$V_{D_1} = V_{D_2} = -0.65V$$


$$I_{R_2} = \frac{-0.65 + 10}{10k} = 0.935mA$$

$$I = I_{R_2} - I_{R_1} = -1.065mA$$



not correct assumption,
current needs to be positive

Assume D_1 cut off D_2 conducting

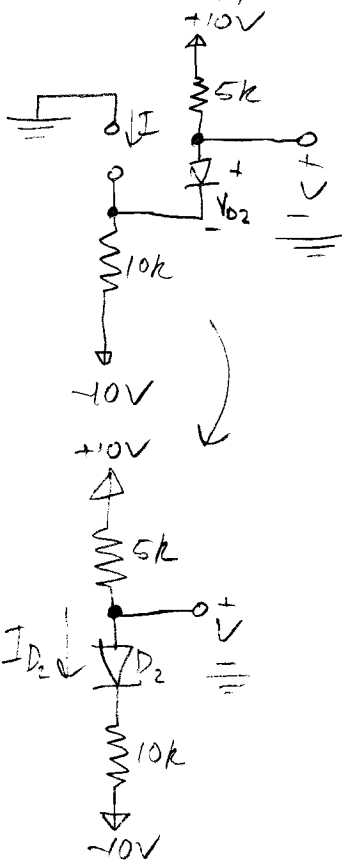



$$I = 0V$$

$$V_{D_2} = 0.65V$$

$$I_{D_2} = \frac{10 - (0.65) - (-10)}{10k + 5k} = 1.29mA$$



$$V = -10 + 1.29(10) + 0.65 = 3.55V$$

5) Problem 4.42

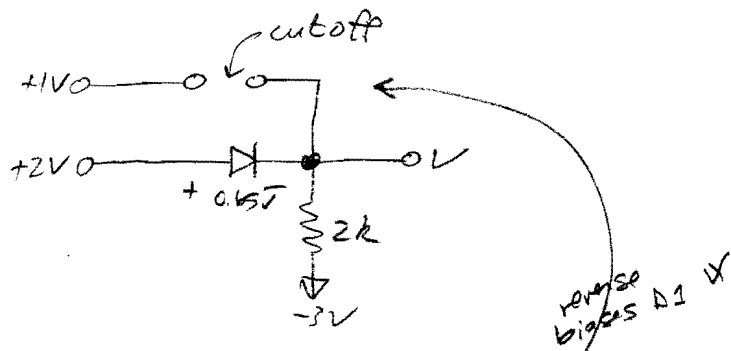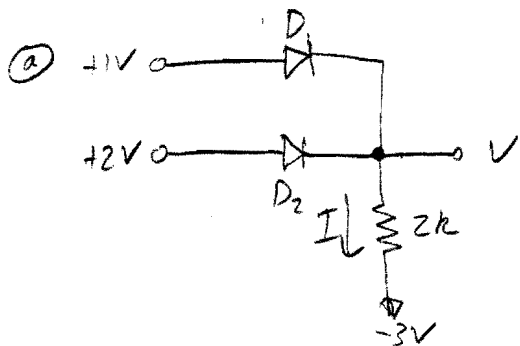

$$V = 2 - 0.65 = \underline{\underline{1.35V}}$$

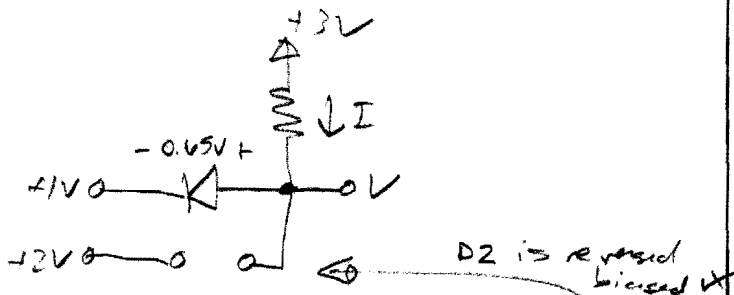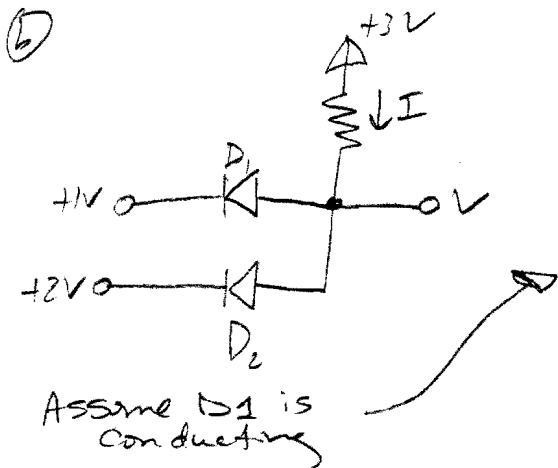
$$I = \frac{1.35 - (-3)}{2k} = \underline{\underline{2.175mA}}$$



$$V = 1 + 0.65V = \underline{\underline{1.65V}}$$


$$I = \frac{3 - 1.65}{2k} = \underline{\underline{0.675mA}}$$

⑥ Problem 4.48

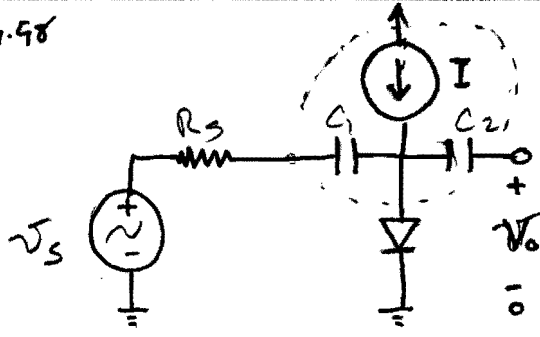

block the dc current from flowing into the signal source or the load.

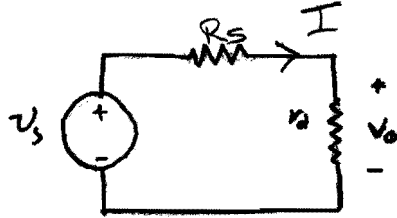Small-signal equivalent ckt (for $r_{e1}, r_{e2} \rightarrow 0$)



$$r_d = \frac{nV_T}{I_D}$$

$$v_o = v_s \times \frac{r_o}{r_o + R_s} = v_s \frac{\frac{nV_T}{I}}{\frac{nV_T}{I} + R_s} = v_s \frac{nV_T}{nV_T + IR_s}$$


w/ $n=1$
$$v_o = 10 \text{ mV} \times \frac{25 \text{ mV}}{25 \text{ mV} + I \times 10^3}$$

Solve v_o , by using given I values (mA)

$I = 1 \text{ mA}, v_o = 0.24 \text{ mV}$

$I = 0.1 \text{ mA}, v_o = 2.0 \text{ mV}$

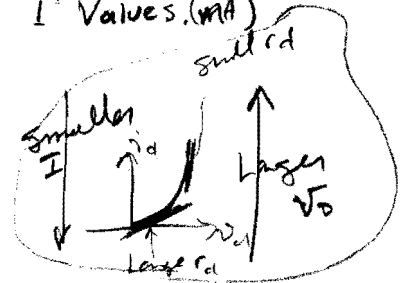$I = 1 \text{ } \mu\text{A}, v_o = 9.6 \text{ mV}$



Signal attenuator controlled by I_{DC} .

v_s cancel, solve for I .

when $v_o = \frac{1}{2} v_s = v_s \times \frac{0.025}{0.025 + I \times 10^3}$

$\Rightarrow I = \underline{25 \text{ } \mu\text{A}}$

⑦ Problem 4.59

From Fig. 4.19 $V_{ZK} \approx V_{Z0}$ and I_{ZK} is very small

$$V_Z = V_{Z0} + I_Z r_Z$$

① $r_Z = 2\Omega$, $V_Z = 6.8V$, $V_{ZK} = 6.6V$. Find I_{ZT}

$$6.8 = 6.6 + I_{ZT} \times 2$$

$$I_{ZT} = 0.1A \rightarrow$$

For power rating, choose $I = 2 \cdot I_{ZT} = 2mA$

$$\text{Then, } V_Z = 6.6 + 0.2 \times 2 = 7V$$

$$P = 7 \times 0.2 = 1.4W$$

② $V_Z = 18V$, $I_{ZT} = 5mA$, $V_{ZK} = 17.6V$. Find r_Z

$$r_Z = \frac{V_Z - V_{Z0}}{I_{ZT}} = \frac{18 - 17.6}{5mA} = 80\Omega$$

For power rating
at $I = 2I_{ZT}$
new

$$I_Z = 2 \times I_{ZT} = 0.01A$$

$$V_Z = 17.6 + 0.01 \times 80 = 18.4V$$

$$P = 18.4 \times 0.01 = 184 \text{ mW}$$

③ Given $I_{ZT} = 200mA$, $V_Z = 7.5V$, $r_Z = 1.5\Omega$ Find V_{Z0}

$$7.5 = V_{Z0} + 0.2 \times 1.5$$

$$V_{Z0} = 7.2V$$

For power rating
at $I = 2I_{ZT}$
 $= 2 \cdot 0.2$
 $= 0.4A$



$$I_Z = 2 \times I_{ZT} = 0.4A$$

$$V_Z = 7.2 + 0.4 \times 1.5 = 7.8V$$

$$P = 7.8 \times 0.4 = 3.12W$$

① PROBLEM 4.61
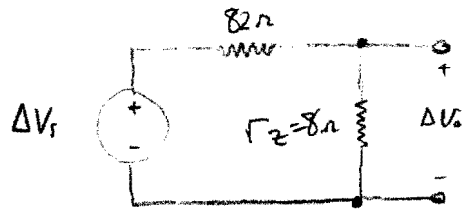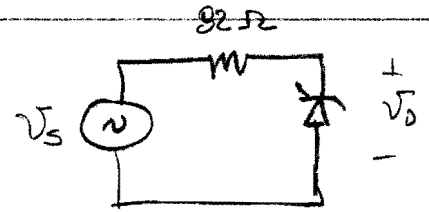
$$r_z = 8\ \Omega, \quad \Delta V_S = 1.0\text{V}$$



$$\frac{\Delta V_0}{\Delta V_S} = \frac{8}{8+82} = \frac{8}{90}$$

$$\Delta V_S = 1.0\text{V} \rightarrow \Delta V_0 = \frac{8}{90} \times \Delta V_S = \underline{\underline{0.0889\text{V}}}$$