

① PROBLEM 4.63


$$V_Z = 7.5V \quad \text{goal!}$$

Diode 7.5V at 10mA

$$r_Z = 30\Omega, \quad I_{ZK} = 0.5mA$$

$$V_S = 10 \pm 10\%$$

$$R_L = 1.5k\Omega$$

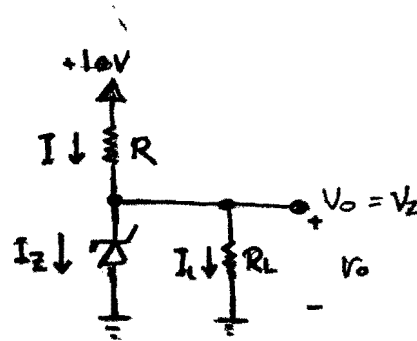

$$I_L = \frac{V_O}{R_L} = \frac{7.5}{1.5} = 5mA, \quad I = I_Z + I_{R_L} = 10mA + 5mA = \underline{15mA}$$

$$R = \frac{10 - 7.5}{15 \times 10^{-3}} = \underline{166.7\Omega}$$

When the supply change ΔV_S , the change in the output voltage ΔV_O can be determined from

$$\frac{\Delta V_O}{\Delta V_S} = \frac{(R_L || r_Z)}{(R_L || r_Z) + R} = \frac{1.5k || 30}{(1.5k || 30) + 166.7} = 0.15$$

$$\text{For } V_S = 10 + 1 \text{ (10\% high)}, \quad V_O = V_O + 0.15V = \underline{7.65V}$$

$$\text{For } V_S = 10 - 1 \text{ (10\% less)}, \quad V_O = V_O - 0.15V = \underline{7.35V}$$

When the load is removed and $V_S = 11V$

$$V_Z = V_{Z0} + I_Z r_Z$$


$$7.5 = V_{Z0} + 0.01 \times 30$$

$$V_{Z0} = \underline{7.2V}$$

$$I = \frac{11 - 7.2}{166.7 + 30} = \underline{19.32\mu A}$$

$$V_O = V_{Z0} + I \cdot r_Z$$
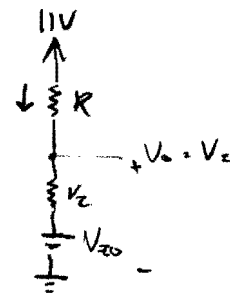
$$= 7.2 + (19.32 \times 10^{-3}) \times 30 = \underline{7.78V}$$



① Cont. PROBLEM 4.63

to determine the smallest allowable value

of R_L while $V_S = 9V$


$$V_Z = V_{Zk} \approx V_{Z0} = \underline{7.2V}$$

$$I = \frac{9 - 7.2}{166.7} = 10.8 \mu A$$

$$I_L = I - I_Z = \underline{10.3 \mu A}$$

$$R_L = \frac{V_o}{I_L} = \frac{7.2}{10.3} = 666.7 \Omega$$

$$V_o = \underline{7.2V}$$

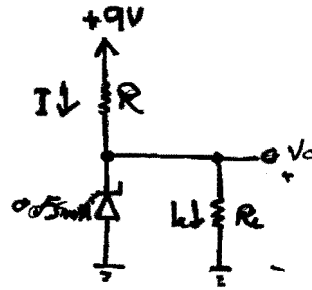

② PROBLEM 4.64

$$V_Z = 6.8 \text{ V}, r_Z = 5 \Omega \text{ for } I_Z = 20 \text{ mA}, \text{ at } I_Z = 0.25 \text{ mA} \quad r_Z = 750 \Omega$$


For both designs $V = 9 \text{ V} \pm 1 \text{ V}$

1st design

$$I_Z = 20 \text{ mA}$$

$$R = \frac{9 - 6.8}{0.020} = \underline{110 \Omega}$$
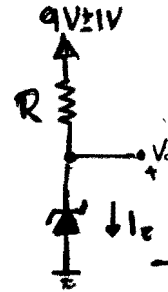
$$\text{Line Regulation} = \frac{\Delta V}{\Delta V_S} = \frac{r_Z}{r_Z + R} = \frac{5}{5 + 110} = \underline{43.48 \text{ mV/V}}$$



2nd design


$$I_Z = 0.25 \text{ mA}, V_Z = V_{Zk} \approx V_{Z0}, V_Z = V_{Zk} + r_Z I_Z \quad (4.20), (2)$$

$$6.8 = V_{Z0} + 5 \times 0.02 \rightarrow V_{Z0} = 6.7 \text{ V}$$

$$R_s = \frac{9 - 6.7}{0.25 \text{ mA}} = \underline{9.2 \text{ k}\Omega}$$

$$\text{Line Regulation} = \frac{r_Z}{r_Z + R} = \frac{750}{750 + 9.2 \text{ k}} = \underline{75.38 \text{ mV/V}}$$


③ Problem 4.67

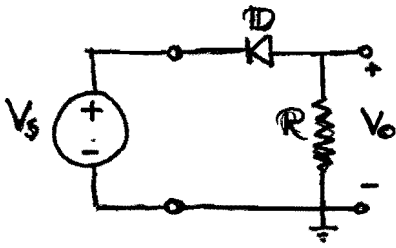

$$V_s = 10V \text{ Peak}$$


$$R = 1k\Omega$$

$$V_D = 0.7V$$

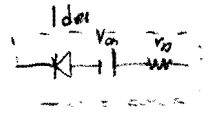


① Transfer Characteristic

$$V_o = 0 \text{ when } V_s \geq -0.7V$$

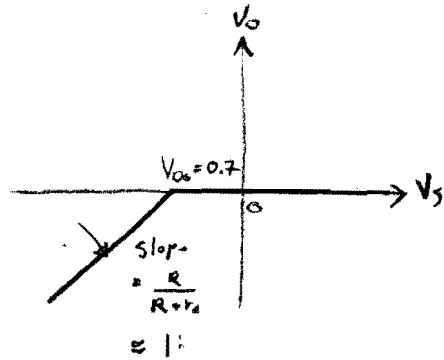

② V_o waveform

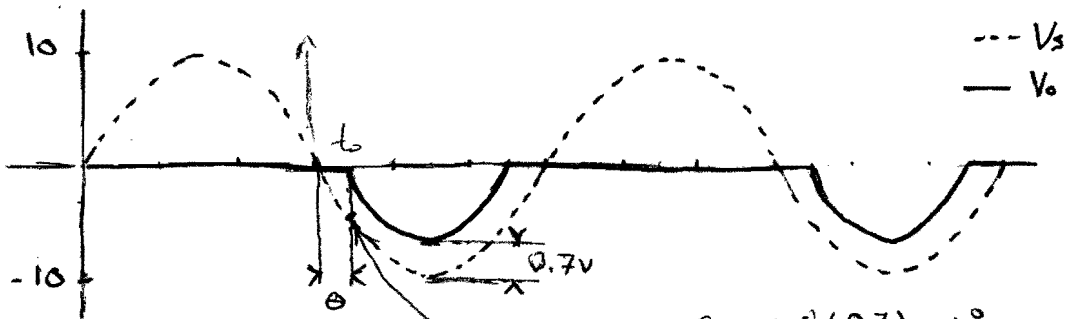

$$\theta = \sin^{-1}\left(\frac{0.7}{10}\right) = 4^\circ$$

③ Average Value of V_o

V_o starts at 4° and stops at $(180^\circ - 4^\circ)$

$$V_{avg} = -\frac{1}{2\pi} \int_{\theta}^{180-\theta} (10 \sin \phi - 0.7) d\phi = \underline{\underline{-2.95V}}$$

$$V_s = -0.7 = -10 \sin(\theta)$$

$$\frac{0.7}{10} = \sin(\theta)$$

$$\theta = \sin^{-1}\left(\frac{0.7}{10}\right)$$

④ Peak current in diode

$$I = \frac{V}{R} = \frac{10 - 0.7}{1k} = \underline{\underline{9.3mA}}$$


⑤ PIV of diode

PIV occurs when V_s is in the peak and $V_o = 0$

$$\text{PIV} = \underline{\underline{10V}}$$

④ Problem 4.71

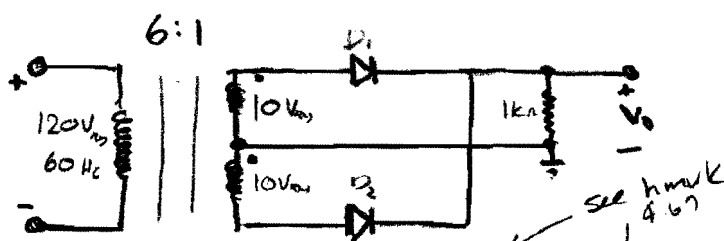Full-wave rectifier circuit with $1\text{ k}\Omega$ load operate from 120 V RMS , 60 Hz 6 to 1 transformer, with center-tapped secondary winding.




$$120/6 = 20 \\ = 10\text{V} + 10 \\ (\text{because of the center-tap})$$

$$V_0 = 10\sqrt{2} - V_0 \\ = 13.44\text{ V}$$

$$\theta_{\text{sin}} = \sin^{-1}\left(\frac{0.7}{10\sqrt{2}}\right) \\ = 2.84^\circ$$

$$\theta_{\text{di}} = 180^\circ - 2.8$$

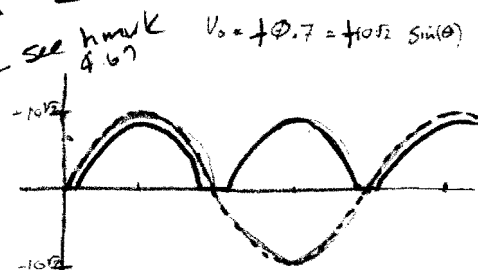

Conduction angle $= 180 - 2\theta = 174.3^\circ$, So the % when one of diodes is conducting is $\left(\cos\frac{174.3}{180}\right) = 96.8\%$, So each diode is conducting 48.4% of the cycle.

$$V_{0,\text{avg}} = \frac{1}{\pi} \int_{\theta}^{180-\theta} (10\sqrt{2} \sin(\phi) - 0.7) d\phi = \underline{8.3\text{ V}}$$

$$I_{L,\text{avg}} = \frac{8.3}{1\text{ k}\Omega} = \underline{8.3\text{ mA}}$$

From text Exercise 4.20,

$$V_0 \approx \frac{2}{\pi} V_s - V_D$$


$$V_s = 10\sqrt{2}\text{ V} \quad ; \quad V_D = 0.7\text{ V}$$

$$\therefore \underline{V_0} \approx \frac{2}{\pi} \cdot 10\sqrt{2} - 0.7 = \underline{8.30\text{ V}}$$



compares extremely favorably w/ $V_{0,\text{avg}}$ calculated above.

⑤ Problem 4.72

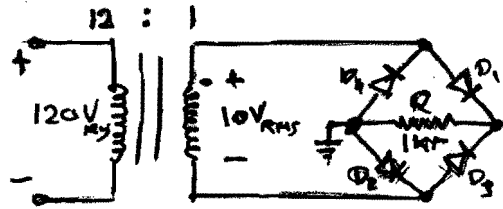

$$V_{R, \text{peak}} = 10\sqrt{2} - 2 \cdot V_0$$

$$= \underline{12.74 \text{ V}}$$

$$V_{0, 0.7}$$

$$\phi = \sin^{-1} \frac{1.4}{10\sqrt{2}} = 5.68^\circ$$

D_1 and D_2 Conduct together, for $\left(100^\circ - \frac{180 - 2\phi}{2}\right) = 46.84\%$ of the cycle.

D_3 and D_4 Conduct the rest of the cycle.

$$\underline{V_{0, \text{avg}}} = \frac{1}{\pi} \int_0^{180-\phi} (10\sqrt{2} - \sin(\phi) - 1.4) d\phi = \underline{7.65 \text{ V}}$$

$$i_{R, \text{avg}} = \frac{V_{0, \text{avg}}}{R} = \frac{7.65}{1 \text{ k}} = \underline{7.65 \text{ mA}}$$

From text Exercise 4.21



$$V_0 \approx \frac{2}{\pi} V_s - 2V_D$$

$$\text{with } V_s = 10 \cdot \sqrt{2} \text{ V} \quad \& \quad V_D = 0.7 \text{ V}$$

$$\text{then } \underline{V_0} \approx \frac{2}{\pi} \cdot 10\sqrt{2} - 2 \cdot 0.7 = \underline{7.60 \text{ V}}$$

↑
Compares very favorably
w/ $V_{0, \text{avg}}$ calculated above.

⑥ PROBLEM 4.74

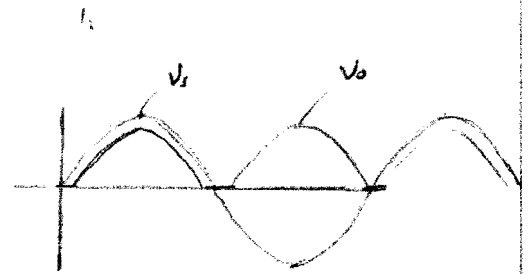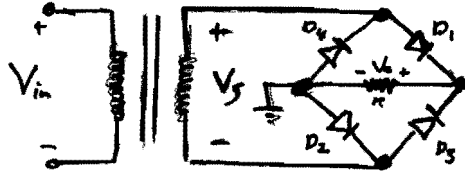

$$V_{o,avg} = \frac{2}{\pi} V_s - 2V_D$$

or $V_{o,avg} = 10V$

$$10 = \frac{2}{\pi} V_s - 1.4$$

$$V_s = 17.91V$$

$$\text{Turn Ratio} = \frac{120\sqrt{2}}{17.91} = \underline{9.47} \text{ to } 1 \approx 9$$


b) $V_{o,avg} = 100V$

$$100 = \frac{2}{\pi} V_s - 1.4$$

$$V_s = 159.3V$$

$$\text{Turn Ratio} = \underline{1.07} \text{ to } 1 \approx 1$$

⑦ Problem 4.75

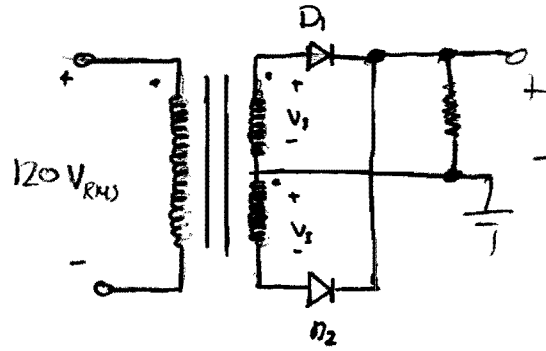

$$2 \times V_s = 20 \text{ V}_{\text{rms}}$$

$$V_s = 10 \text{ V}_{\text{rms}}$$

find PIV of the diode,

$$\text{Turn Ratio: } 120\sqrt{2} \pm 10\% : 20\sqrt{2} \pm 10\% \rightarrow \frac{120}{20} = \underline{\underline{6 \pm 1}}$$

$$V_s = \frac{20\sqrt{2}}{2} \pm 10\% = 10\sqrt{2} \pm 10\% \text{ V}$$

$$\text{PIV} = 2V_s - V_D$$

$$= 2 \times 10\sqrt{2} (1.1) - 0.7 = 30.41 \text{ V}$$

+10%

Using factor of 2 for safety

$$\text{PIV} = \underline{\underline{60.83 \text{ V}}}$$