

EE 320 – *Electronics I*

Homework #5

10 points

Date Assigned: 9/15

Date Due: 9/22

- 5.1 Text problem 4.77 Remember to account for $V_{D0}=0.7$ V in the diode.
- 5.2 Text problem 4.79 Remember to account for $V_{D0}=0.7$ V in the diodes.
- 5.3 Text problem 4.80
- 5.4 Text problem 4.87
- 5.5 Text problem 4.88
- 5.6 Text problem 4.92
- 5.7 Text problem 4.93
- 5.8 Text problem 4.96
- 5.9 Text problem 4.97 Only do parts (a), (b), (c), (d), and (g).