
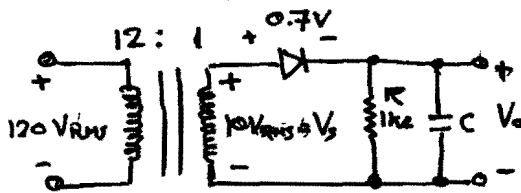


① PROBLEM 4.77

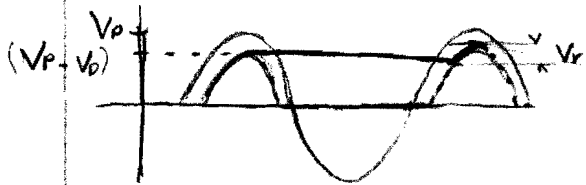

$$V_s = \frac{120}{12} = 10 V_{\text{RMS}}$$



$$\text{(Eq. 4.28)} \quad V_r \approx (V_p - V_o) \frac{T}{CR} \quad \therefore \text{when } f = \frac{1}{T}$$

$$10\% \quad 0.1 (V_p - V_o) = (V_o - V_o) \frac{T}{CR}$$

$$C = \frac{1}{0.1 \times 1000 \times 60} = 166.7 \mu\text{F}$$

$$1\% \quad 0.01 (V_p - V_o) = (V_p - V_o) \frac{T}{CR}$$

$$C = \frac{1}{0.01 \times 1000 \times 60} = 1666.7 \mu\text{F}$$

②

$$10\% \quad V_{o, \text{avg}} = V_p - V_o - \frac{1}{2} V_r \quad \text{(Eq. 4.27)}$$

$$\begin{aligned} \text{RMS} \quad &= 10\sqrt{2} - 0.7 - \frac{1}{2} (10\sqrt{2} - 0.7) 0.1 \\ &= \underline{12.77 \text{ V}} \end{aligned}$$

①

$$\begin{aligned} &= 10\sqrt{2} - 0.7 - \frac{1}{2} (10\sqrt{2} - 0.7) 0.01 \\ &= \underline{13.37 \text{ V}} \end{aligned}$$

① Cont. Problem 4.77

b)

10%

$$\omega \Delta t \approx \sqrt{2V_r / (V_p - V_0)} = \sqrt{2 \times 0.1 (V_p - 0.7) / (V_p - 0.7)} \quad V_r$$

$$\omega \Delta t = \sqrt{0.2} = 0.4472 \text{ rad of } 2\pi$$

$$\text{So diode is conducting } \frac{0.4472}{2\pi} \times 100\% = \underline{7.2\%}$$

1%

$$\omega \Delta t = \sqrt{2 \times 0.01} = 0.1414 \text{ rad}$$

$$\frac{0.1414}{2\pi} \times 100\% = \underline{2.25\%} \quad \text{diode is conducting}$$

c)

10%

$$\text{(Eq. 4.31)} \quad i_{D, \text{avg}} = I_L \left(1 + \pi \sqrt{\frac{2(V_p - V_0)}{V_r}} \right)$$

$$\text{from part a} = \frac{V_{0, \text{avg}}}{R} \left(1 + \pi \sqrt{\frac{2(V_p - V_0)}{0.1(V_p - V_0)}} \right) = \frac{12.77}{1000} \left(1 + \pi \sqrt{\frac{2}{0.1}} \right)$$

$$I_{D, \text{avg}} = \underline{192.2 \text{ mA}}$$

1%

$$I_{D, \text{avg}} = \frac{13.37}{1000} \left(1 + \pi \sqrt{\frac{2}{0.01}} \right) = \underline{607.4 \text{ mA}}$$

d)

10%

$$\text{(Eq. 4.32)} \quad i_{D, \text{peak}} = I_L \left(1 + 2\pi \sqrt{\frac{2(V_p - V_0)}{V_r}} \right) \approx I_L (V_p - V_0)$$


$$= \frac{V_{0, \text{avg}}}{R} \left(1 + 2\pi \sqrt{\frac{2(V_p - V_0)}{0.1(V_p - V_0)}} \right) = \frac{12.77}{10^3} \left(1 + 2\pi \sqrt{\frac{2}{0.1}} \right) =$$

$$= \underline{371.6 \text{ mA}}$$

1%

$$= \frac{13.37}{10^3} \left(1 + 2\pi \sqrt{\frac{2}{0.01}} \right) = \underline{1.201 \text{ A}}$$

② Problem 4.79

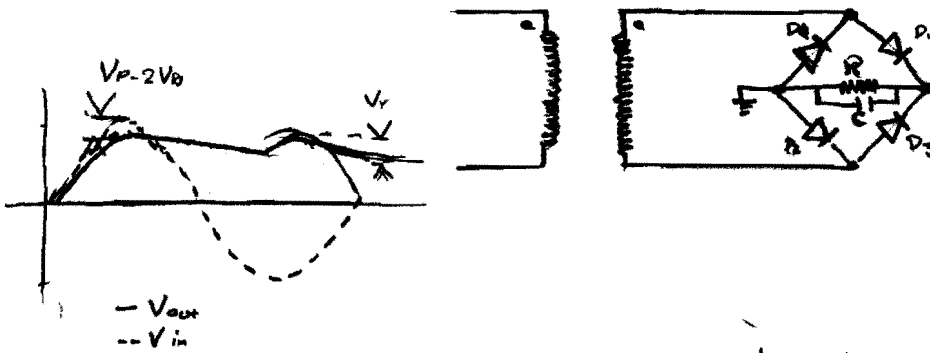

$$V_r = 0.1 (V_p - V_D \times 2) = \frac{V_p - 2V_D}{2fCR} \quad \text{See Problem 4.77} \quad \text{(Eq. 4.28)}$$

$$\textcircled{10\%} \quad C = \frac{(V_p - 2V_D)}{(V_p - 2V_D) \times 2 \times 0.1 \times fR} = \frac{1}{2 \times 0.1 \times 60 \times 10^3} = \underline{83.3 \mu\text{F}}$$

$$\textcircled{1\%} \quad C = \frac{1}{2 \times 0.01 \times 60 \times 10^3} = \underline{833.3 \mu\text{F}}$$

$$\textcircled{a} \quad V_o = V_p - 2V_D - \frac{1}{2} V_r \quad \text{(Eq. 4.27)}$$

$$\begin{aligned} \textcircled{10\%} \quad V_{o,10\%} &= V_p - 2V_D - \frac{1}{2} (V_p - 2V_D) \times 0.1 \\ &= (V_p - 2V_D) \times (1 - \frac{1}{2} \times 0.1) \\ &= (10\sqrt{2} - 2 \times 0.7) \times (0.95) = \underline{12.1\text{V}} \end{aligned}$$

$$\textcircled{1\%} \quad V_{o,1\%} = (10\sqrt{2} - 2 \times 0.7) \times (1 - \frac{1}{2} \times 0.01) = \underline{12.68\text{V}}$$

$$\textcircled{b} \quad \textcircled{10\%} \quad \text{Fraction of cycle} = \frac{2\omega \Delta t}{2\pi} \times 100$$

$$\text{(Eq. 4.38)} \quad \omega \Delta t = \sqrt{\frac{2V_r}{V_p - 2V_D}} = \sqrt{\frac{2(V_p - 2V_D) \times 0.1}{(V_p - 2V_D)}} = \sqrt{\frac{2 \times 0.1}{1}} = 0.4472 \text{ rad}$$

$$100 \times \frac{0.4472}{\pi} = \underline{14.24\%}$$

$$\textcircled{1\%} \quad = \sqrt{2 \times 0.01} = 0.1414 \text{ rad}$$

$$100 \times \frac{0.1414}{\pi} = \underline{4.5\%}$$

② Cont. Problem 4.79

C

10%

$$I_{D, \text{avg}} = I_L \left(1 + \pi \sqrt{\frac{V_P - V_D}{2 V_r}} \right) \quad (4.34)$$

$$= \frac{V_{o, \text{avg}}}{R} \left(1 + \pi \sqrt{\frac{-(V_P - V_D)}{0.1(V_P - V_D) \times 2}} \right)$$

from a

$$= \frac{12.1}{10^3} \left(1 + \pi \sqrt{\frac{1}{0.2}} \right) = \underline{97.1 \text{ mA}}$$

1%

$$I_{D, \text{avg}} = \frac{12.68}{10^3} \left(1 + \pi \sqrt{\frac{1}{0.02}} \right) = \underline{294.4 \text{ mA}}$$

d

$$10\% \quad I_{D, \text{peak}} = I_L \left(1 + 2\pi \sqrt{\frac{V_P - V_D}{2 V_r}} \right)$$


$$= \frac{V_{o, \text{max}}}{R} \left(1 + 2\pi \sqrt{\frac{V_P - V_D}{2 \times 0.1(V_P - V_D)}} \right)$$

$$= \frac{12.1}{1000} \left(1 + 2\pi \sqrt{\frac{1}{0.2}} \right) = \underline{182.1 \text{ mA}}$$

1%


$$I_{D, \text{peak}} = \frac{12.68}{1000} \left(1 + 2\pi \sqrt{\frac{1}{0.02}} \right) = \underline{576.0 \text{ mA}}$$

③ Problem 4.80

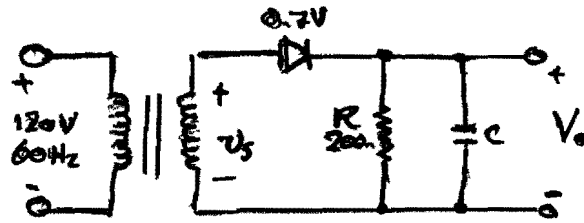

$$V_o = 12V \pm 1V \text{ (ripple)}$$

$$R_L = 200 \Omega$$

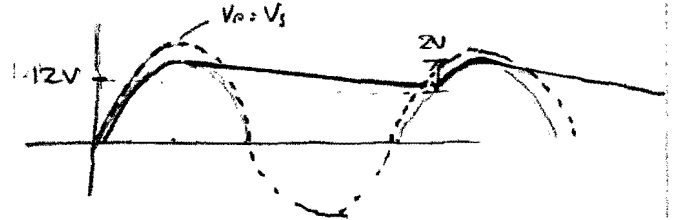

$$\textcircled{a} \quad V_o = V_p - V_D - I$$

$$\text{for half cycle } V_{s, \text{avg}} = V_p - V_D - \frac{V_r}{2} \quad (4.27)$$

$$V_p = 12 + 1 + V_D = 13.7V, \quad V_{p, \text{RMS}} = \frac{13.7}{\sqrt{2}} = \underline{9.7V}$$

$$\textcircled{b} \quad V_r = \frac{V_r - V_D}{fCR} \quad (\text{Eq. 4.29})$$

$$C = \frac{V_p - V_D}{f \cdot R (V_r)} = \frac{13.7 - 0.7}{60 \times 200 \times 2} = \underline{541.7 \mu\text{F}}$$

③ — When the diode is cutoff, the maximum reverse voltage across it will occur when $v_s = -V_p$. At this time, $v_o = V_o$ and maximum reverse voltage will be $V_o + V_p = 12 + 13.7 = \underline{25.7V}$


$$\text{Using factor of safety of 1.5} \quad \text{PIV} = 1.5 \times 25.7 = \underline{38.5V}$$

$$\textcircled{d} \quad \text{---} \quad (\text{Eq. 4.31}) \quad \dot{I}_{\text{OAV}} = \frac{V_{s, \text{avg}}}{R} = I_L \left(1 + \pi \sqrt{\frac{2(V_p - V_D)}{V_r}} \right) = \frac{12V}{200} \left(1 + \pi \sqrt{\frac{2(13.7 - 0.7)}{2}} \right) = \underline{0.7396A}$$

$$\textcircled{e} \quad \text{---} \quad (\text{Eq. 4.32}) \quad \dot{I}_{D, \text{MAX}} = I_L \left[1 + 2\pi \sqrt{\frac{2(V_p - V_D)}{V_r}} \right] = \frac{12V}{200} \left[1 + 2\pi \sqrt{\frac{2(13.7 - 0.7)}{2}} \right] = \underline{1.419A}$$


④ Problem 4.87

①

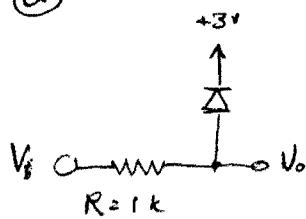

$$V_i = V_o + iR$$


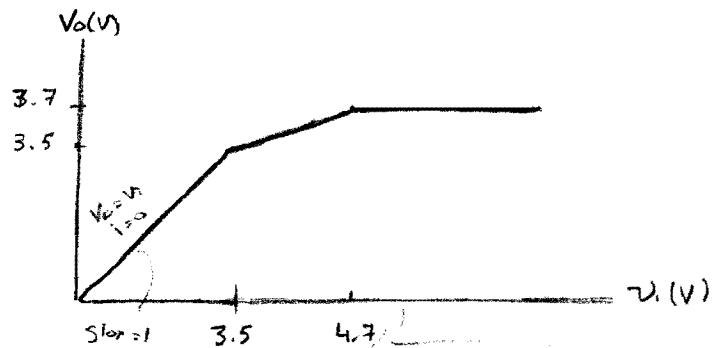
$$V_i \leq 3.5V, i = 0 \text{ and } V_o = V_i$$



at $V_i = 3.7V$ the diode is conducting $i = 1mA$ so $V_i = V_o + 1mA \times 10^3 = 4.7V$

for $V_i > 4.7V$ the diode current is $0.7V$, thus V_o flattens and V_o vs V_i becomes a horizontal line. In practice, the diode current increases slowly and the line will have a small nonzero slope.

②

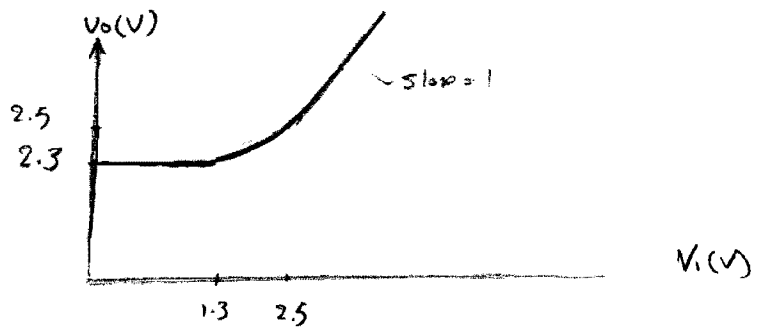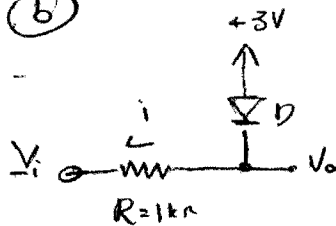

$$\text{If } V_o > 2.5V, V_o = V_i$$



diode conducting when $V_o = 2.5V$ so $I_o = 1mA$ with drop of 0.7 at

$$V_o = 2.3$$

$$\text{so } V_i = V_o + iR = 2.3 + 1mA \times 10^3 = \underline{\underline{3.3V}}$$

(c) Cont. Problem 4.87

(c)

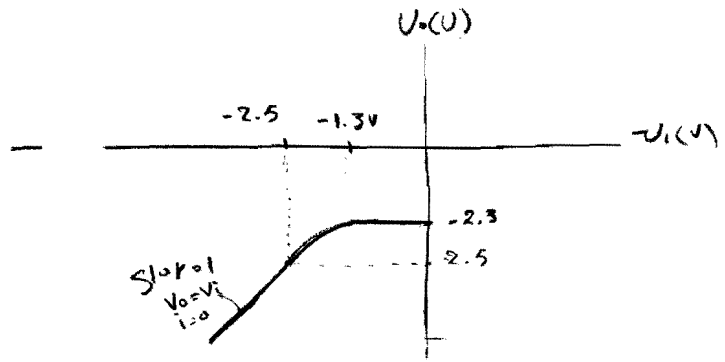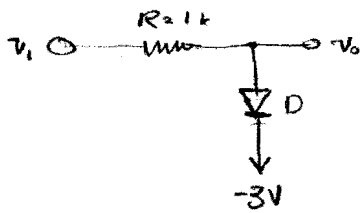

For $V_i \leq -2.5V$ the diode will be off and $v_o = v_i$. at $v_i = -2.5V$ the diode begins to conduct and its current reaches $1mA$ at $v_i = -1.3V$ (corresponding to $v_o = -2.3V$). As v_i further increases, the diode current increases but its voltage remains constant at $0.7V$ Thus v_o flattens



$$V_o = -3V + 0.5 = -2.5V$$

full conducting $V_D = 0.7V$

$$V_o = -2.3V$$

$$V_i = -2.3 + 1mA \times 1000 = -1.3V$$

(d)

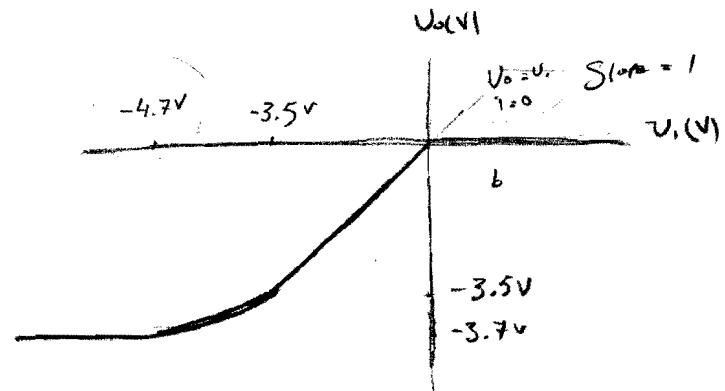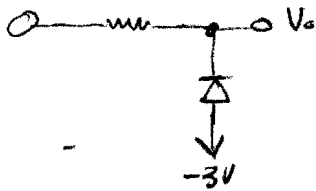


begin conducting at $0.5V$

$$V_o = -3.5V$$

full conducting $V_o = -3 - 0.7 = -3.7V$

$$V_i = -3.7 - 1mA \times 1000 = -4.7V$$

⑤ PROBLEM 4.87

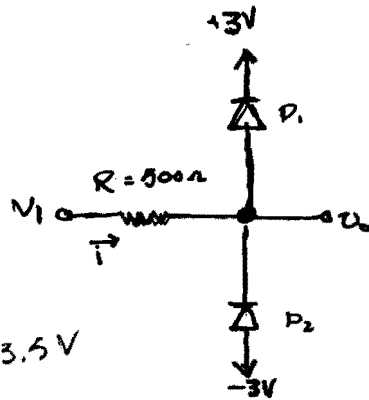

$$\text{So } -3.5 \leq V_1 \leq +3.5 \text{ V}$$

diodes D_1 and D_2 will be

cut-off and $i = 0$, thus $V_0 = V_1$. For $V_1 > 3.5 \text{ V}$ D_1 will begin conducting

and its voltage reaches 0.7 V (and thus $V_0 = +3.7 \text{ V}$) at $i = 1 \text{ mA}$, the corresponding

value of V_1 is $V_1 = V_0 - iR$,

$$V_1 = 3.7 + 1 \text{ m} \times 500 = +4.2 \text{ V}$$

for $V_1 > 4.2 \text{ V}$, the voltage of diode D_1 remains 0.7 V and V_0 saturates at $+3.7 \text{ V}$


if $V_1 \leq -3.5$ D_2 conducts at $V_1 = -3.5 \text{ V}$ and its voltage becomes 0.7

$V_0 = -3.7$ at $i = 1 \text{ mA}$ (in the direction into V_1) at $V_1 = -4.2 \text{ V}$

for $V_1 \leq -4.2$, $V_0 = -3.7 \text{ V}$

if $V_0 > 3.7$
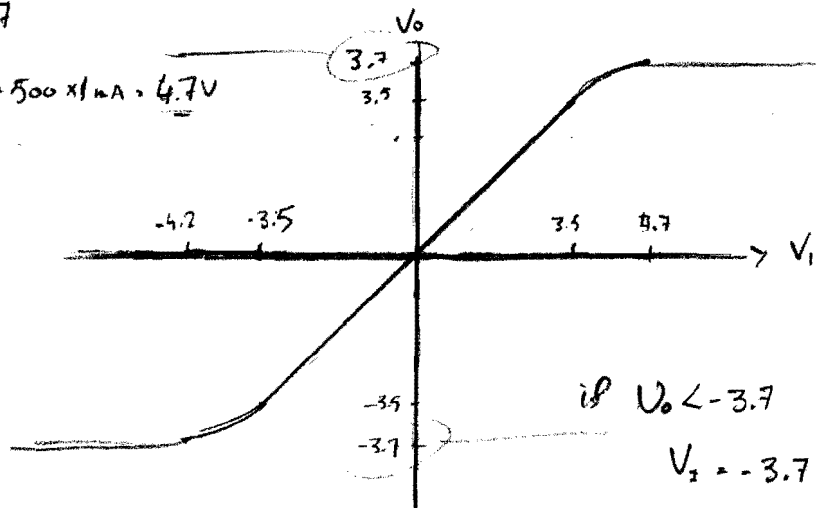
$$V_1 = 3.7 + 500 \times 1 \text{ mA} = \underline{4.7 \text{ V}}$$



if $V_0 < -3.7$ D_2 ON

$$V_1 = -3.7 - 500 \times 1 \text{ m} = \underline{-4.2 \text{ V}}$$

D_2 ON



D_1 OFF

D_1 and D_2 OFF



D_1 ON

D_2 OFF



⑥ Problem 4.92

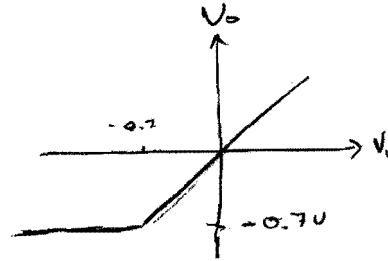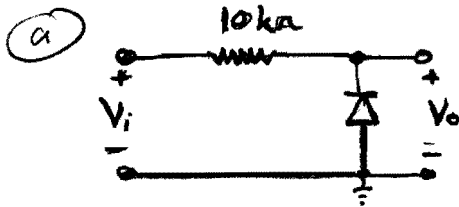Limiting Circuit Using Diodes and $10\text{ k}\Omega$ resistor① -0.7V and above, ② -2.1V and above, ③ $\pm 1.4\text{V}$ 


②

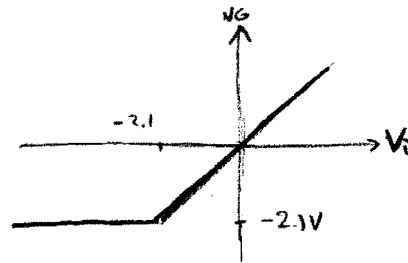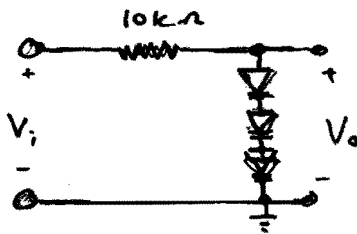 $2.1/0.7 = 3$ diodes

③

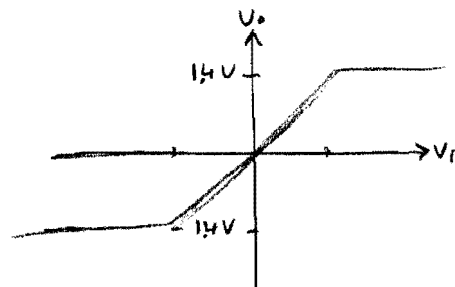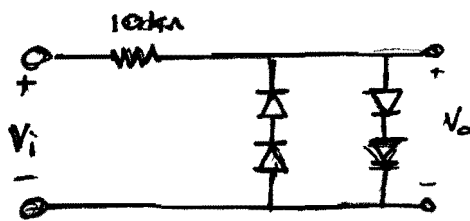


⑦ Problem 4.93

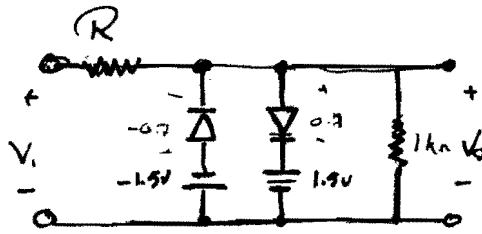Two side limiting circuit using 2 Diodes and resistor. limiting level of $\pm 3.8V$ 

In the nonlimiting region




$$\frac{V_o}{V_i} = \frac{1000}{1000 + R} \approx 0.94$$

$$R \leq 63.8 \Omega$$

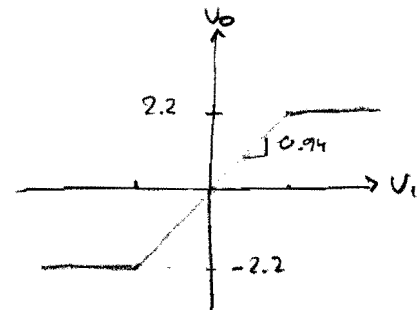

⑧ Problem 496

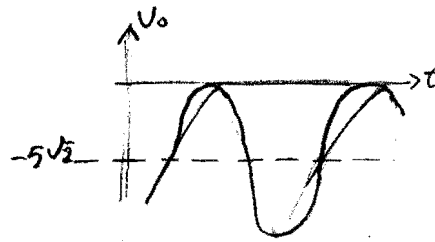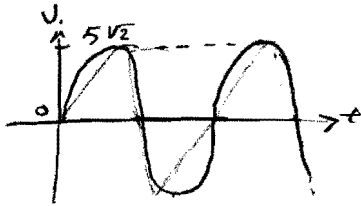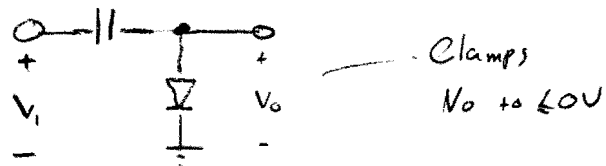
A clamped capacitor using an ideal diode with cathode grounded is supplied with a sine wave of 10-V_{rms} . What is the average (dc) value of resulting output?





$$V_{o,\text{avg}} = -5\sqrt{2} = -7.071\text{V}$$

9



PROBLEM 4.97

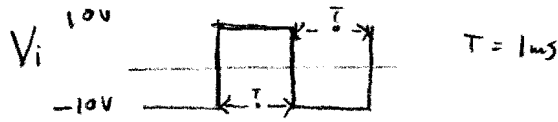



(a)

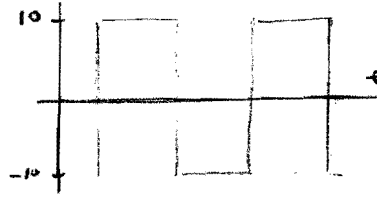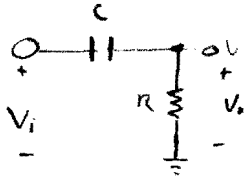



(b)

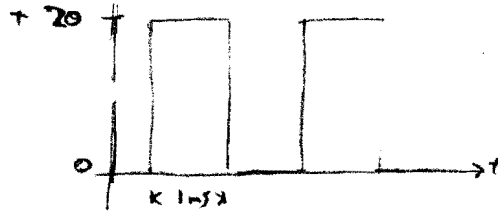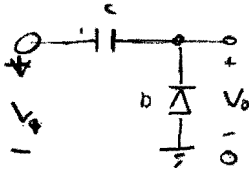



(c)

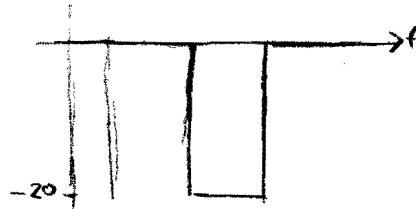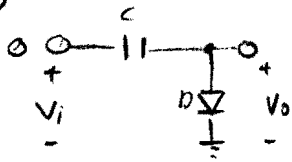

(d)

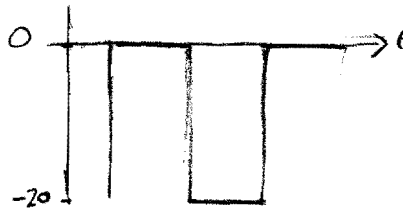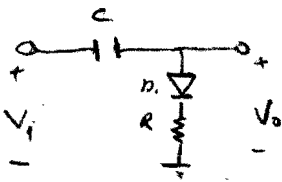

(e)

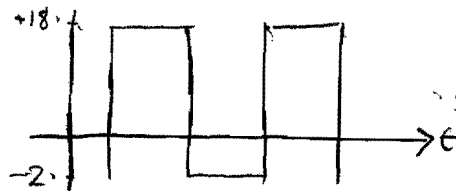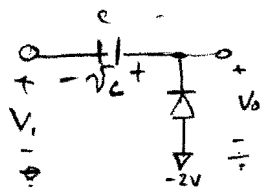

$$V_c \rightarrow -2 - (-10) = -8\text{V}$$

$$V_o = V_i + V_c$$

$$-10 + 8 = -2\text{V}$$

$$+10 + 8 = 18$$