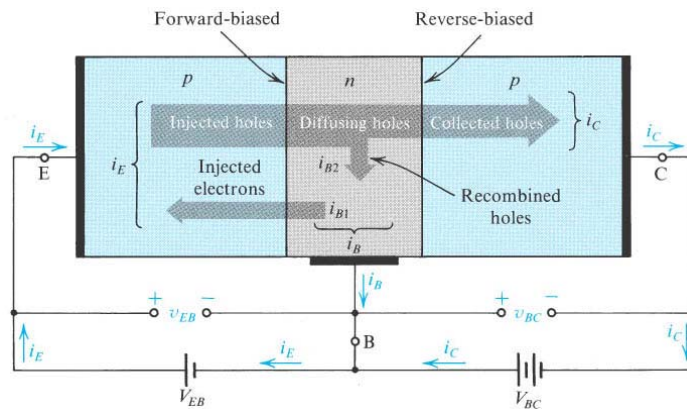


# Lecture 11: PNP Bipolar Junction Transistor Physical Operation. BJT Examples.

The second type of BJT is formed from *pn*p doped regions as




(Fig. 5.11)

Differences between *pn*p and *npn* BJTs are:


- Biasing voltages are **applied oppositely** to the *npn*, though still forward biasing EBJ and reverse biasing the CBJ for active mode operation, for example.
- Current is primarily composed of holes (in the *p* type regions) rather than electrons as in the *npn* BJT.
- The current direction conventions are  $i_E$  **into** the emitter while  $i_C$  and  $i_B$  are **out** from the device.

The circuit symbol for the *pn*p BJT is

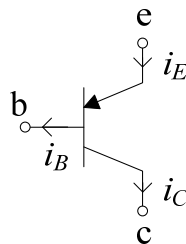

Once again, the **filled arrow** is always located on the emitter and helps us to remember the direction of the emitter current. Notice that the currents are pointed in **opposite directions** compared to the *npn* BJT.

For biasing in the active mode, a possible circuit is

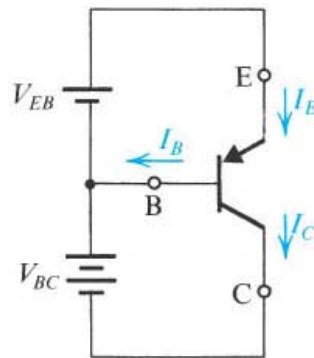

(Fig. 5.14b)

As with the *npn*, for the *pnp* BJT in the active mode and **with the current convention** shown above

$$i_C = \alpha i_E \quad (5.16),(1)$$

$$i_B = (1 - \alpha) i_E \quad (2)$$

$$i_C = \beta i_B \quad (5.10),(3)$$

$$\beta = \frac{\alpha}{1 - \alpha} \quad (5.19),(4)$$


$$\alpha = \frac{\beta}{\beta + 1} \quad (5.17),(5)$$

Consequently, we need to only **memorize this one set of equations** for use with both *npn* and *pnp* BJTs, plus the current conventions for these two BJTs.

## Examples

We'll now consider a few examples of the DC analysis of *npn* and *pnp* BJT circuits.

**Example N11.1** (text example 5.1). Design the following circuit so that  $I_C = 2 \text{ mA}$  and  $V_C = 5 \text{ V}$ . For this particular transistor,  $\beta = 100$  and  $V_{BE} = 0.7 \text{ V}$  at  $I_C = 1 \text{ mA}$ .

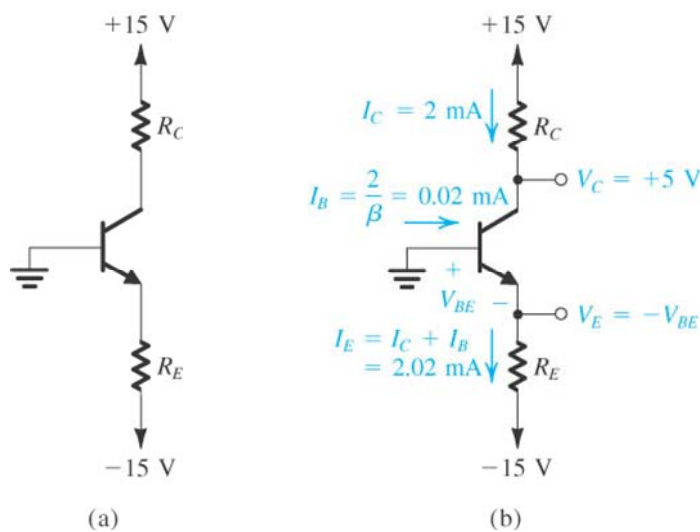

(Fig. 5.15)

The “design” of this circuit is to determine the  $R_C$  and  $R_E$  that provide the specified  $I_C$  and  $V_C$ .

For  $I_C = 2 \text{ mA}$ , then

$$\frac{15 - V_C}{R_C} = 2 \text{ mA} \quad \text{or} \quad R_C = \frac{15 - 5}{2 \times 10^{-3}} = 5 \text{ k}\Omega.$$

We're assuming that the transistor is in the **active mode** with the EBJ forward biased and the CBJ reversed biased.

For the forward biased EBJ junction,

$$i_C = I_S e^{\frac{v_{BE}}{V_T}} \quad (5.3),(6)$$

It's given that at  $I_C = 1$  mA,  $V_{BE} = 0.7$  V. What is  $V_{BE}$  when  $I_C = 2$  mA? Using (6) for two different  $i_C$  and  $v_{BE}$  we find that

$$\frac{i_{C1}}{i_{C2}} = e^{\frac{v_{BE1} - v_{BE2}}{V_T}} \quad \text{or} \quad \frac{v_{BE1} - v_{BE2}}{V_T} = \ln\left(\frac{i_{C1}}{i_{C2}}\right)$$

Therefore,

$$v_{BE2} = v_{BE1} + V_T \ln\left(\frac{i_{C1}}{i_{C2}}\right) \quad (7)$$

For this particular case,

$$V_{BE2} = 0.7 + 25 \times 10^{-3} \ln\left(\frac{2}{1}\right) = 0.717 \text{ V}$$

This is **not much of an increase** from 0.7 V, which is what we typically observe when the BJT is in the active mode.

Consequently,  $V_E = -0.717$  V

Next,  $i_C = \alpha i_E \Rightarrow i_E = \frac{i_C}{\alpha} = \frac{\beta + 1}{\beta} i_C$

then  $I_E = \frac{100 + 1}{100} \cdot 2 \text{ mA}$  or  $I_E = 2.02 \text{ mA}$

We can use this emitter current to select the proper resistor  $R_E$ :

$$I_E = \frac{V_E - (-15 \text{ V})}{R_E}$$

or

$$R_E = \frac{-0.717 + 15}{2.02 \times 10^{-3}} = 7.07 \text{ k}\Omega$$


That completes the design.

One last thing, though. **Notice** how small the base current  $I_B$  is relative to  $I_C$  and  $I_E$ :

$$I_B = I_C - I_E = 20 \text{ }\mu\text{A}.$$

This is **typical** of BJTs operating in the active mode.

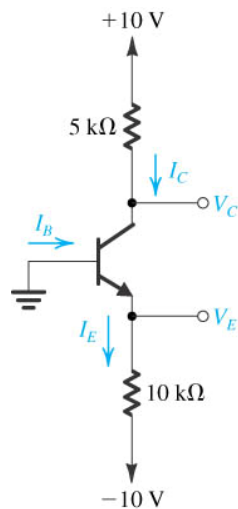**Example N11.2** (text exercise 5.10). Determine  $I_E$ ,  $I_B$ ,  $I_C$ , and  $V_C$  in the circuit below if  $\beta = 50$  and  $V_E = -0.7 \text{ V}$ .



(Fig. E5.10)

Because  $V_B = 0$ , then the given  $V_E$  means the BJT may be operating in the **active mode** since  $V_{BE} = 0.7$  V. (It could also be operating in the saturation mode.) We'll assume active mode operation for now, and confirm this assumption when we're finished.

(i) Compute  $I_E$ .

$$I_E = \frac{-0.7 - (-10)}{10,000} = 0.93 \text{ mA}$$

(ii) Compute  $I_C$ .

$$I_C = \alpha I_E = \frac{\beta}{\beta + 1} I_E = \frac{50}{51} \cdot 0.93 \text{ mA} = 0.91 \text{ mA}$$

(iii) Compute  $I_B$ .

$$I_C = \beta I_B \Rightarrow I_B = \frac{I_C}{\beta} = \frac{0.91 \text{ mA}}{50} = 18.2 \text{ } \mu\text{A}$$


(iv) Compute  $V_C$ .

$$V_C = 10 - 5,000 \cdot I_C = 5.45 \text{ V}$$

Note that since  $V_{CB} = V_C - V_B = 5.45 - 0 = 5.45$  V is greater than zero (thus reverse biasing the CBJ) and the EBJ is forward biased, the *npn* BJT is indeed operating in the active mode, as assumed.

---

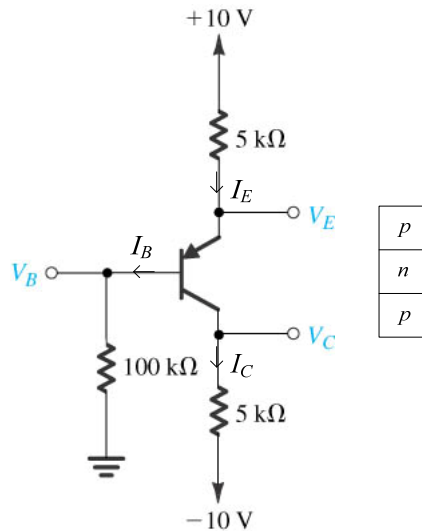**Example N11.3** (text exercise 5.11). Given that  $V_B = 1.0$  V and  $V_E = 1.7$  V, determine  $\alpha$  (and  $\beta$ ) for the transistor in the circuit below. Also calculate  $V_C$ .



(Fig. E5.11)

Because  $V_{EB} = V_E - V_B = 0.7$  V, the *pnp* transistor may be operating in the **active mode**, which is what we will assume.

(i) Determine  $\alpha$  and  $\beta$ . We'll use the relationships  $i_C = \alpha i_E$  and  $i_C = \beta i_B$  to determine  $\alpha$  and  $\beta$ .

$$\text{From the circuit, } I_B = \frac{V_B}{100 \times 10^3} = \frac{1.0}{100 \times 10^3} = 10 \mu\text{A}$$

$$\text{and } I_E = \frac{10 - 1.7}{5,000} = 1.66 \text{ mA}$$

Using KCL:

$$I_C = I_E - I_B = 1.66 \times 10^{-3} - 10 \times 10^{-6} = 1.65 \text{ mA.}$$

Therefore,

$$\beta = \frac{I_C}{I_B} = \frac{1.65 \times 10^{-3}}{10 \times 10^{-6}} = 165$$

and

$$\alpha = \frac{I_C}{I_E} = \frac{1.65 \times 10^{-3}}{1.66 \times 10^{-3}} = 0.994$$

Alternatively,

$$\alpha = \frac{\beta}{\beta + 1} = 0.994$$

(ii) Compute  $V_C$ .

$$V_C = -10 \text{ V} + 5,000 \cdot I_C = -10 \text{ V} + 5,000 \cdot 1.65 \times 10^{-3}$$

or

$$V_C = -1.75 \text{ V}.$$

Note that this  $V_C$  means that the CBJ is reversed biased by the voltage  $1.0 - (-1.75) = 2.75 \text{ V}$ . Hence, the active mode operation for the *pn*p BJT is the proper assumption since we've already determined that the EBJ is forward biased.