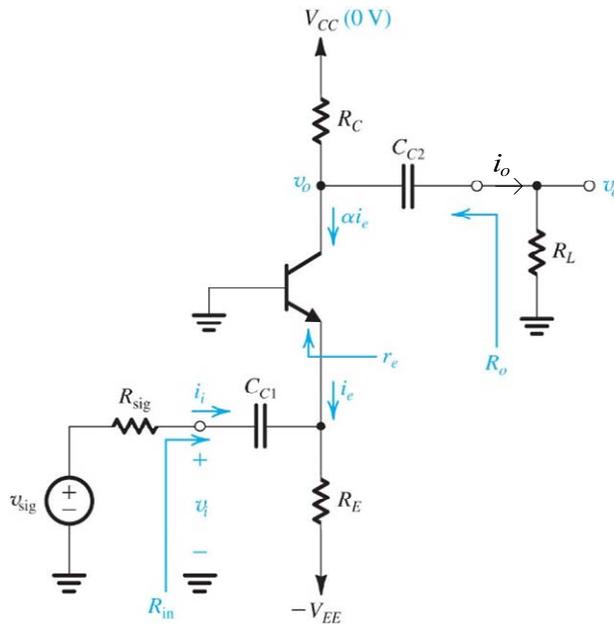



Lecture 20: Common Base Amplifier.

We will cover the **second** of the three families of BJT amplifiers in this lecture by discussing the **common base** amplifier shown in Fig. 7.58a:



(Fig. 7.58a)

The small-signal equivalent circuit for this amplifier is shown in Fig. 7.58b (ignoring r_o):

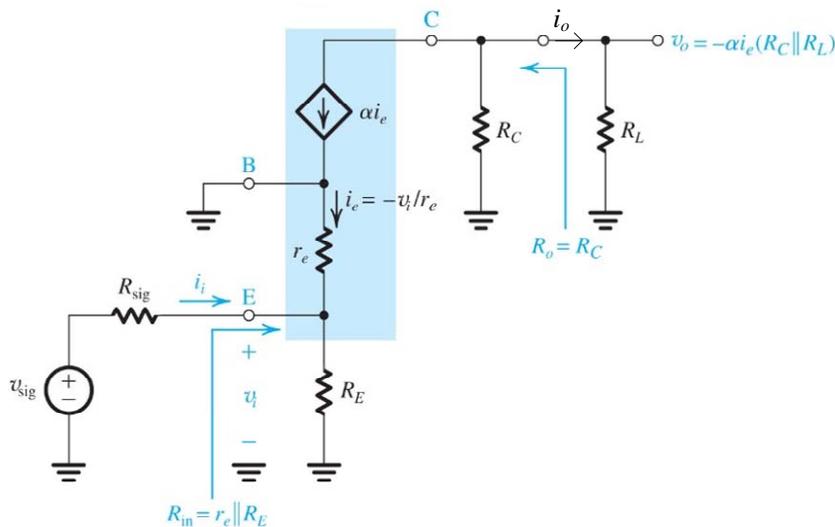

(Fig. 7.58b)

As before, let's determine the small-signal AC characteristics of this amplifier by solving for R_{in} , G_v , G_i , A_{is} , and R_{out} .

- Input resistance, R_{in} . From direct inspection of the small-signal equivalent circuit, we see that

$$R_{in} = r_e \parallel R_E \quad (1)$$

Since r_e is often small (on the order of 20 to 30 Ω), then R_{in} of the CB amplifier is **very small**. Generally this is not desirable, though in the case of certain high frequency amplifiers input impedances near 50 Ω is very useful (to reduce so-called “mismatch reflections” at the input).

- Small-signal voltage gain, G_v . We'll first calculate the **partial voltage gain**

$$A_v \equiv \frac{v_o}{v_i} \quad (2)$$

At the output,

$$v_o = -\alpha i_e (R_C \parallel R_L) \quad (3)$$

The small-signal emitter current is

$$i_e = \frac{-v_i}{r_e} \quad (4)$$

Substituting (3) and (4) into (2) gives the partial voltage gain to be

$$A_v = \frac{\alpha}{r_e} (R_C \parallel R_L) = g_m (R_C \parallel R_L) \quad (5)$$

This is the **same** gain as for the CE amplifier (without r_o), except the gain here for the CB amplifier is positive.

The **overall** (from the input to the output) small-signal voltage gain G_v is defined as

$$G_v \equiv \frac{v_o}{v_{\text{sig}}} \quad (6)$$

We can equivalently write this voltage gain as

$$G_v = \frac{v_i}{v_{\text{sig}}} \cdot \frac{v_o}{v_i} \equiv \frac{v_i}{v_{\text{sig}}} A_v \quad (7)$$

with A_v given in (5).

By simple voltage division at the input to the small-signal equivalent circuit

$$v_i = \frac{R_{\text{in}}}{R_{\text{in}} + R_{\text{sig}}} v_{\text{sig}} \quad (8)$$

Substituting this result and (5) into (7) yields the final expression for the **overall small-signal voltage gain**

$$G_v = \frac{\alpha(R_C \parallel R_L)}{r_e} \frac{R_{\text{in}}}{R_{\text{in}} + R_{\text{sig}}} \quad (9)$$

or since $r_e = \alpha/g_m$ as in (7.74)

$$G_v = g_m (R_C \parallel R_L) \frac{R_{\text{in}}}{R_{\text{in}} + R_{\text{sig}}} \quad (7.155), (10)$$

This gain can be fairly large, though if R_{sig} is nearly the same size as R_{in} , or larger, the gain will be small. In other words, if

this amplifier is connected to a high output impedance stage at the input, it will be **difficult** to realize high gain.

- Overall small-signal current gain, G_i . By definition

$$G_i \equiv \frac{i_o}{i_i} \quad (11)$$

Using current division at the output of the small-signal equivalent circuit above

$$i_o = \frac{-R_C}{R_C + R_L} i_c = \frac{-\alpha R_C}{R_C + R_L} i_e \quad (12)$$

With

$$i_i = \frac{-R_E}{R_E + R_{\text{sig}}} i_e$$

then substituting this into (12) gives

$$G_i = \frac{i_o}{i_i} = \frac{\alpha R_C}{R_C + R_L} \frac{R_E + R_{\text{sig}}}{R_E} \quad (13)$$

- Short circuit current gain, A_{is} . In the case of a short circuit load ($R_L = 0$), G_i in (13) reduces to the **short circuit current gain**:

$$A_{is} = \frac{i_{os}}{i_i} = \alpha \frac{R_E + R_{\text{sig}}}{R_E} \quad (14)$$

- Output resistance, R_o . Referring to the small-signal equivalent circuit above and shorting out the input $v_{\text{sig}} = 0$

$$R_o = R_C \quad (15)$$

which is the same as the CE amplifier (when ignoring r_o).

Summary

Summary of the CB small-signal amplifier:

1. Low input resistance.
2. G_v is positive and can be very large, though critically dependent on R_{sig} .
3. From (13), if $R_{\text{sig}} \ll R_E$ and $R_L \ll R_C$, then $G_i \approx \alpha$.
4. Potentially large output resistance (dependent on R_C).

One very important use of the CB amplifier is as a **unity-gain current amplifier**, which is also called a current buffer amplifier. This type of amplifier accepts an input signal current at a low impedance level ($\approx r_e \parallel R_E$ in Fig. 7.58b) and outputs nearly the same current amplitude, but at a high output impedance level ($\approx R_C$). (See 3. above.) Even though this is a buffer amplifier, there can still be **power gain**.