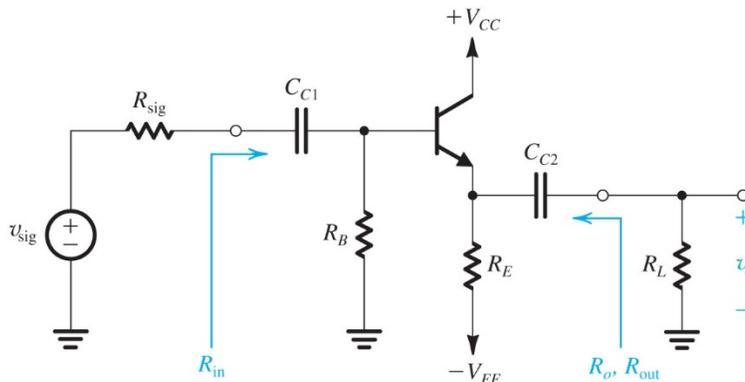



## Lecture 21: Common Collector (Emitter Follower) Amplifier.

The **third**, and final, small-signal BJT amplifier we will consider is the **common collector amplifier** shown below:



(Fig. 7.59a)


The small-signal equivalent circuit is shown in Fig. 7.59b:

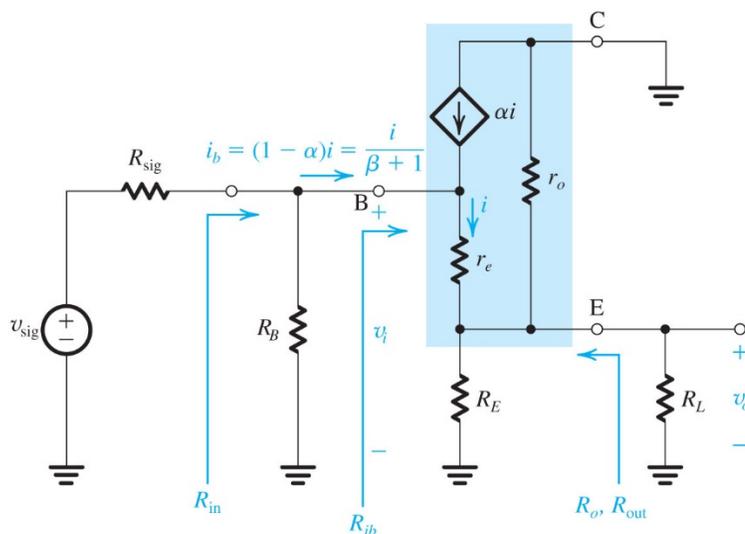

(Fig. 7.59b)

We've **included**  $r_o$  in this model since it can have an appreciable effect on the operation of this amplifier. Additionally, its effects can be accounted for analytically quite simply.

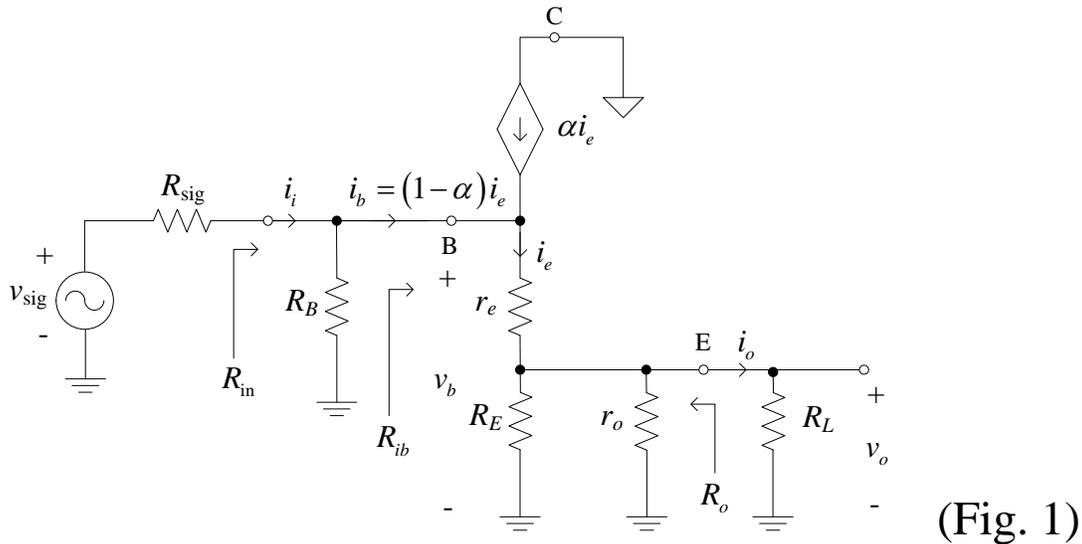Notice that  $r_o$  is connected from the emitter to an AC ground. We can **considerably simplify** the AC small-signal analysis of this circuit by moving the collector-side lead of  $r_o$  to the DC ground, as shown below:



Similar to the previous BJT amplifiers, we'll determine the characteristics of this one by solving for  $R_{in}$ ,  $G_v$ ,  $G_i$ ,  $A_{is}$ , and  $R_o$ .

- Input resistance,  $R_{in}$ . Looking into the base of the BJT,

$$R_{ib} = \frac{v_b}{i_b} \quad (1)$$

From the circuit above, we see that

$$v_b = i_e (r_e + R_E \parallel r_o \parallel R_L) \quad (2)$$

Substituting this and  $i_b = i_e / (\beta + 1)$  into (1) yields

$$R_{ib} = (\beta + 1)(r_e + R_E \parallel r_o \parallel R_L) \quad (7.157), (3)$$

This expression for  $R_{ib}$  follows the so-called **resistance reflection rule**: the input resistance is  $(\beta+1)$  times the total

resistance in the emitter lead of the amplifier, as seen in the T small-signal model. (We saw a similar result in Lecture 19 for the CE amplifier with emitter degeneration.)

In the special case when  $r_e \ll R_E \parallel R_L \ll r_o$  then

$$R_{ib} \approx (\beta + 1)(R_E \parallel R_L) \quad (4)$$

which can potentially be a **large** value.

Referring to circuit above, the **input resistance** to the amplifier is

$$R_{in} = R_B \parallel R_{ib} \stackrel{(3)}{=} R_B \parallel [(\beta + 1)(r_e + R_E \parallel r_o \parallel R_L)] \quad (7.156),(5)$$

- Small-signal voltage gain,  $G_v$ . We'll first calculate the **partial voltage gain**

$$A_v \equiv \frac{v_o}{v_b} \quad (6)$$

Beginning at the output,

$$v_o = \frac{R_E \parallel r_o \parallel R_L}{R_E \parallel r_o \parallel R_L + r_e} v_b \quad (7.159),(7)$$

from which we can directly determine that

$$A_v = \frac{R_E \parallel r_o \parallel R_L}{R_E \parallel r_o \parallel R_L + r_e} \quad (8)$$

The **overall** (from the input to the output) small-signal voltage gain  $G_v$  is defined as

$$G_v \equiv \frac{v_o}{v_{\text{sig}}} \quad (9)$$

We can equivalently write this voltage gain as

$$G_v = \frac{v_b}{v_{\text{sig}}} \cdot \frac{v_o}{v_b} \equiv \frac{v_b}{v_{\text{sig}}} A_v \quad (10)$$

with  $A_v$  given in (8).

By simple voltage division at the input to the small-signal equivalent circuit

$$v_b = \frac{R_{\text{in}}}{R_{\text{in}} + R_{\text{sig}}} v_{\text{sig}} \quad (11)$$

Substituting this result into (10) yields an expression for the **overall** small-signal voltage gain

$$G_v \equiv \frac{v_o}{v_{\text{sig}}} = \frac{R_E \parallel r_o \parallel R_L}{R_E \parallel r_o \parallel R_L + r_e} \frac{R_{\text{in}}}{R_{\text{in}} + R_{\text{sig}}} \quad (7.160)$$

or

$$G_v = \frac{R_E \parallel r_o \parallel R_L}{R_E \parallel r_o \parallel R_L + r_e} \frac{R_B \parallel [(\beta + 1)(r_e + R_E \parallel r_o \parallel R_L)]}{R_B \parallel [(\beta + 1)(r_e + R_E \parallel r_o \parallel R_L)] + R_{\text{sig}}} \quad (12)$$

We can observe directly that each of the two factors in this expression is less than one, so this overall small-signal voltage gain is **less than unity**.

In the **special instance** that  $r_o \gg R_E \parallel R_L$  then (12) simplifies to

$$G_v \approx \frac{R_E \parallel R_L}{R_E \parallel R_L + r_e} \frac{R_B \parallel [(\beta + 1)(r_e + R_E \parallel R_L)]}{R_B \parallel [(\beta + 1)(r_e + R_E \parallel R_L)] + R_{\text{sig}}} \quad (13)$$

and if  $R_B \gg (\beta + 1)(r_e + R_E \parallel R_L)$  then this further simplifies to

$$G_v \approx \frac{R_E \parallel R_L}{r_e + R_E \parallel R_L + \frac{R_{\text{sig}}}{\beta + 1}} \quad (14)$$

We see from this expression that under the above two assumptions and a third  $R_E \parallel R_L \gg r_e + R_{\text{sig}}/(\beta + 1)$ , the small-signal voltage gain is less than but approximately equal to one. This means that

$$G_v \equiv \frac{v_o}{v_{\text{sig}}} \lesssim 1 \quad \text{or} \quad v_o \lesssim v_{\text{sig}} \quad (15)$$

Because of this result, the common collector amplifier is also called an **emitter follower amplifier**.

- Overall small-signal current gain,  $G_i$ . By definition

$$G_i \equiv \frac{i_o}{i_i} \quad (16)$$

Using current division at the output of the small-signal equivalent circuit above

$$i_o = \frac{r_o \parallel R_E}{r_o \parallel R_E + R_L} i_e = \frac{r_o \parallel R_E}{r_o \parallel R_E + R_L} (\beta + 1) i_b \quad (17)$$

while using current division at the input

$$i_b = \frac{R_B}{R_B + R_{ib}} i_i \quad (18)$$

Substituting this into (17) gives

$$i_o = \frac{r_o \parallel R_E}{r_o \parallel R_E + R_L} (\beta + 1) \frac{R_B}{R_B + R_{ib}} i_i \quad (19)$$

from which we find that

$$G_i \equiv \frac{i_o}{i_i} = \frac{(\beta + 1)(r_o \parallel R_E)R_B}{(r_o \parallel R_E + R_L)(R_B + R_{ib})} \quad (20)$$

or 
$$G_i = \frac{(\beta + 1)(r_o \parallel R_E)R_B}{(r_o \parallel R_E + R_L) \left[ R_B + (\beta + 1)(r_e + R_E \parallel R_L) \right]} \quad (21)$$

- Short circuit current gain,  $A_{is}$ . In the case of a short circuit load ( $R_L = 0$ ),  $G_i$  in (21) reduces to the **short circuit current gain**:

$$A_{is} = \frac{i_{os}}{i_i} = \frac{(\beta + 1)R_B}{R_B + (\beta + 1)r_e} \quad (22)$$


In the case that  $R_B \gg (\beta + 1)(r_e + R_E \parallel R_L) = (\beta + 1)r_e$ , as was used earlier, then

$$A_{is} \approx \beta + 1 \quad (23)$$

which can be very large.

So even though the amplifier has a voltage gain less than one (and approaching one in certain circumstances), it has a very large small-signal current gain. Overall, the amplifier can provide **power gain** to the AC signal.

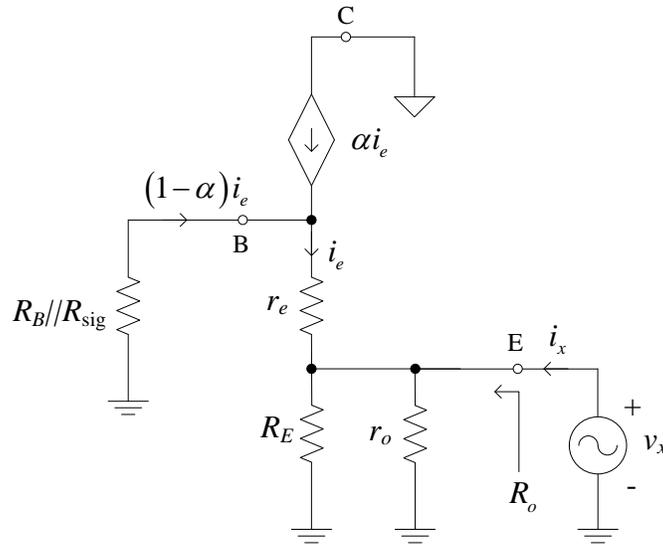- Output resistance,  $R_o$ . With  $v_{sig} = 0$  in the small-signal equivalent circuit, we're left with



It is a bit difficult to determine  $R_o$  directly from this circuit because of the dependent current source. The [trick](#) here is to apply a signal source  $v_x$  and then determine  $i_x$ . The output resistance is computed from the ratio of these quantities as

$$R_o \equiv \frac{v_x}{i_x} \quad (24)$$

Applying KVL from the output through the input of this circuit gives

$$\begin{aligned} v_x &= -i_e r_e - (1 - \alpha) i_e (R_{\text{sig}} \parallel R_B) \\ &= -i_e \left[ (1 - \alpha) (R_{\text{sig}} \parallel R_B) + r_e \right] \end{aligned} \quad (25)$$

Using KCL at the output

$$i_x = \frac{v_x}{r_o \parallel R_E} - i_e \quad (26)$$

Substituting (26) into (25)

$$v_x = \left( i_x - \frac{v_x}{r_o \parallel R_E} \right) \left[ (1-\alpha)(R_{\text{sig}} \parallel R_B) + r_e \right]$$

$$v_x \left[ 1 + \frac{(1-\alpha)(R_{\text{sig}} \parallel R_B) + r_e}{r_o \parallel R_E} \right] = i_x \left[ (1-\alpha)(R_{\text{sig}} \parallel R_B) + r_e \right] \quad (27)$$

Forming the ratio of  $v_x$  and  $i_x$  in (27) gives

$$R_o = \frac{v_x}{i_x} = \frac{(1-\alpha)(R_{\text{sig}} \parallel R_B) + r_e}{1 + \frac{(1-\alpha)(R_{\text{sig}} \parallel R_B) + r_e}{r_o \parallel R_E}}$$

or

$$R_o = \frac{(r_o \parallel R_E) \left[ (1-\alpha)(R_{\text{sig}} \parallel R_B) + r_e \right]}{r_o \parallel R_E + (1-\alpha)(R_{\text{sig}} \parallel R_B) + r_e}$$

such that  $R_o = (r_o \parallel R_E) \parallel \left[ (1-\alpha)(R_{\text{sig}} \parallel R_B) + r_e \right]$

This is equivalent to

$$R_o = (r_o \parallel R_E) \parallel \left( \frac{R_{\text{sig}} \parallel R_B}{\beta + 1} + r_e \right) \quad (7.161), (28)$$

In the case  $r_o \parallel R_E$  is “large”, then

$$R_o \approx \frac{R_{\text{sig}} \parallel R_B}{\beta + 1} + r_e \quad (29)$$

which is generally **relatively small**.

## Summary

Summary of the CC (emitter follower) small-signal amplifier:

1. High input resistance.
2.  $G_v$  less than one, and can be close to one.
3.  $A_{is}$  can be large.
4. Low output resistance.

These characteristics mean that the emitter follower amplifier is highly suited as a **voltage buffer amplifier**.