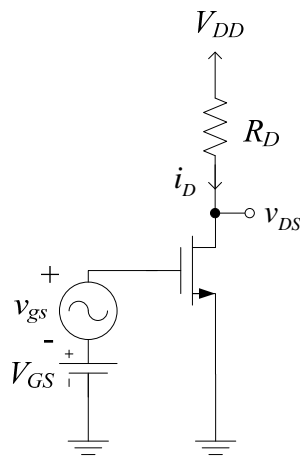


## Lecture 28: MOSFET as an Amplifier. Small-Signal Equivalent Circuit Models.

As with the BJT, we can use MOSFETs as **AC small-signal amplifiers**. An example is the so-called conceptual MOSFET amplifier shown in Fig. 7.2:



(Fig. 7.2)

This is only a “conceptual” amplifier for **two** primary reasons:

1. The bias with  $V_{GS}$  is impractical. (Will consider others later.)
2. In ICs, resistors take up too much room. (Would use another triode-region biased MOSFET in lieu of  $R_D$ .)

To operate as a small-signal amplifier, we bias the MOSFET in the saturation region. For the analysis of the DC operating point, we set  $v_{gs} = 0$  so that from (7.25) with  $\lambda = 0$

$$i_D = \frac{1}{2} k_n' \frac{W}{L} (v_{GS} - V_t)^2 \quad (7.25), (1)$$

From the circuit 
$$V_{DS} = V_{DD} - I_D R_D \quad (7.26), (2)$$

For operation in the saturation region

$$v_{GD} \leq V_t \Rightarrow v_{GS} - v_{DS} \leq V_t$$

or

$$v_{DS} \geq v_{GS} - V_t \quad (3)$$

where the total drain-to-source voltage is

$$v_{DS} = \underbrace{V_{DS}}_{\text{bias}} + \underbrace{v_{ds}}_{\text{AC}}$$

Similar to what we saw with BJT amplifiers, we need make sure that (3) is satisfied for the **entire signal swing** of  $v_{ds}$ .

With an AC signal applied at the gate

$$v_{GS} = V_{GS} + v_{gs} \quad (7.27),(4)$$

Substituting (4) into (1)

$$i_D = \frac{1}{2} k_n' \frac{W}{L} (V_{GS} + v_{gs} - V_t)^2 = \frac{1}{2} k_n' \frac{W}{L} [(V_{GS} - V_t) + v_{gs}]^2 \quad (5)$$

$$= \frac{1}{2} k_n' \frac{W}{L} (V_{GS} - V_t)^2 + \frac{2}{2} k_n' \frac{W}{L} (V_{GS} - V_t) v_{gs} + \frac{1}{2} k_n' \frac{W}{L} v_{gs}^2 \quad (7.28),(6)$$

$$\begin{array}{l} = I_D \text{ (DC)} \\ \text{(time varying)} \end{array}$$

The last term in (6) is **nonlinear** in  $v_{gs}$ , which is undesirable for a linear amplifier. Consequently, for linear operation we will require that the last term be “small”:

$$\frac{1}{2} k_n' \frac{W}{L} v_{gs}^2 \ll k_n' \frac{W}{L} (V_{GS} - V_t) v_{gs}$$

or

$$\underline{v_{gs} \ll 2(V_{GS} - V_t)} \quad (7.29),(7)$$

If this small-signal condition (7) is satisfied, then from (6) the total drain current is approximately the **linear summation**

$$i_D \approx \underbrace{I_D}_{\text{DC}} + \underbrace{i_d}_{\text{AC}} \quad (7.31),(8)$$

where

$$i_d = k_n' \frac{W}{L} (V_{GS} - V_t) v_{gs}. \quad (9)$$

From this expression (9) we see that the AC drain current  $i_d$  is related to  $v_{gs}$  by the so-called **transistor transconductance,  $g_m$** :

$$g_m \equiv \frac{i_d}{v_{gs}} = k_n' \frac{W}{L} (V_{GS} - V_t) \text{ [S]} \quad (7.32),(10)$$


which is sometimes expressed in terms of the **overdrive voltage**  $V_{OV} \equiv V_{GS} - V_t$

$$g_m = k_n' \frac{W}{L} V_{OV} \text{ [S]} \quad (7.33),(11)$$

Because of the  $V_{GS}$  term in (10) and (11), this  $g_m$  **depends on the bias**, which is just like a BJT.

Physically, this transconductance  $g_m$  equals the **slope** of the  $i_D$ - $v_{GS}$  characteristic curve at the Q point:

$$g_m \equiv \left. \frac{\partial i_D}{\partial v_{GS}} \right|_{v_{GS}=V_{GS}} \quad (7.34),(12)$$

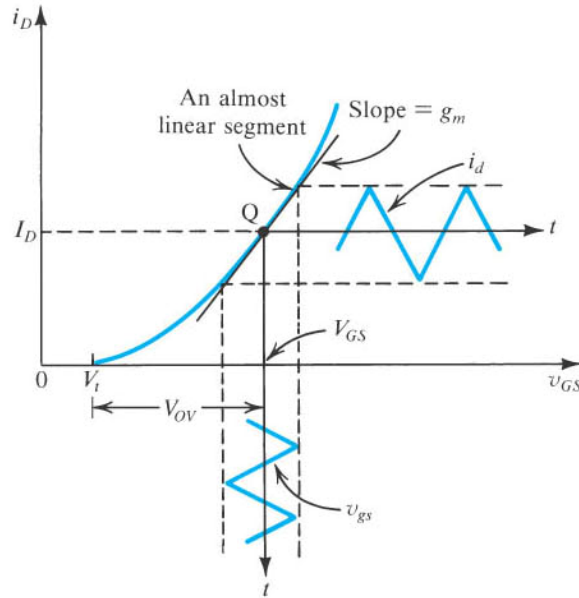

(Fig. 7.11)

Lastly, it can be easily show that for this conceptual amplifier in Fig. 7.2,


$$A_v \equiv \frac{v_{ds}}{v_{gs}} = -g_m R_D \quad (7.36), (13)$$

Consequently,  $A_v \propto g_m$ , which is the same result we found for a similar BJT conceptual amplifier [see (7.78)].

## MOSFET Small-Signal Equivalent Models

For circuit analysis, it is convenient to use equivalent small-signal models for MOSFETs – as it was with BJTs.

In the saturation mode, the MOSFET acts as a **voltage controlled current source**. The control voltage is  $v_{gs}$  and the output current is  $i_d$ , which gives rise to this small-signal  $\pi$  model:

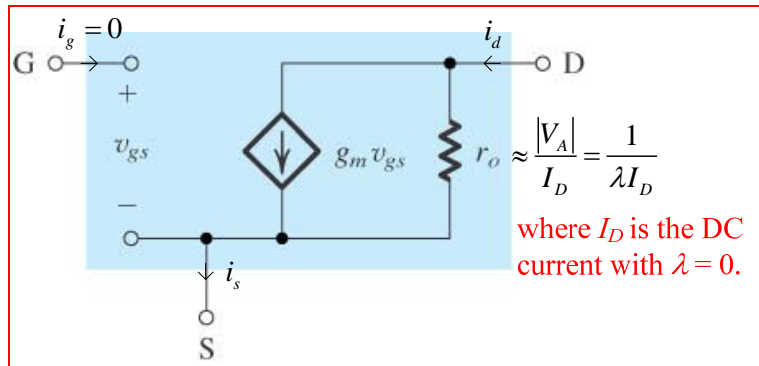

(Fig. 7.13b)

Things to note from this small-signal model include:

1.  $i_g = 0$  and  $v_{gs} \neq 0 \Rightarrow$  infinite input impedance.
2.  $r_o$  models the finite output resistance. Practically speaking, it will range from  $\approx 10 \text{ k}\Omega \rightarrow 1 \text{ M}\Omega$ . Note that it depends on the bias current  $I_D$ .
3. From (10) we found

$$g_m = k_n' \frac{W}{L} (V_{GS} - V_t) \quad (14)$$


Alternatively, it can be shown that

$$g_m = \frac{2I_D}{V_{OV}} = \frac{I_D}{(V_{GS} - V_t) / 2} \quad (7.42), (15)$$

which is similar to  $g_m = I_C / V_T$  for BJTs.

One big difference from BJTs is  $V_T \approx 25 \text{ mV}$  while  $V_{eff} = 0.1 \text{ V}$  or greater. Hence, for the same bias current  $g_m$  is much larger for **BJTs** than for MOSFETs.

A small-signal **T model** for the MOSFET is shown in Fig. 7.17:

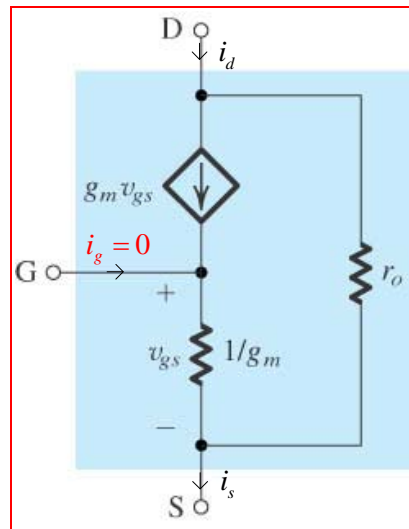

(Fig. 7.17a)

Notice the direct connection between the gate and both the dependent current source and  $1/g_m$ . While this model is correct, we've **added the explicit boundary condition that  $i_g = 0$**  to this small-signal model.


It isn't necessary to do this because the currents in the two vertical branches are both equal to  $g_m v_{gs}$ , which means  $i_g = 0$ . But adding this condition  $i_g = 0$  to the small-signal model in Fig. 7.17a makes this explicit in the circuit calculations. (The T model usually shows this direct connection while the  $\pi$  model usually doesn't.)

MOSFETs have **many advantages** over BJTs including:

1. High input resistance
2. Small physical size
3. Low power dissipation
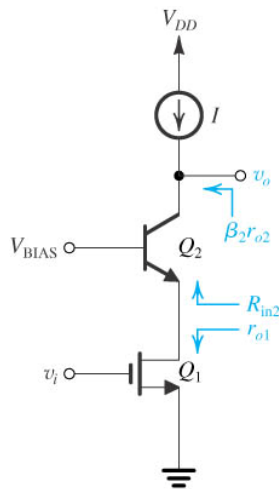
#### 4. Relative ease of fabrication.

One can **combine** advantages of both technologies (BJT and MOSFET) into what are called BiCMOS amplifiers:



(Sedra and Smith, 5<sup>th</sup> ed.)

Such a combination provides a very large input resistance from the MOSFET and a large output impedance from the BJT.