

Lecture 10: Non-ideal Behavior of Physical Circuit Elements. Skin Effect.

At “low” frequencies (say $\lesssim 1$ MHz), physical resistors, capacitors, and inductors usually have terminal characteristics nearly identical to ideal theoretical prediction.


However, at “high” frequencies (say $\gtrsim 100$ MHz), resistor, capacitor, and inductor circuit elements **can behave very differently than expected**.

We will consider in this lecture the frequency behavior of these three circuit elements as well as the current density distribution across a round wire at high frequencies.

Non-Ideal Resistor

The **leads** of the resistor **create an inductance L_{lead} and a capacitance C_{par}** (for “parasitic”). Additional capacitance from the resistor body can also contribute.

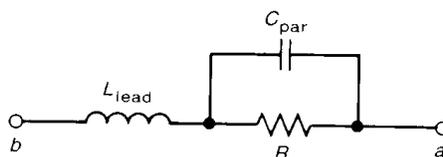An **equivalent circuit** representation for a physical resistor is:



Measured frequency response of a 1-k Ω carbon resistor with ¼” lead lengths:

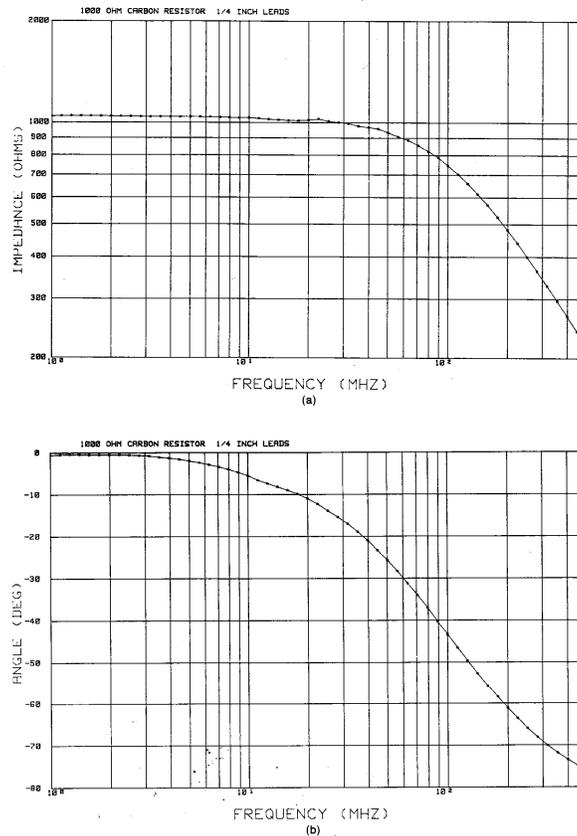


FIGURE 6.19 Measured impedance of a 1000 Ω , carbon resistor having ¼ inch lead lengths: (a) magnitude; (b) phase.


(C. R. Paul, *Introduction to Electromagnetic Compatibility*. New York: John Wiley & Sons, 1992.)

Non-Ideal Capacitor

The leads of the capacitor create an inductance L_{lead} and a capacitance C_{par} . It may often be the case that the C of the capacitor is so large that C_{par} can be ignored.

The resistance of the leads and the conduction current **through** the dielectric of the capacitor can be modeled by a resistance R_s (which should be very large).

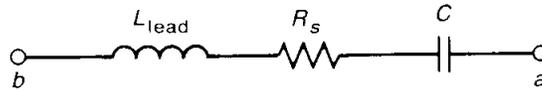An equivalent circuit representation for a physical capacitor:



Measured frequency response of a 470-pF ceramic capacitor with essentially no lead lengths:

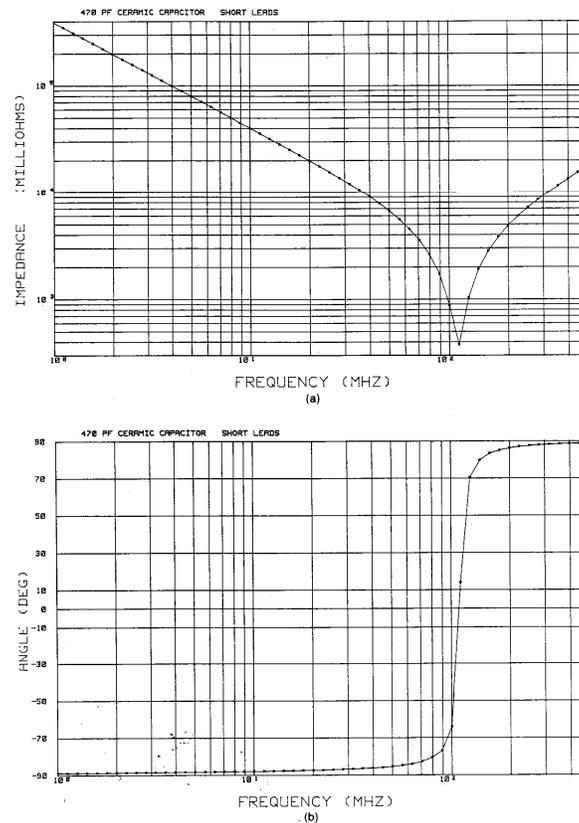


FIGURE 6.25 Measured impedance of a 470 pF ceramic capacitor with short lead lengths: (a) magnitude; (b) phase.


(C. R. Paul, *Introduction to Electromagnetic Compatibility*. New York: John Wiley & Sons, 1992.)

Non-Ideal Inductor

The leads of the inductor create a resistance as well as an inductance. However, both of these are usually much smaller than the resistance of the windings R_{par} and the inductance L of the inductor.

Additionally, a parasitic capacitance C_{par} between turns of wire in the windings is also present.

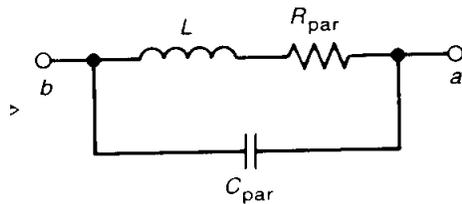An equivalent circuit representation for a physical inductor:



Measured frequency response of a 1.2- μH inductor with “very short” lead lengths:

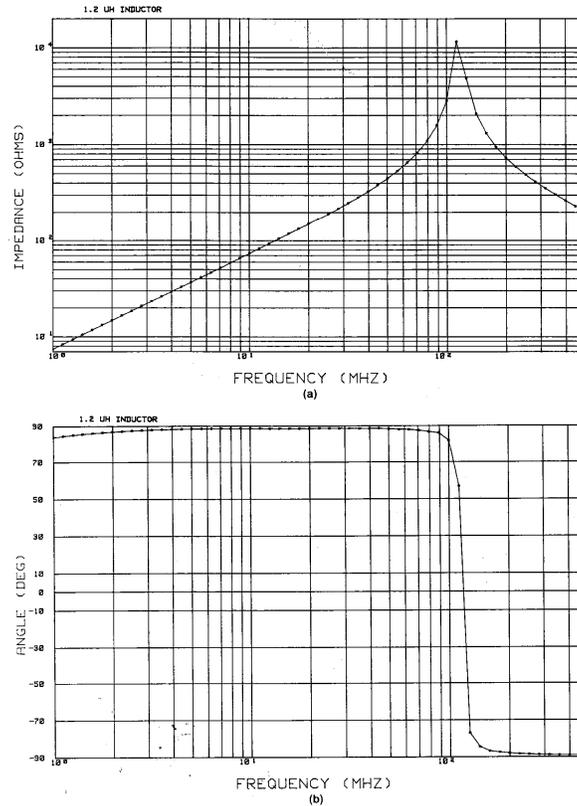


FIGURE 6.32 Measured impedance of a 1.2 μH inductor having very short lead lengths: (a) magnitude; (b) phase.


(C. R. Paul, *Introduction to Electromagnetic Compatibility*. New York: John Wiley & Sons, 1992.)

Skin Effect

On a related topic, you've likely seen in EE 381 that the **current density is uniform** over the cross section of a wire that is supporting a **direct current**.

It was likely mentioned then that this behavior is not present at higher frequencies. Shown in the figure below is the behavior of

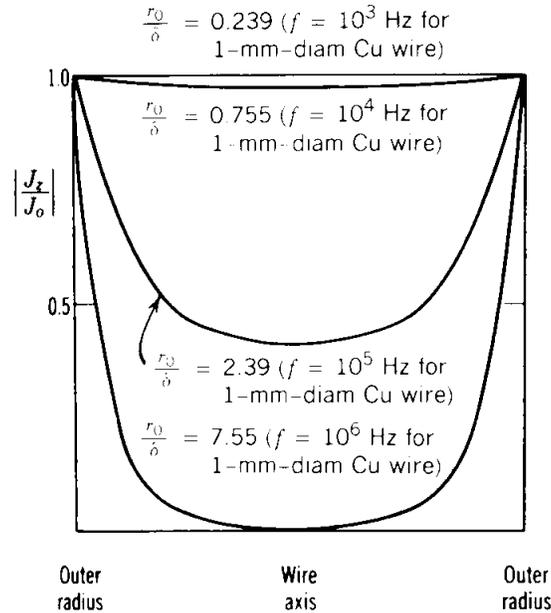the current density in a 1-mm diameter copper wire at four frequencies (1 kHz, 10 kHz, 100 kHz, and 1 MHz.)



(S. Ramo, J. R. Whinnery and T. Van Duzer, *Fields and Waves in Communication Electronics*. New York: John Wiley & Sons, third ed., 1994.)

As the frequency increases, the current density becomes concentrated near the outer surface of the round wire. This behavior of the current density is called the “**skin effect**”.