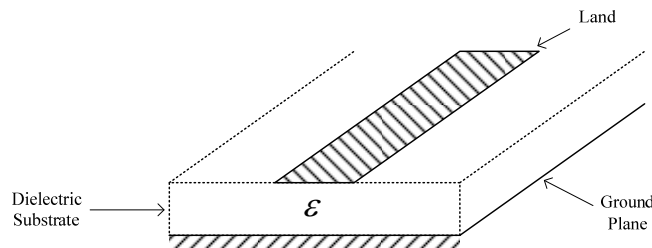



Lecture 2: Telegrapher Equations For Transmission Lines. Power Flow.

Microstrip is one method for making electrical connections in a microwave circuit. It is constructed with a ground plane on one side of a PCB and “lands” on the other:



Microstrip is an example of a **transmission line**, though technically it is only an approximate model for microstrip, as we will see later in this course.

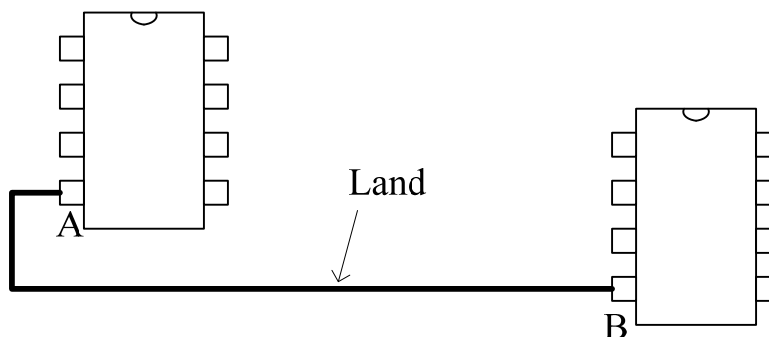Why TLs? Imagine two ICs are connected together as shown:



When the voltage at A changes state, does that new voltage appear at B instantaneously? No, of course not.

If these two points are separated by a large electrical distance, there will be a **propagation delay** as the change in state (electrical signal) travels to B. Not an instantaneous effect.

In microwave circuits, even distances as small as a few inches may be “far” and the propagation delay for a voltage signal to appear at another IC may be significant.

This propagation of voltage signals is modeled as a “**transmission line**” (TL). We will see that **voltage and current can propagate along a TL as waves**! Fantastic.

The transmission line model can be used to solve many, many types of high frequency problems, either exactly or approximately:

- Coaxial cable.
- Two-wire.
- Microstrip, stripline, coplanar waveguide, etc.

All true TLs share one common characteristic: the \vec{E} and \vec{H} fields are all perpendicular to the direction of propagation, which is the long axis of the geometry. These are called **TEM fields** for transverse electric and magnetic fields.

An excellent example of a TL is a coaxial cable. On a TL, the **voltage and current vary along the structure in time t and**

spatially in the z direction, as indicated in the figure below. There are no instantaneous effects.


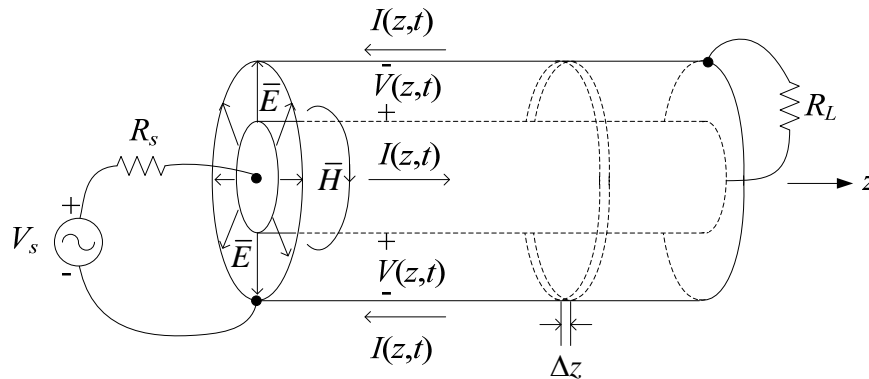



Fig. 1

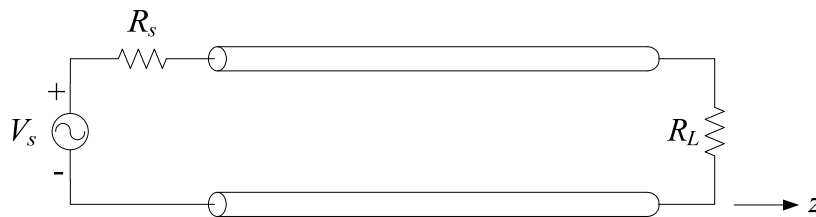A common **circuit symbol** for a TL is the two-wire (parallel) symbol to indicate any transmission line. For example, the equivalent circuit for the coaxial structure shown above is:



Analysis of Transmission Lines

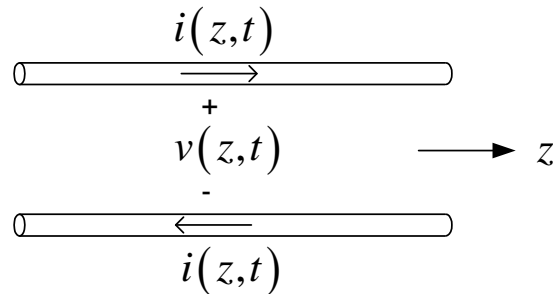As mentioned, on a TL the voltage and current vary along the structure in time (t) and in distance (z), as indicated in the figure above. **There are no instantaneous effects.**



How do we solve for $v(z,t)$ and $i(z,t)$? We first need to develop the governing equations for the voltage and current, and then solve these equations.

Notice in Fig. 1 above that there is **conduction current** in the center conductor and outer shield of the coaxial cable, and a **displacement current** between these two conductors where the electric field \bar{E} is varying with time. **Each of these currents has an associated impedance:**

- Conduction current impedance effects:
 - **Resistance**, R , due to losses in the conductors,
 - **Inductance**, L , due to the current in the conductors and the magnetic flux linking the current path.
- Displacement current impedance effects:
 - **Conductance**, G , due to losses in the dielectric between the conductors,
 - **Capacitance**, C , due to the time varying electric field between the two conductors.

To develop the governing equations for $V(z,t)$ and $I(z,t)$, we will consider only a **small section** Δz of the TL. This Δz is so

small that the **electrical effects are occurring instantaneously and we can simply use circuit theory** to draw the relationships between the conduction and displacement currents. This equivalent circuit is shown below:


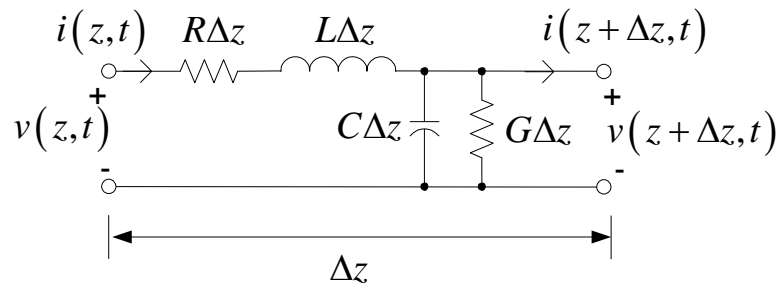


Fig. 2

The variables R , L , C , and G are **distributed** (or **per-unit length**, PUL) **parameters** with units of Ω/m , H/m , F/m , and S/m , respectively. We will sometimes ignore losses in this course.

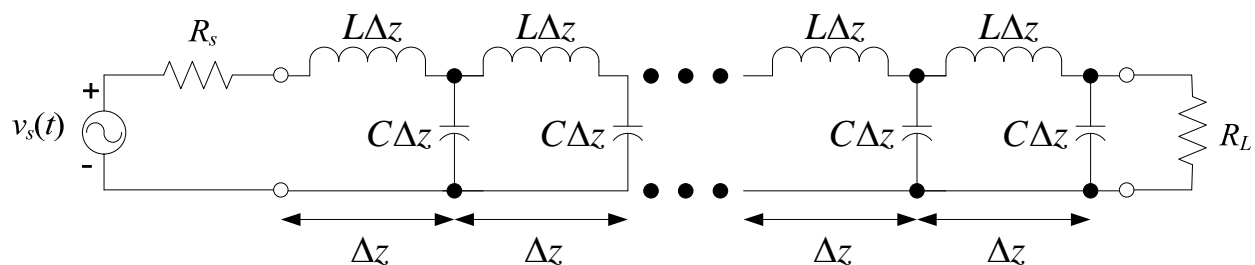A finite length of TL can be constructed by cascading many, many of these subsections along the total length of the TL. In the case of a lossless TL where $R = G = 0$ this cascade appears as:



This is a **general model**: it applies to **any TL** regardless of its cross sectional shape provided the actual electromagnetic field is TEM.

However, the PUL-parameter values change depending on the **specific geometry** (whether it is a microstrip, stripline, two-wire, coax, or other geometry) and the construction materials.

Transmission Line Equations

To develop the governing equation for $v(z,t)$, apply KVL in Fig. 2 above (ignoring losses)

$$v(z,t) = L\Delta z \frac{\partial i(z,t)}{\partial t} + v(z + \Delta z, t) \quad (2.1a),(1)$$

Similarly, for the current $i(z,t)$ apply KCL at the node

$$i(z,t) = C\Delta z \frac{\partial v(z + \Delta z, t)}{\partial t} + i(z + \Delta z, t) \quad (2.1b),(2)$$

Then:

1. Divide (1) by Δz :

$$\frac{v(z + \Delta z, t) - v(z, t)}{\Delta z} = -L \frac{\partial i(z, t)}{\partial t} \quad (3)$$

In the limit as $\Delta z \rightarrow 0$, the term on the LHS in (3) is the **forward difference definition** of derivative. Hence,

$$\boxed{\frac{\partial v(z, t)}{\partial z} = -L \frac{\partial i(z, t)}{\partial t}} \quad (2.2a),(4)$$

2. Divide (2) by Δz :

$$\frac{i(z + \Delta z, t) - i(z, t)}{\Delta z} = -C \frac{\partial v(z + \Delta z, t)}{\partial t} \quad (5)$$

Again, in the limit as $\Delta z \rightarrow 0$ the term on the LHS is the forward difference definition of derivative. Hence,

$$\boxed{\frac{\partial i(z, t)}{\partial z} = -C \frac{\partial v(z, t)}{\partial t}} \quad (2.2b), (6)$$

Equations (4) and (6) are a pair of coupled first order partial differential equations (PDEs) for $v(z, t)$ and $i(z, t)$. These two equations are called the **telegrapher equations** or the **transmission line equations**.

Recap: We expect that v and i are not constant along microwave circuit interconnects. Rather, (4) and (6) dictate how v and i vary along the TL at all times.

TL Wave Equations

We will now combine (4) and (6) in a special way to form two equations, each a function of v or i only.

To do this, take $\frac{\partial}{\partial z}$ of (4) and $\frac{\partial}{\partial t}$ of (6):

- $\frac{\partial}{\partial z}$ (4):
$$\frac{\partial^2 v(z, t)}{\partial z^2} = -L \frac{\partial^2 i(z, t)}{\partial z \partial t} \quad (7)$$

- $\frac{\partial}{\partial t}$ (6):
$$\frac{\partial^2 i(z,t)}{\partial t \partial z} = -C \frac{\partial^2 v(z,t)}{\partial t^2} \quad (8)$$

Substituting (8) into (7) gives:

$$\frac{\partial^2 v(z,t)}{\partial z^2} = LC \frac{\partial^2 v(z,t)}{\partial t^2} \quad (9)$$

Similarly,

$$\frac{\partial^2 i(z,t)}{\partial z^2} = LC \frac{\partial^2 i(z,t)}{\partial t^2} \quad (10)$$

Equations (9) and (10) are the governing equations for the z and t dependence of v and i . These are very special equations. In fact, they are **wave equations** for v and i !

We will define the **(phase) velocity** of these waveforms as

$$v_p = \frac{1}{\sqrt{LC}} \quad [\text{m/s}] \quad (2.16)$$

so that (9) becomes

$$\frac{\partial^2 v(z,t)}{\partial z^2} = \frac{1}{v_p^2} \frac{\partial^2 v(z,t)}{\partial t^2} \quad (11)$$

Voltage Wave Equation Solutions


There are two **general solutions** to (11):

1. $v(z,t) = v_+ \left(t - \frac{z}{v_p} \right) \quad (12)$

v_+ is any twice-differentiable function that contains t , z , and v_p in the form of the argument shown. It can be verified that (12) is a solution to (11) by substituting (12) into (11) and showing that the LHS equals the RHS.

Equation (12) represents a wave traveling in the $+z$ direction with **speed** $v_p = 1/\sqrt{LC}$ m/s.

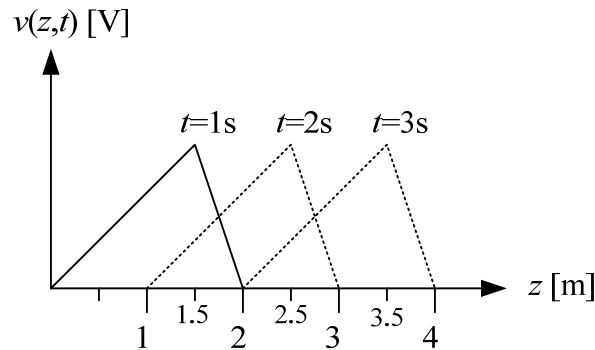To see this, consider the example below with $v_p = 1$ m/s:



At $t = 1$ s, focus on the peak located at $z = 1.5$ m. Then,

$$s_+ \equiv t - \frac{z}{v_p} = 1 - \frac{1.5}{1} = -0.5$$

The argument s_+ stays **constant** for varying t and z . Therefore, at $t = 2$ s, for example, then

$$s_+ = -0.5 = t - \frac{z}{v_p}$$

Therefore,

$$z = 2.5 \text{ m}$$

So the peak has now moved to position $z = 2.5$ m at $t = 2$ s.

Likewise, every point on this function moves the same distance (1 m) in this time (1 s). This is called **wave motion**.

The speed of this movement is

$$\frac{\Delta z}{\Delta t} = \frac{1 \text{ m}}{1 \text{ s}} = 1 \frac{\text{m}}{\text{s}} = v_p$$

$$2. v(z, t) = v_- \left(t + \frac{z}{v_p} \right) \quad (13)$$

This is the second general solution to (11). This function v_- represents a wave moving in the $-z$ direction with speed v_p .

The complete solution to the wave equation (11) is the sum of (12) and (13)

$$v(z, t) = v_+ \left(t - \frac{z}{v_p} \right) + v_- \left(t + \frac{z}{v_p} \right) \quad (14)$$

v_+ and v_- can be any suitably differentiable functions, but with arguments as shown.

Current Wave Equation Solutions

A similar analysis can be performed for current waves on the TL. The governing equation for $i(z, t)$ is

$$\frac{\partial^2 i(z, t)}{\partial z^2} = \frac{1}{v_p^2} \frac{\partial^2 i(z, t)}{\partial t^2} \quad (15)$$

The complete general solution to this **current wave equation** can be determined in a manner similar to the voltage as

$$i(z, t) = \underbrace{i_+ \left(t - \frac{z}{v_p} \right)}_{+z \text{ wave}} + \underbrace{i_- \left(t + \frac{z}{v_p} \right)}_{-z \text{ wave}} \quad (16)$$

Furthermore, the function i_+ can be **related** to the function v_+ and i_- can be related to v_- .

For example, substituting $i_+ \left(t - \frac{z}{v_p} \right)$ and $v_+ \left(t - \frac{z}{v_p} \right)$ into (6), differentiating then integrating gives

$$-\frac{1}{v_p} i_+ = -C v_+$$

or

$$i_+ = v_p C v_+ \quad (17)$$

But,

$$v_p C = \frac{1}{\sqrt{LC}} C = \sqrt{\frac{C}{L}}$$

We will define

$$Z_0 \equiv \sqrt{\frac{L}{C}} \quad [\Omega] \quad (2.13), (18)$$

as the **characteristic impedance** of the transmission line. (Note that in some texts, Z_0 is denoted as R_c , the characteristic resistance of the TL).

With (18), (17) can be written as

$$i_+ \left(t - \frac{z}{v_p} \right) = \frac{v_+ \left(t - \frac{z}{v_p} \right)}{Z_0} \quad (19)$$

Similarly, it can be shown that

$$i_- \left(t + \frac{z}{v_p} \right) = -\frac{v_- \left(t + \frac{z}{v_p} \right)}{Z_0} \quad (20)$$

The minus sign results since the current is in the $-z$ direction.

Finally, substituting (19) and (20) into (16) gives

$$i(z, t) = \frac{1}{Z_0} v_+ \left(t - \frac{z}{v_p} \right) - \frac{1}{Z_0} v_- \left(t + \frac{z}{v_p} \right) \quad (21)$$

This equation as well as (14)

$$v(z, t) = v_+ \left(t - \frac{z}{v_p} \right) + v_- \left(t + \frac{z}{v_p} \right) \quad (22)$$

are the **general wave solutions** for v and i on a transmission line.

Power Flow

These voltage and current waves transport power along the TL.

The **power flow** carried by the forward wave $p_+(z, t)$ is

$$p_+(z, t) = v_+(z, t) i_+(z, t) = \frac{v_+^2(z, t)}{Z_0} \quad (23)$$

which is positive indicating power flows in the $+z$ direction.

Similarly, the power flow of the reverse wave is

$$p_-(z,t) = v_-(z,t)i_-(z,t) = -\frac{v_-^2(z,t)}{Z_0} \quad (24)$$

which is negative indicating power flows in the $-z$ direction.