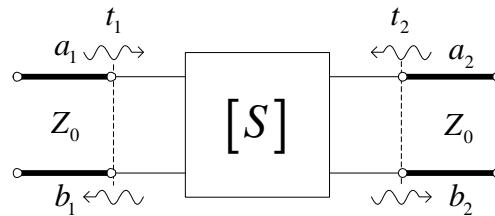


## Lecture 21: Signal Flow Graphs.

Consider the following two-port network (Fig 4.14a):




(Fig. 1)

A **signal flow graph** is a diagram depicting certain relationships between signals in a **linear** network. It can also be used to solve for ratios of these signals.

Signal flow graphs are used in control systems, power systems, and other fields besides microwave engineering.

**Key elements** of a signal flow graph are:

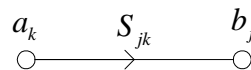1. Nodes represent the system variables,
2. Branches represent paths for signal flow.
3. A signal  $S_{jk}$  traveling along a branch between nodes  $a_k$  and  $b_j$  is multiplied by the gain of that branch:



That is,

$$b_j = S_{jk} a_k$$

4. Signals travel along branches only in the direction of the arrows.

This restriction exists so that a branch from  $a_k$  to  $b_j$  denotes a proportional dependence of  $b_j$  on  $a_k$ , but **not** the reverse.


5. Multiple branches into a node represent a summation of signals.

For example, referring to the two-port above, where

$$b_1 = S_{11}a_1 + S_{12}a_2$$

$$b_2 = S_{21}a_1 + S_{22}a_2$$

the signal flow graph is (Fig 4.14b):

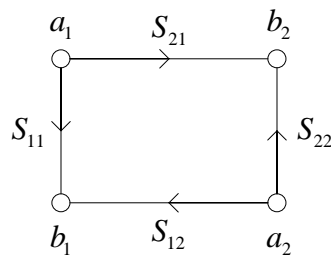

**(Fig. 2)**

The signals  $a_1$ ,  $a_2$ ,  $b_1$ , and  $b_2$  are denoted by nodes whereas certain interactions between the signals are denoted by the branches and the transmission factors ( $S$  parameters) of those branches.

## Construction of Signal Flow Graphs

Let's take a more careful look at the construction of the signal flow graph (SFG) in Fig. 2. Starting with the definition of the matrix description of the two port in Fig. 1

$$[b] = [S] \cdot [a] \quad (1)$$


or

$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} a_1 \\ a_2 \end{bmatrix} \quad (2)$$

The first equation in (2) is

$$b_1 = S_{11}a_1 + S_{12}a_2 \quad (3)$$

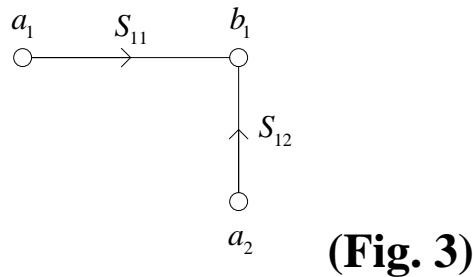
Using items 3 and 5 listed above, the SFG representation for (3) is



The second equation in (2) is

$$b_2 = S_{21}a_1 + S_{22}a_2 \quad (4)$$

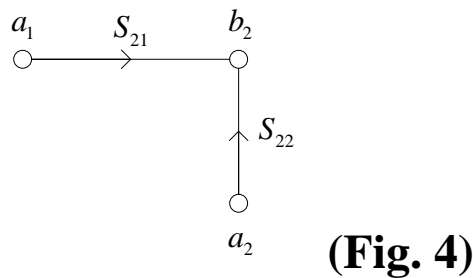Using items 3 and 5 listed above, the SFG representation for (4) is



Combining these two SFGs in Figs. 3 and 4 gives the overall SFG show earlier in Fig. 2.

If we wish to construct **just a single branch** of this signal flow graph we only need to **match the transmitted port**. For example, if  $a_2 = 0$ , we see from (3) and Fig. 3 that

$$b_1 = S_{11}a_1 \quad \Rightarrow \quad \begin{array}{c} a_1 \quad S_{11} \quad b_1 \\ \circ \longrightarrow \circ \end{array}$$

while from (4) and Fig. 4

$$b_2 = S_{21}a_1 \quad \Rightarrow \quad \begin{array}{c} a_1 \quad S_{21} \quad b_2 \\ \circ \longrightarrow \circ \end{array}$$

## Solving Signal Flow Graphs

Signal flow graphs can form an **intuitive picture** of the signal flow in a network. As an application, we will develop SFGs in the next lecture to help us calibrate out systematic errors present when we make measurements with a VNA.


Another useful characteristic is that we can **solve for ratios** of signals directly from a SFG using a simple graphical algebra.

There are **four rules** that form the algebra of SFGs:

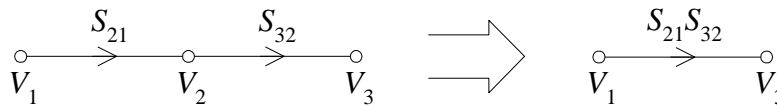**1. Series Rule.** Given the two proportional relations

$$\begin{array}{l} V_2 = S_{21}V_1 \quad \text{and} \quad V_3 = S_{32}V_2 \\ \text{then} \quad V_3 = (S_{32}S_{21})V_1 \end{array} \quad (4.75),(5)$$

In a SFG, this is represented as (Fig. 4.16a):




In other words, two series paths are equivalent to a single path with a transmission factor equal to a **product** of the two original transmission factors.

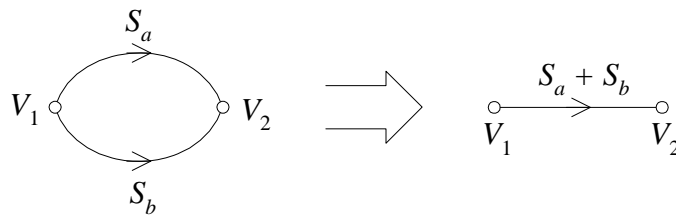**2. Parallel Rule.** Consider the relation:

$$V_2 = S_a V_1 + S_b V_1 = (S_a + S_b) V_1 \quad (4.76), (6)$$

In a SFG, this is represented as (Fig 4.16b):



In other words, two parallel paths are equivalent to a single path with a transmission factor equal to the **sum** of the original transmission coefficients.

**3. Self-Loop Rule.** Consider the relations

$$V_2 = S_{21} V_1 + S_{22} V_2 \quad (4.77a), (7)$$

and

$$V_3 = S_{32} V_2 \quad (4.77b), (8)$$


We will choose to eliminate  $V_2$  from these two equations.  
From (7)

$$V_2(1 - S_{22}) = S_{21}V_1 \Rightarrow V_2 = \frac{S_{21}}{1 - S_{22}}V_1$$

Substituting this into (8) gives

$$V_3 = \frac{S_{32}S_{21}}{1 - S_{22}}V_1 \quad (4.78),(9)$$

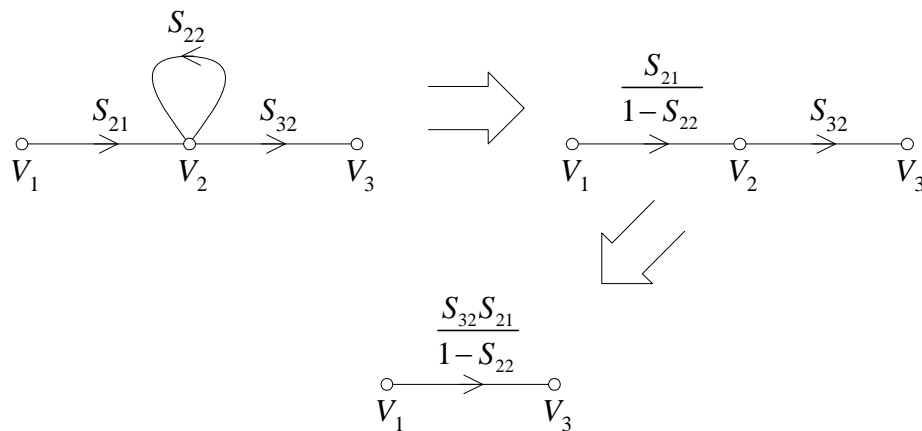In a SFG, this is represented as (Fig 4.16c):



In other words, a feedback loop may be eliminated by **dividing** the input transmission factor by one minus the transmission factor around the loop.

**4. Splitting Rule.** Consider the relationships:


$$V_4 = S_{42}V_2 \quad (10)$$

$$V_2 = S_{21}V_1 \quad (11)$$

and

$$V_3 = S_{32}V_2 \quad (12)$$


The SFG is

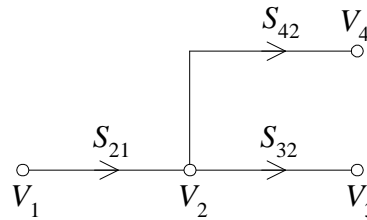

From (10) and (11) we find that  $V_4 = S_{42}S_{21}V_1$ . Hence, if we use the Series Rule “in reverse” we can define:


$$V_4 = S_{42}V_2' \quad \text{and} \quad V_2' = S_{21}V_1$$

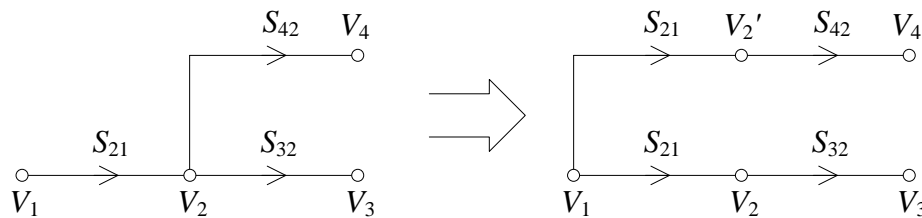In a SFG, this is represented as (Fig 4.16d):




In other words, a node can be **split** such that the product of transmission factors from input to output is unchanged.

**Example N21.1.** Construct a signal flow graph for the network shown below. Determine  $\Gamma_{in}$  and  $V_L$  using only SFG algebra.

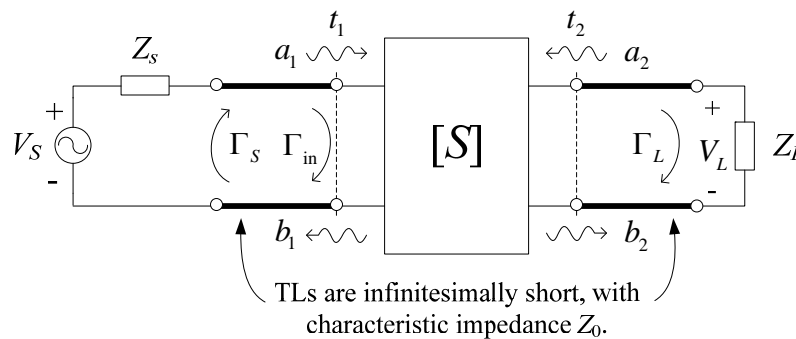

(Fig. 5)

The signal flow graph is:

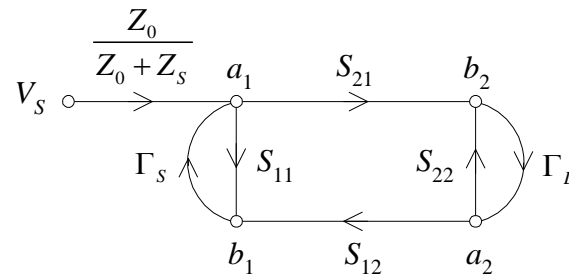

Notice the **arrow directions** for  $\Gamma_s$  and  $\Gamma_L$ . These are the correct orientations since

$$\Gamma_s = \frac{a_1}{b_1} \Rightarrow a_1 = \Gamma_s b_1$$

and

$$\Gamma_L = \frac{a_2}{b_2} \Rightarrow a_2 = \Gamma_L b_2$$

Also notice the branch relating  $V_S$  and  $a_1$  in Fig. 5. As mentioned near the beginning of this lecture, a single branch relationship between two nodes can be found by **matching the transmitted port**. In this case, we match the TL connected to the source  $V_S$  giving only a forward propagating wave with a voltage amplitude found from voltage division to be


$$a_1 = \frac{Z_0}{Z_0 + Z_s} V_S \quad (13)$$

We will systematically apply the four rules above to reduce this diagram to a form that will directly allow us to determine both  $\Gamma_{in}$  and  $V_L$ .




**Starting** this solution process is probably the most difficult part. The rest is fairly systematic.

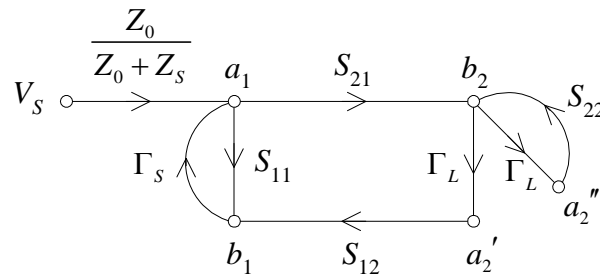**Step 1.** Start by splitting node  $a_2$  using Rule 4:




Why split the  $\Gamma_L$  branch and not the  $S_{22}$  branch? Because the  $\Gamma_L$  arrow is in the **same direction** as  $S_{12}$ .

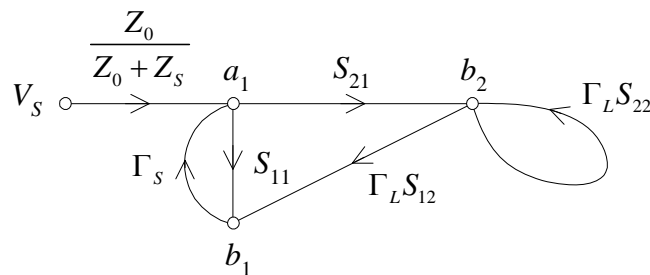
**Step 2.** Eliminate nodes  $a_2'$  and  $a_2''$  using Rule 1 twice:



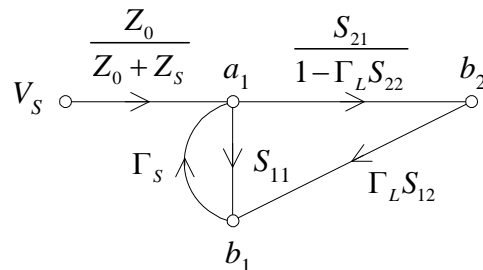
**Step 3.** Eliminate the self loop at  $b_2$  using Rule 3:



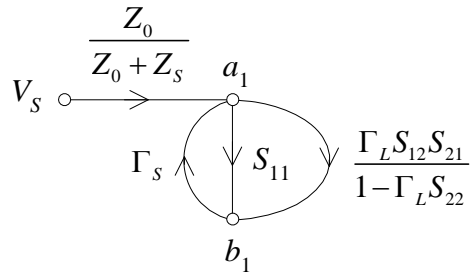**Step 4.** Eliminate node  $b_2$  using Rule 1:



**Step 5.** Apply Rule 2:

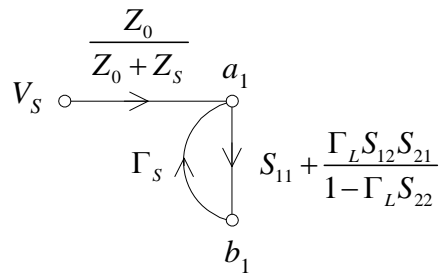

From this last diagram we can directly solve for  $\Gamma_{in}$ :

$$\Gamma_{in} \equiv \frac{b_1}{a_1} = S_{11} + \frac{\Gamma_L S_{12} S_{21}}{1 - \Gamma_L S_{22}} \quad (14)$$


Next, we will **determine the load voltage**  $V_L$ . The voltage on this TL can be expressed as  $V_2(z) = b_2(e^{-j\beta z} + \Gamma_L e^{j\beta z})$ . At the terminal plane  $z = 0$ , then

$$V_2(0) = V_L = b_2(1 + \Gamma_L) \quad (15)$$


In this expression,  $V_2(0) = V_L$  because the TL is very short.

So, we see from (15) that to find  $V_L$  we need to **determine**  $b_2$ . In Step 4, however, we eliminated that node. Let's start again from Step 3, but now split node  $b_1$ :

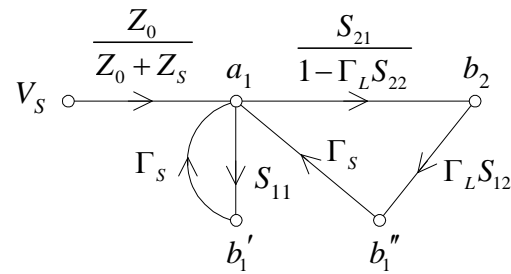
**Step 4'**. Split node  $b_1$  using Rule 4:



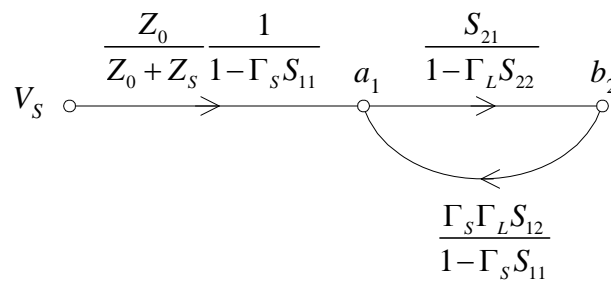
**Step 5'**. Next, we can use Rule 1, then Rule 3 (Self-Loop Rule) to all branches feeding node  $a_1$ :



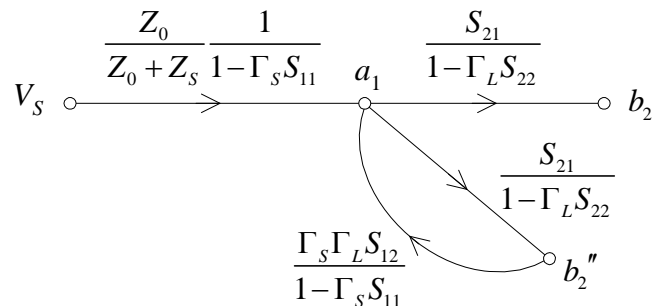**Step 6'**. Split node  $b_2$  using Rule 4:



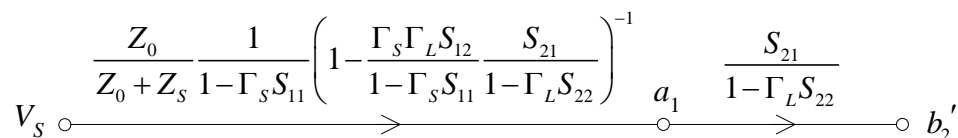**Step 7'**. Apply Rule 3 one last time to remove the self loop:



**Step 8'**. Using the Series Rule, we can now find  $b_2$  as:

$$\begin{aligned}
 b_2 &= \frac{Z_0}{Z_0 + Z_s} \frac{1}{1 - \Gamma_s S_{11}} \left[ \frac{(1 - \Gamma_s S_{11})(1 - \Gamma_L S_{22}) - \Gamma_s \Gamma_L S_{12} S_{21}}{(1 - \Gamma_s S_{11})(1 - \Gamma_L S_{22})} \right]^{-1} \frac{S_{21}}{1 - \Gamma_L S_{22}} V_s \\
 &= \frac{Z_0 S_{21} V_s (1 - \Gamma_s S_{11})(1 - \Gamma_L S_{22})}{(Z_0 + Z_s)(1 - \Gamma_s S_{11})[(1 - \Gamma_s S_{11})(1 - \Gamma_L S_{22}) - \Gamma_s \Gamma_L S_{12} S_{21}](1 - \Gamma_L S_{22})}
 \end{aligned}$$

or 
$$b_2 = \frac{Z_0 S_{21} V_s}{(Z_0 + Z_s) [(1 - \Gamma_s S_{11})(1 - \Gamma_L S_{22}) - \Gamma_s \Gamma_L S_{12} S_{21}]}$$

Using this  $b_2$ , we can determine  $V_L$  from (15) to be

$$V_L = \frac{Z_0 S_{21} (1 + \Gamma_L)}{(Z_0 + Z_s) [(1 - \Gamma_s S_{11})(1 - \Gamma_L S_{22}) - \Gamma_s \Gamma_L S_{12} S_{21}]} V_s$$

---

## Reference

R. E. Collin, *Foundations for Microwave Engineering*. New York: McGraw-Hill, second ed., 1992.