

# TL Resonators


Certain EM waveguiding structures can be used as resonators, and in some cases with extremely high  $Q$ 's. These are used in filters, oscillators, and material measurement systems. In the latter case, cavity-type resonators provide the highest accuracy measurements for low-loss materials.

Ref. Pozar 3rd ed.,  
Sections 6.1 & 6.2

## TL Resonators


Transmission lines can be constructed to operate as resonators when the "load" is an open or short circuit.

• Short-circuited TL -

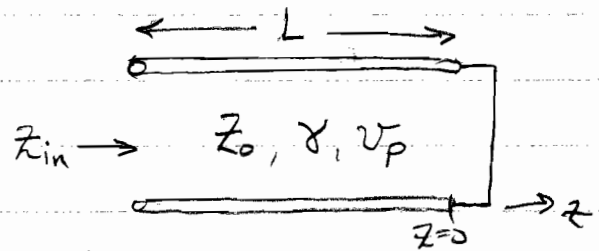

Since we're interested in the  $Q$ 's of this resonator as well as its resonance frequencies, we will include effects of small loss.


For a nearly lossless s.c. TL:

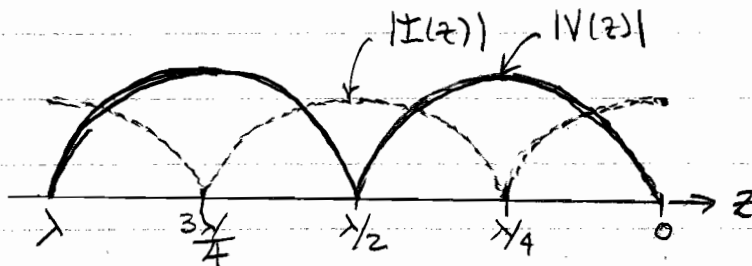


→ At  $z = \frac{n\lambda}{2}$ ,  $Z_{in} \approx 0$ ,  $n = 1, 2, 3, \dots$

→ At  $z = \frac{n\lambda}{4}$ ,  $Z_{in} \approx \infty$ ,  $n = 1, 3, 5, \dots$

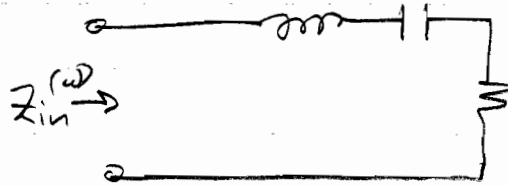Pozar shows that near the frequencies where  $L \approx \frac{n\lambda}{2}$ ,  $(n=1, 2, \dots)$ ,  $Z_{in}(\omega)$  has the form of a series resonant circuit:



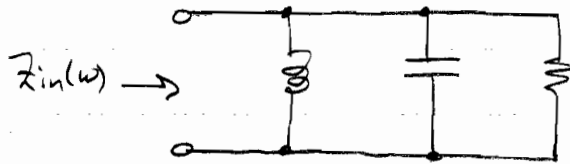while at the frequencies where  $L \approx \frac{n\lambda}{4}$ ,  $(n=1, 3, 5, \dots)$ ,  $Z_{in}(\omega)$  has the form of a parallel resonant circuit:



To estimate the  $Q$  of these resonators, we'll follow a different method than is traditionally used. We'll begin with the general definition of  $Q$  for <sup>a circuit in</sup> steady state:

$$Q = 2\pi \frac{\text{Max. energy stored at some time } t}{\text{Total energy lost per period}} \quad (1)$$

$$= 2\pi \frac{E_{\text{max}}}{P_a \cdot T}$$

$$\text{or } Q = \omega \frac{E_{\text{max}}}{P_a} \quad (2)$$

where  $P_a$  is average power dissipated in the circuit.

For a TL, where is the energy stored? Stored in the wave that is launched at the input & prop. down the TL to the end. (Once reflected & starts back, energy decreases)

With energy = power · time, then

$$E_{\max} = P_+ \cdot t_d = P_+ \frac{L}{v_p} \quad (3)$$

where  $P_+$  is power in forward wave &  $t_d$  is one way delay time (when energy max.)

To determine the average dissipated power, we know for the lossy TL that  $V^+ \propto e^{-\alpha L}$ , so that  $P_+ \propto (e^{-\alpha L})^2 = e^{-2\alpha L}$ . Therefore, the one-way dissipated power is

$$P_d = P_+ - P_+ e^{-2\alpha L} \quad (4)$$

if  $2\alpha L$  is small, then  $e^{-2\alpha L} \approx 1 - 2\alpha L$ , using the truncated series expansion  $e^x \approx 1 + x$  if  $x \ll 1$ . Then (4) becomes

$$P_d \approx P_+ [1 - (1 - 2\alpha L)] = 2\alpha L P_+ \quad (5)$$

Consequently, using (3) & (5) in (2) gives

$$Q \approx \omega \frac{P_+ \frac{L}{v_p}}{2\alpha L P_+} = \frac{\omega v_p}{2\alpha}$$


or

$$\underline{\underline{Q \approx \frac{\beta}{2\alpha}}} \quad (6)$$


## ● Open-circuited TL -



$$Z_{in} \rightarrow Z_0, \gamma, v_p$$

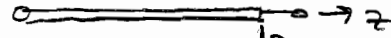

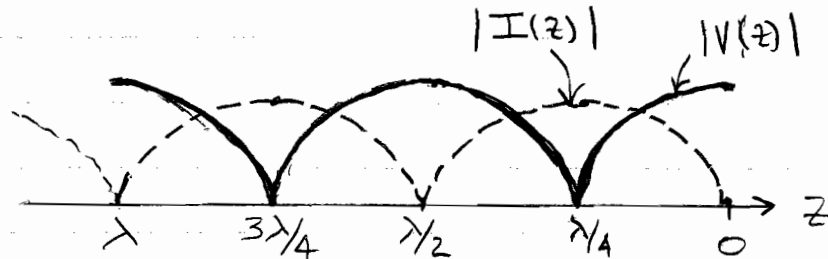For a nearly lossless open-circuited TLs:



$$\rightarrow \text{At } z = \frac{n\lambda}{2}, \quad Z_{in} \approx \infty, \quad n=1, 2, 3, \dots$$

$$\rightarrow \text{At } z = \frac{n\lambda}{4}, \quad Z_{in} \approx 0, \quad n=1, 3, 5, \dots$$

Borzi shows that near frequencies where  $L \approx \frac{n\lambda}{2}$ ,  $n=1, 2, 3, \dots$ ,  $Z_{in}(\omega)$  has the form of a parallel resonant ckt. Conversely, near frequencies where  $L \approx \frac{n\lambda}{4}$ ,  $n=1, 3, 5, \dots$ , the  $Z_{in}(\omega)$  has the form of a series resonant ckt.


The derivation of  $Q$  for the open-ckt termination is identical to s.c. termination. Hence, for a open-ckt terminated TL resonator  $Q$  is

$$Q \approx \frac{\beta}{2\alpha}$$



Applications are many in microwave ckt's, though few at RF because of length of coax.

### Examples

- Notch filter in microstrip.

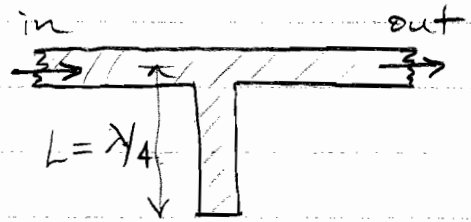

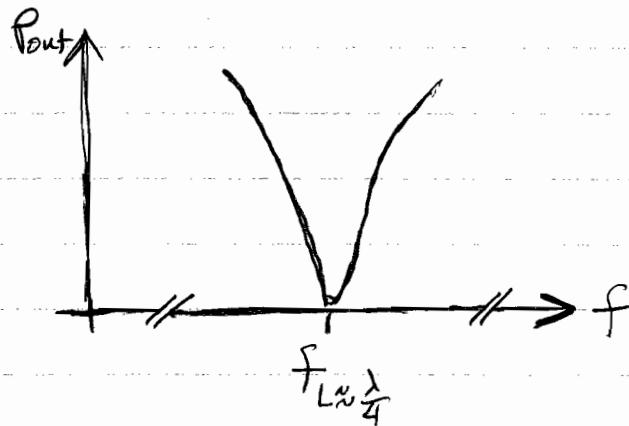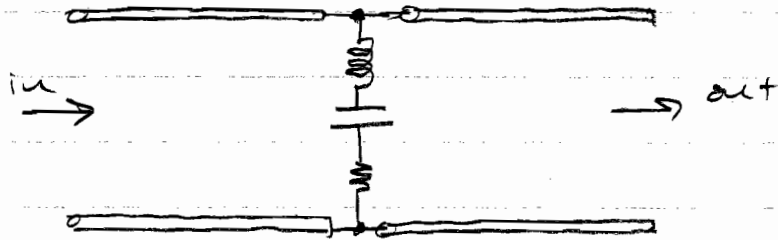Near the frequency where  $L \approx \lambda/4$ , equivalent input impedance of O.C. TL is a series resonant ckt:



Behaves as a notch filter.