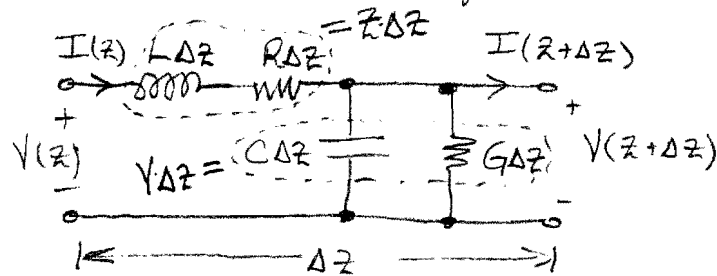


The first fixture we'll use to extract material parameters from samples placed within them is a shorted coaxial line.

We model this structure as a transmission line (TL); in particular, a lossy TL.

The lumped ckt model for an infinitesimal section of a TL is



- $R$  is due to conductor losses in the metal parts of the coax.
- $G$  is due to losses in the material between the conductors.  
(Note that  $G \neq \frac{1}{R}$ )

The phasor-domain telegrapher's eqns for this lossy TL are:

$$\frac{dV(z)}{dz} = -Z I(z) \quad (1)$$

$$\frac{dI(z)}{dz} = -Y V(z) \quad (2)$$

$$\text{where } Z = R + j\omega L \quad \& \quad Y = G + j\omega C \quad (3), (4)$$

(1) and (2) can be combined in ways to produce second-order ODE'S for  $V(z)$  and  $I(z)$  as:

$$\frac{d^2 V(z)}{dz^2} - \gamma^2 V(z) = 0 \quad (5)$$

and

$$\frac{d^2 I(z)}{dz^2} - \gamma^2 I(z) = 0 \quad (6)$$

$$\text{where } \gamma^2 = Z \cdot Y = (R + j\omega L)(G + j\omega C) \quad (7)$$

(S.t.  $\gamma = \pm \sqrt{\gamma^2}$  need to be aware of this!)

Solutions to (5) & (6) are

$$V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z} \quad (8)$$

$$I(z) = \frac{V_0^+}{Z_0} e^{-\gamma z} - \frac{V_0^-}{Z_0} e^{+\gamma z} \quad (9)$$



$$\text{where } Z_0 = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{R + j\omega L}{G + j\omega C}}.$$

The propagation constant  $\gamma$  is a complex quantity, as we can deduce from (7). We define the real & imag. parts of  $\gamma$  as

$$\gamma \equiv \alpha + j\beta \quad (10)$$

Hence, the voltage & current waves in (8) & (9) are attenuated as they propagate.

ref 322  
notes for  
figs.

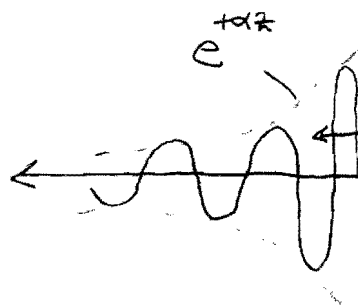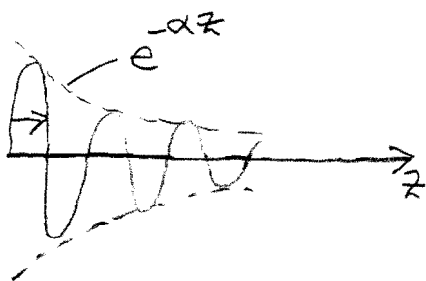

Another non-ideal characteristic of lossy TL's is the signal dispersion, which occurs when the signal velocity is a fun. of frequency.

Phase velocity on a lossy line is given by the same expression as a lossless line,

$$v_p = \frac{\omega}{\beta} \quad (11)$$

where  $\beta = \alpha \operatorname{Im}(\gamma)$ , and will not <sup>generally</sup> be proportional to  $\omega$  for a lossy line. (Exception is Heaviside dispersionless TL where  $R/L = G/C$ . In this case,  $\alpha$  and  $v_p$  are not funs. of  $\omega$ !)